

# Lecture 2

## Basic Laws


# Basic Laws

In order to determine circuit parameters (Resistance, Voltage, Current, Power, etc.)

- Resistance
- Ohm's Law
- Kirchhoff's Law

# Resistance

- Materials in general have a characteristic behavior of resisting the flow of electric charge.
- This physical property, or ability to resist current, is known as ***resistance***.
- Copper, aluminum have low resistivities and mica, paper have high resistivities

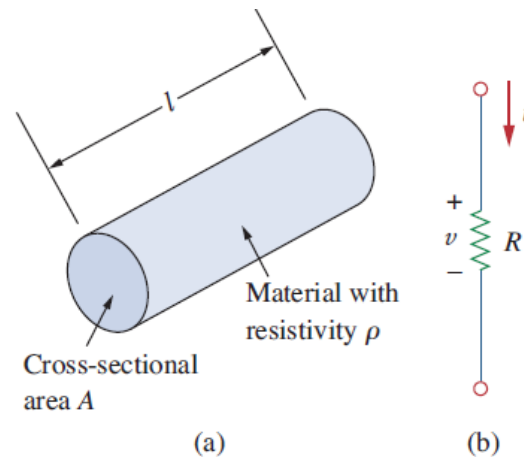

**Figure 2.1**

(a) Resistor, (b) Circuit symbol for resistance.

$$R = \rho \frac{\ell}{A}$$

# Resistance

**TABLE 2.1**

Resistivities of common materials.

Material	Resistivity ( $\Omega \cdot \text{m}$ )	Usage
Silver	$1.64 \times 10^{-8}$	Conductor
Copper	$1.72 \times 10^{-8}$	Conductor
Aluminum	$2.8 \times 10^{-8}$	Conductor
Gold	$2.45 \times 10^{-8}$	Conductor
Carbon	$4 \times 10^{-5}$	Semiconductor
Germanium	$47 \times 10^{-2}$	Semiconductor
Silicon	$6.4 \times 10^2$	Semiconductor
Paper	$10^{10}$	Insulator
Mica	$5 \times 10^{11}$	Insulator
Glass	$10^{12}$	Insulator
Teflon	$3 \times 10^{12}$	Insulator


# Ohm's Law

- Ohm's law states that the voltage  $v$  across a resistor is directly proportional to the current  $i$  flowing through the resistor.
- $R$  represents the constant of proportionality denoted by ohm's


$$v \propto i$$

$$v = iR$$

# Ohm's Law

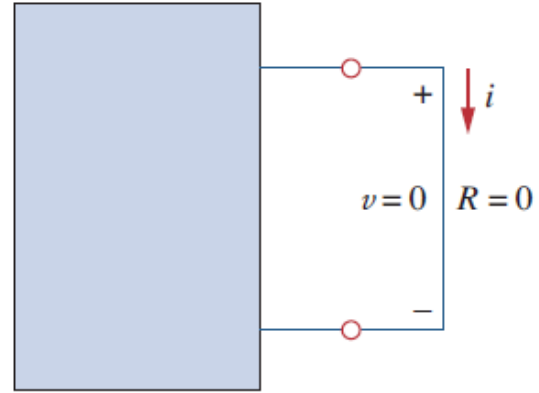

(a)

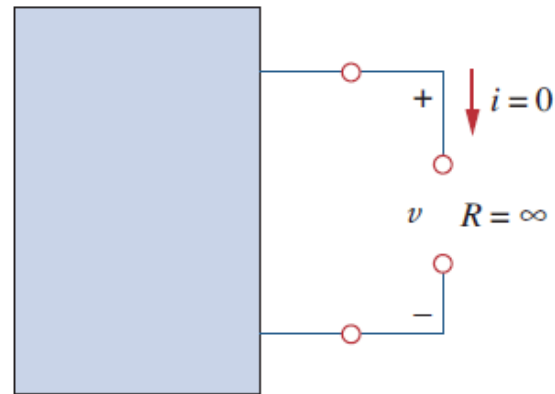


(b)

**Figure 2.2**


(a) Short circuit ( $R = 0$ ), (b) Open circuit ( $R = \infty$ ).

# Ohm's Law

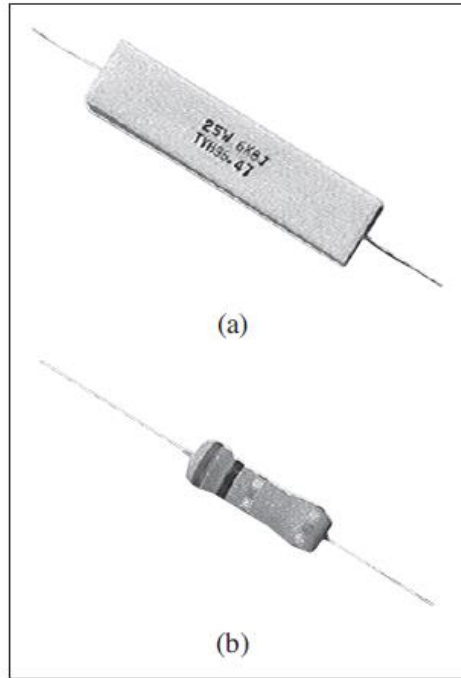

**Figure 2.3**

Fixed resistors: (a) wirewound type,  
(b) carbon film type.  
Courtesy of Tech America.

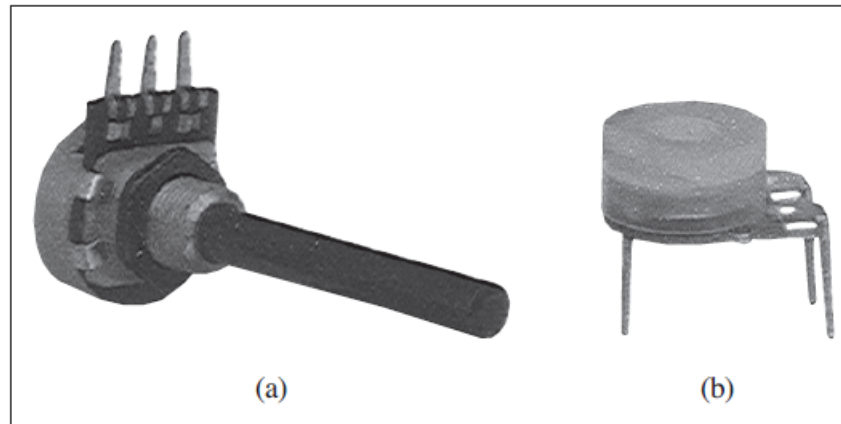


**Figure 2.5**

Variable resistors: (a) composition type, (b) slider pot.  
Courtesy of Tech America.

# Ohm's Law

In the circuit shown in Fig. 2.8, calculate the current  $i$ , the conductance  $G$ , and the power  $p$ .

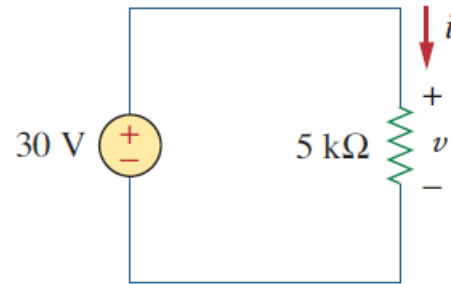

**Figure 2.8**  
For Example 2.2.



# Ohm's Law

## **Solution:**

The voltage across the resistor is the same as the source voltage (30 V) because the resistor and the voltage source are connected to the same pair of terminals. Hence, the current is

$$i = \frac{v}{R} = \frac{30}{5 \times 10^3} = 6 \text{ mA}$$

The conductance is

$$G = \frac{1}{R} = \frac{1}{5 \times 10^3} = 0.2 \text{ mS}$$

We can calculate the power in various ways using either Eqs. (1.7), (2.10), or (2.11).

$$p = vi = 30(6 \times 10^{-3}) = 180 \text{ mW}$$


or

$$p = i^2R = (6 \times 10^{-3})^2 5 \times 10^3 = 180 \text{ mW}$$

or

$$p = v^2G = (30)^2 0.2 \times 10^{-3} = 180 \text{ mW}$$

# Nodes, Branches, and Loops

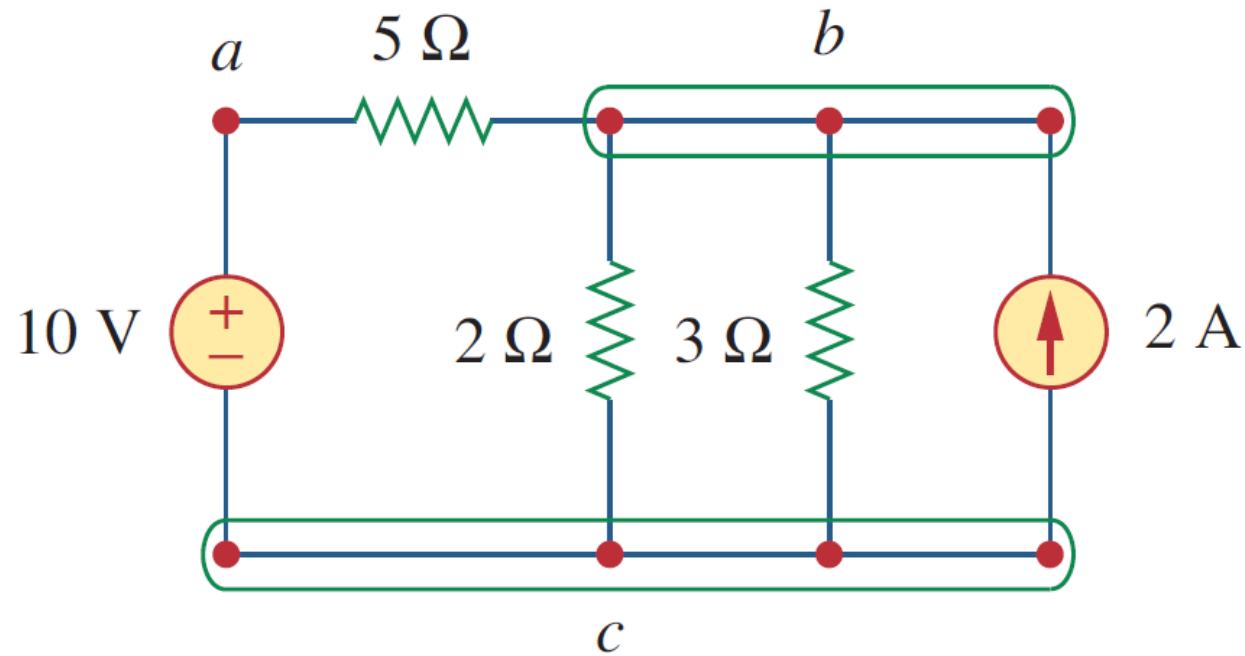

**Figure 2.10**

Nodes, branches, and loops.


# Kirchhoff's Laws

- How to pronounce **Kirchhoff**?
- (কিরচফ, কিরকফ)

# Kirchhoff's Laws

- KCL- It states that the algebraic sum of currents entering a node (or a closed boundary) is zero.

$$\sum_{n=1}^N i_n = 0$$

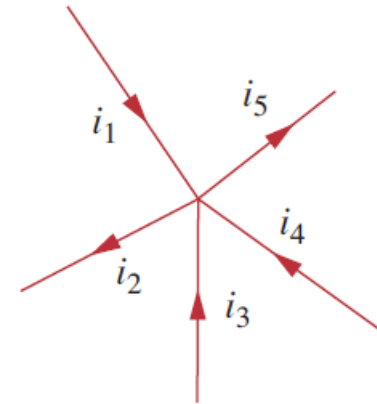


**Figure 2.16**

Currents at a node illustrating KCL.

# Kirchhoff's Laws

- KVL- Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.

$$\sum_{m=1}^M v_m = 0$$

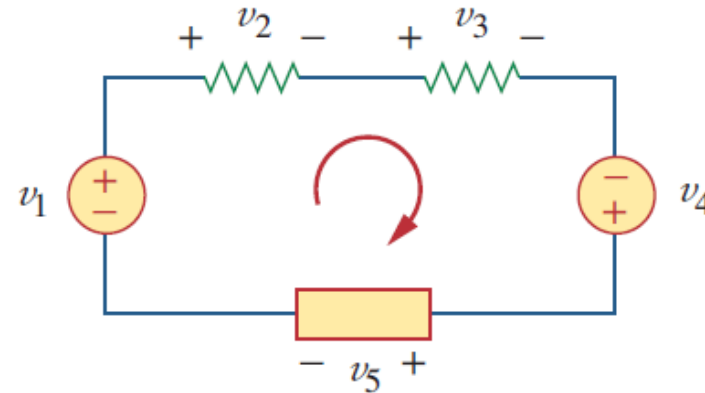


**Figure 2.19**

A single-loop circuit illustrating KVL.

# Kirchhoff's Laws

- KVL- Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.

$$\sum_{m=1}^M v_m = 0$$

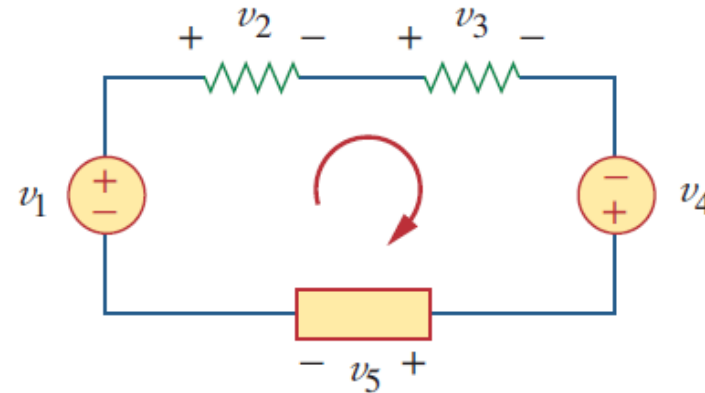


**Figure 2.19**

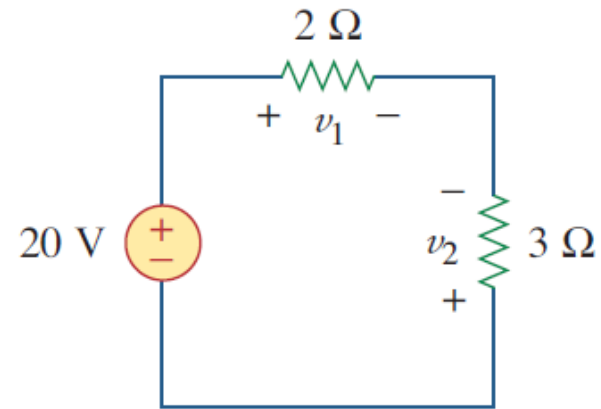
A single-loop circuit illustrating KVL.

# Kirchhoff's Laws

For the circuit in Fig. 2.21(a), find voltages  $v_1$  and  $v_2$ .



(a)

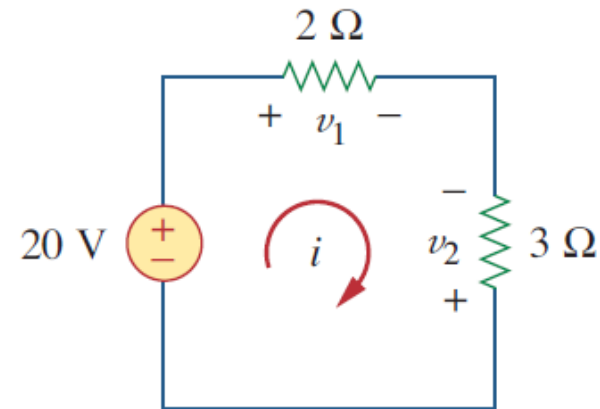

(b)

**Figure 2.21**  
For Example 2.5.

# Kirchhoff's Laws

## **Solution:**

To find  $v_1$  and  $v_2$ , we apply Ohm's law and Kirchhoff's voltage law. Assume that current  $i$  flows through the loop as shown in Fig. 2.21(b). From Ohm's law,

$$v_1 = 2i, \quad v_2 = -3i \quad (2.5.1)$$

Applying KVL around the loop gives

$$-20 + v_1 - v_2 = 0 \quad (2.5.2)$$

Substituting Eq. (2.5.1) into Eq. (2.5.2), we obtain

$$-20 + 2i + 3i = 0 \quad \text{or} \quad 5i = 20 \quad \Rightarrow \quad i = 4 \text{ A}$$


Substituting  $i$  in Eq. (2.5.1) finally gives

$$v_1 = 8 \text{ V}, \quad v_2 = -12 \text{ V}$$



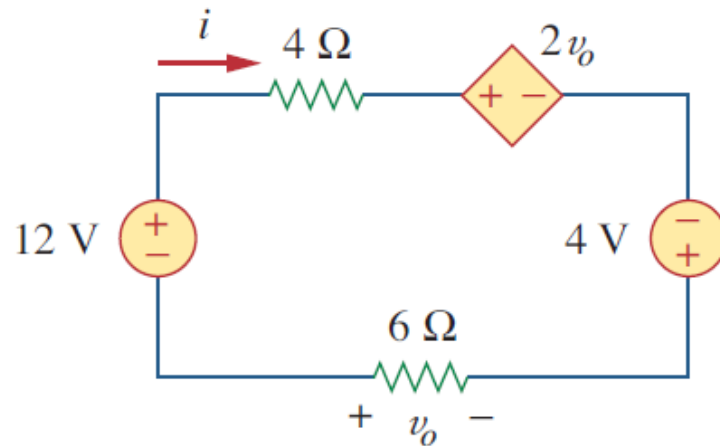
# Kirchhoff's Laws

Determine  $v_o$  and  $i$  in the circuit shown in Fig. 2.23(a).



(a)

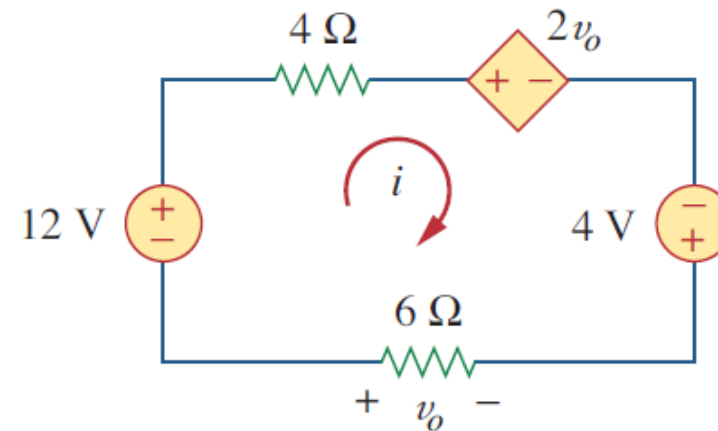

(b)

**Figure 2.23**

For Example 2.6.

# Kirchhoff's Laws

## **Solution:**

We apply KVL around the loop as shown in Fig. 2.23(b). The result is

$$-12 + 4i + 2v_o - 4 + 6i = 0 \quad (2.6.1)$$

Applying Ohm's law to the 6- $\Omega$  resistor gives

$$v_o = -6i \quad (2.6.2)$$

Substituting Eq. (2.6.2) into Eq. (2.6.1) yields

$$-16 + 10i - 12i = 0 \quad \Rightarrow \quad i = -8 \text{ A}$$

and  $v_o = 48 \text{ V}$ .