

Sheikh Hasina University, Netrokona
Department of Computer Science and Engineering
CSE-2205: Introduction to Mechatronics

Lec-25: Programmable Logic Controller (PLC)


Mechatronics: Electronic Control Systems in Mechanical Engineering by W. Bolton

Md. Ariful Islam
Assistant Professor
Dept. of Robotics and Mechatronics Engineering
University of Dhaka
&
Adjunct Faculty
Sheikh Hasina University, Netrokona
Department of Computer Science and Engineering

Function blocks:



FBD

Ladder
FBD

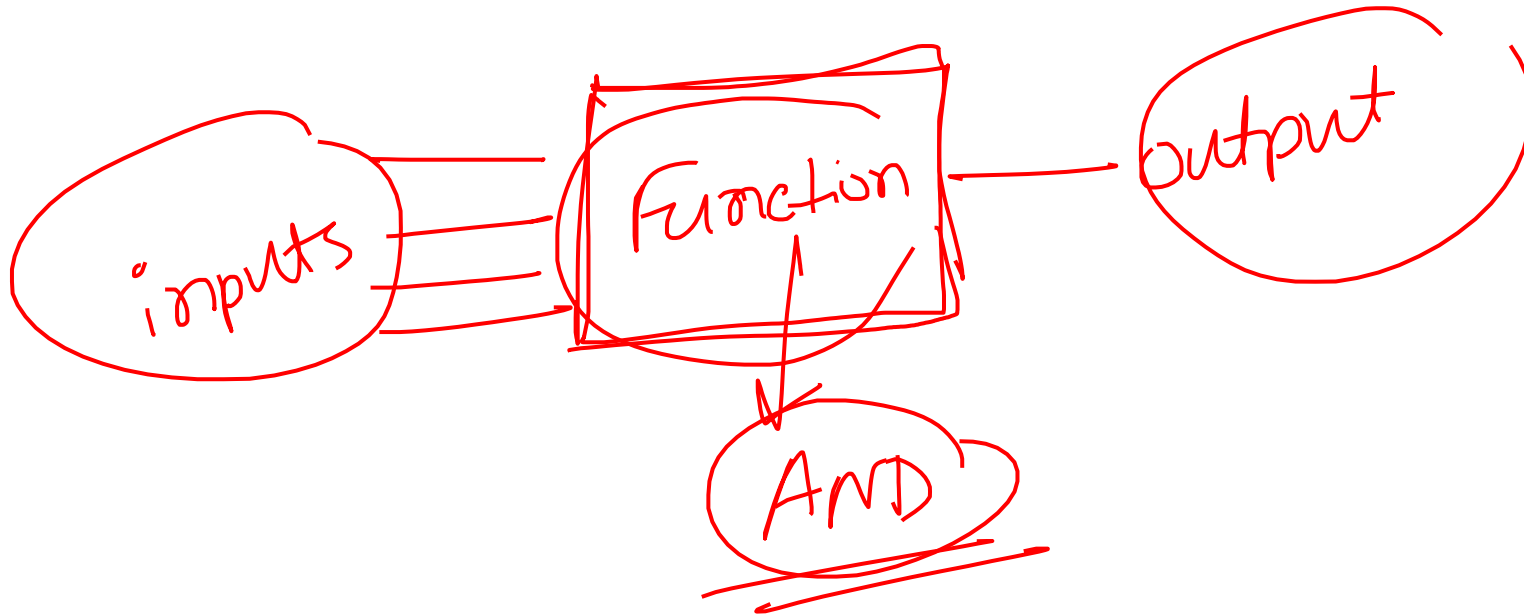


Logic Gates:


NOT Gate:

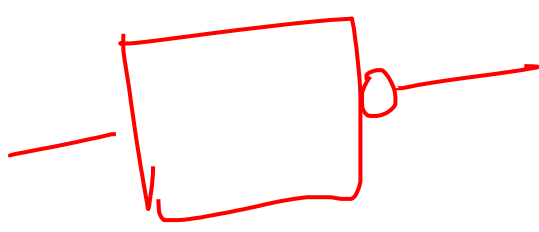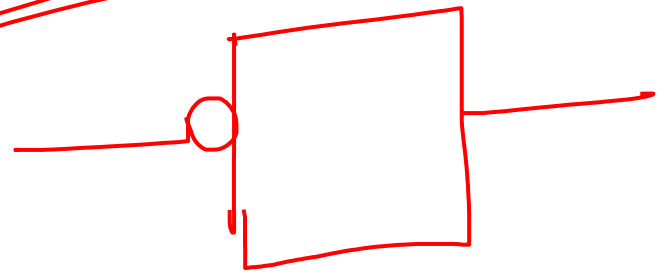


AND:

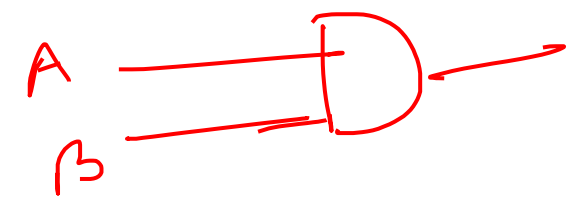


OR:

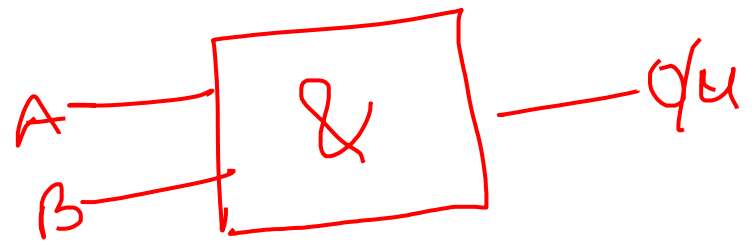


OR

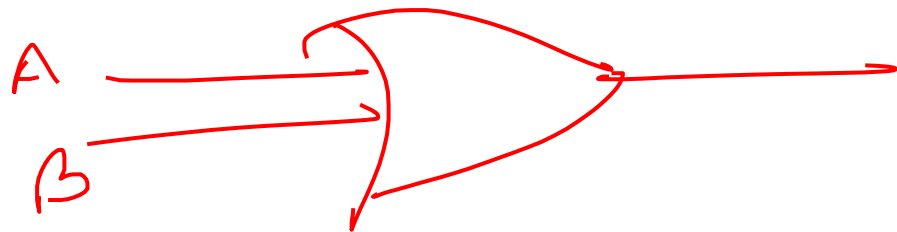


FBD

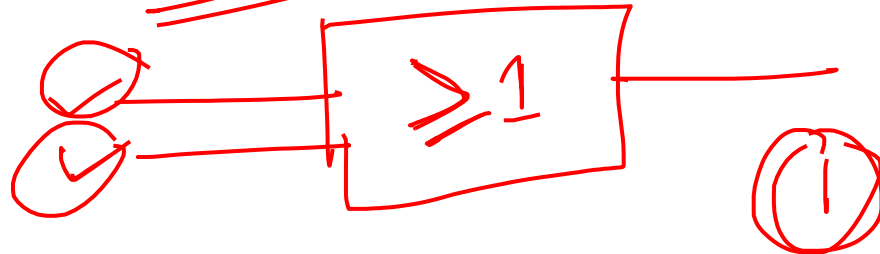

NAND.


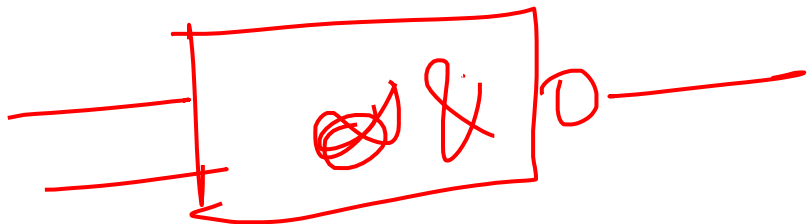


NOR:

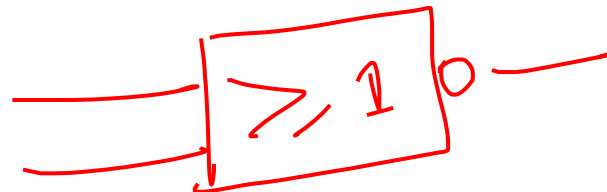


XOR



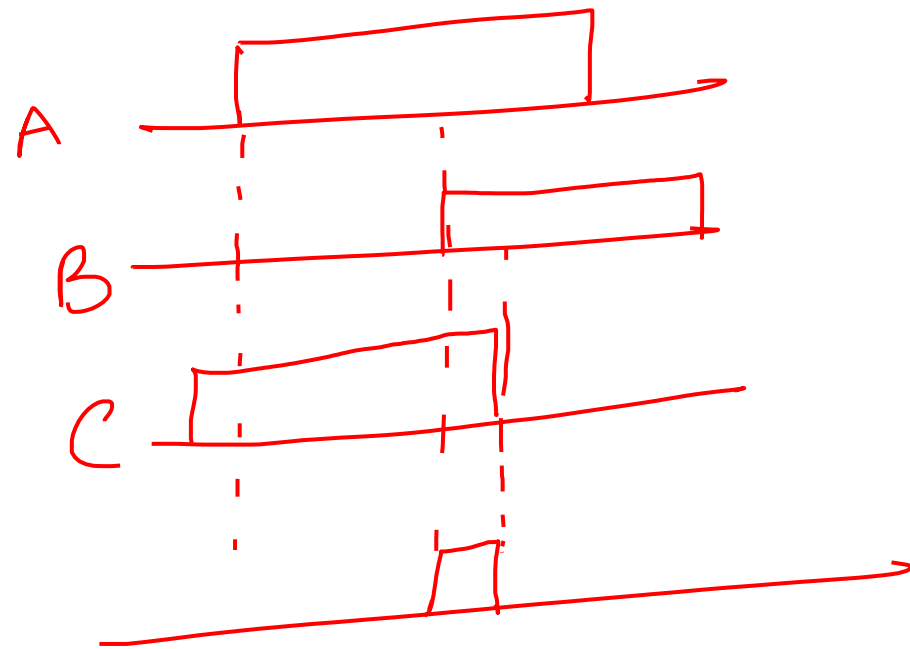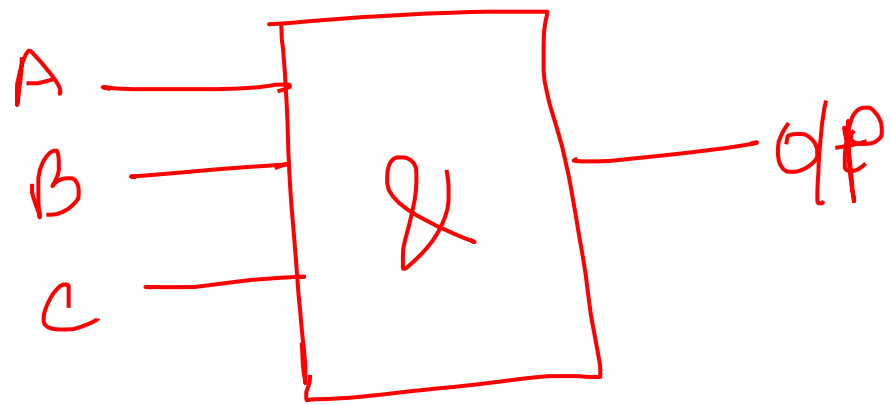


O/P

Ladder


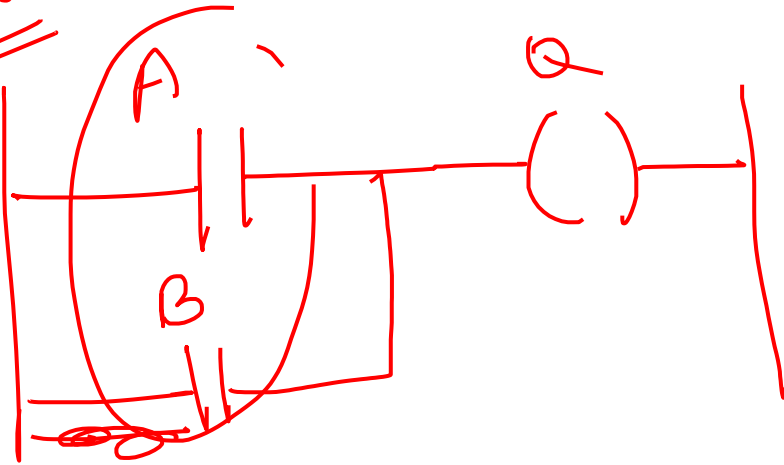


FBD

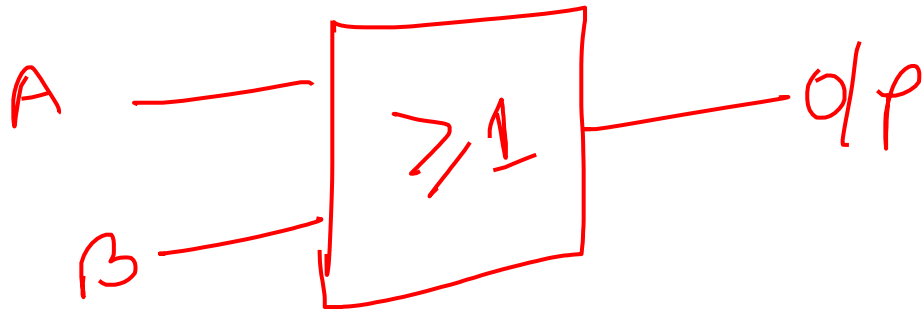



Program examples

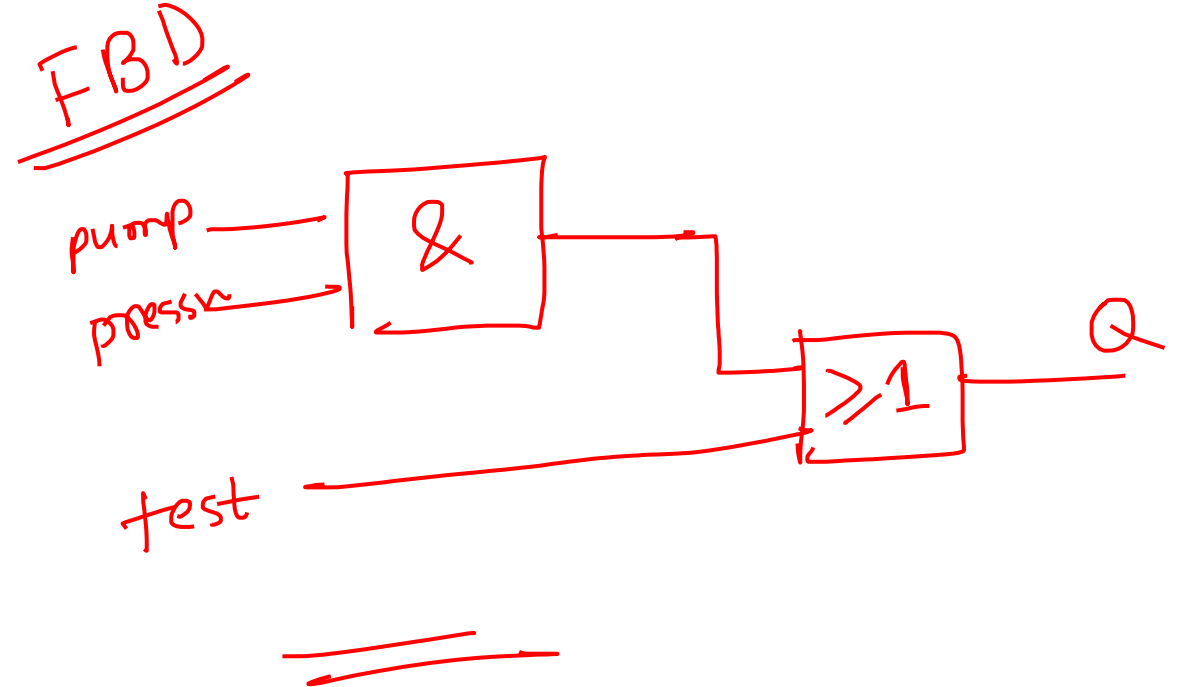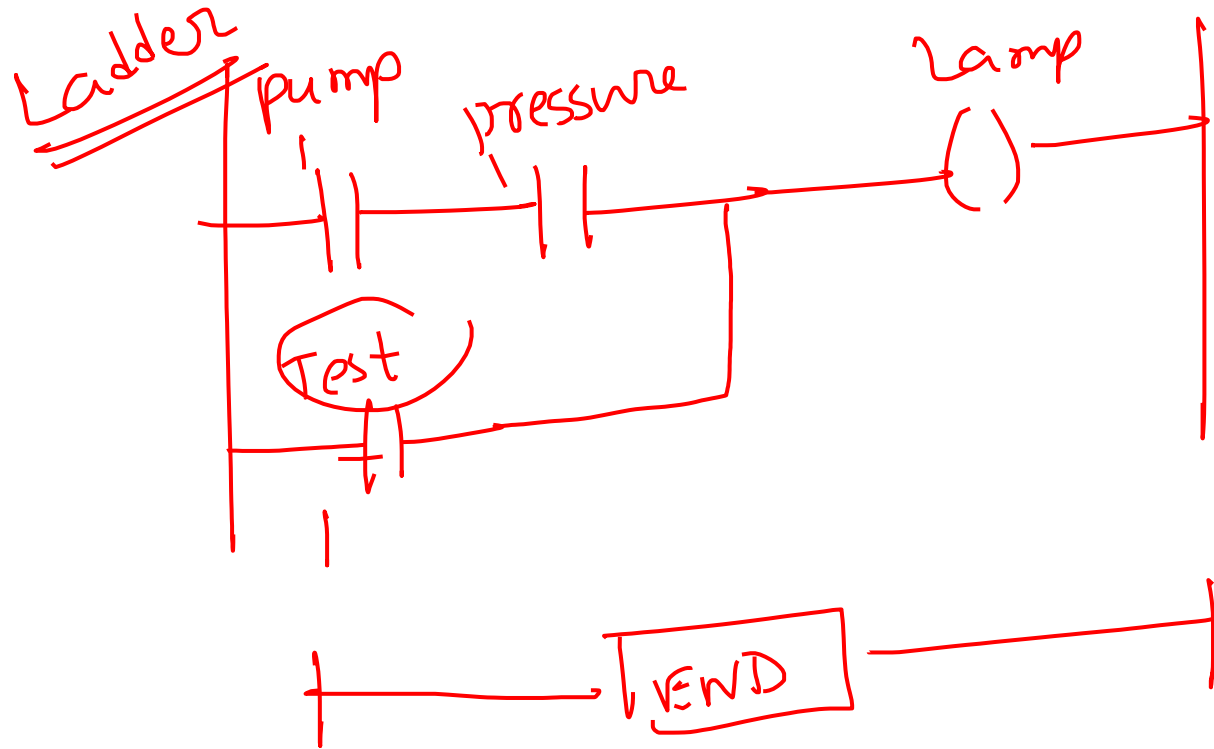1. A signal lamp is required to be switched on if a pump is running and the pressure is satisfactory, or if the lamp test switch is closed.



Program examples

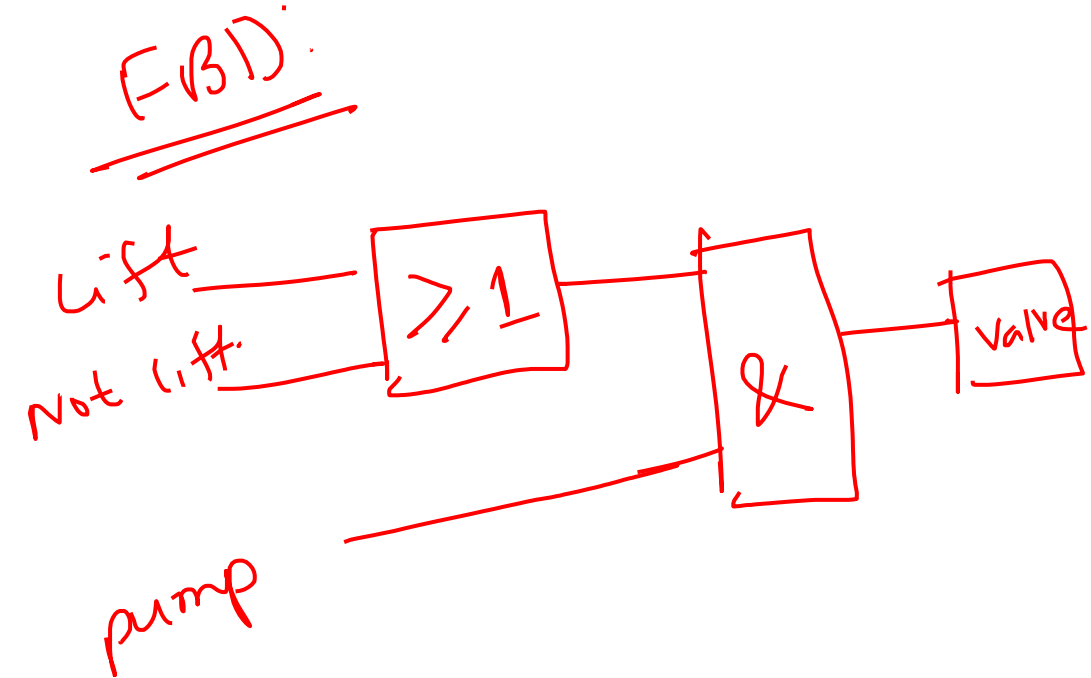
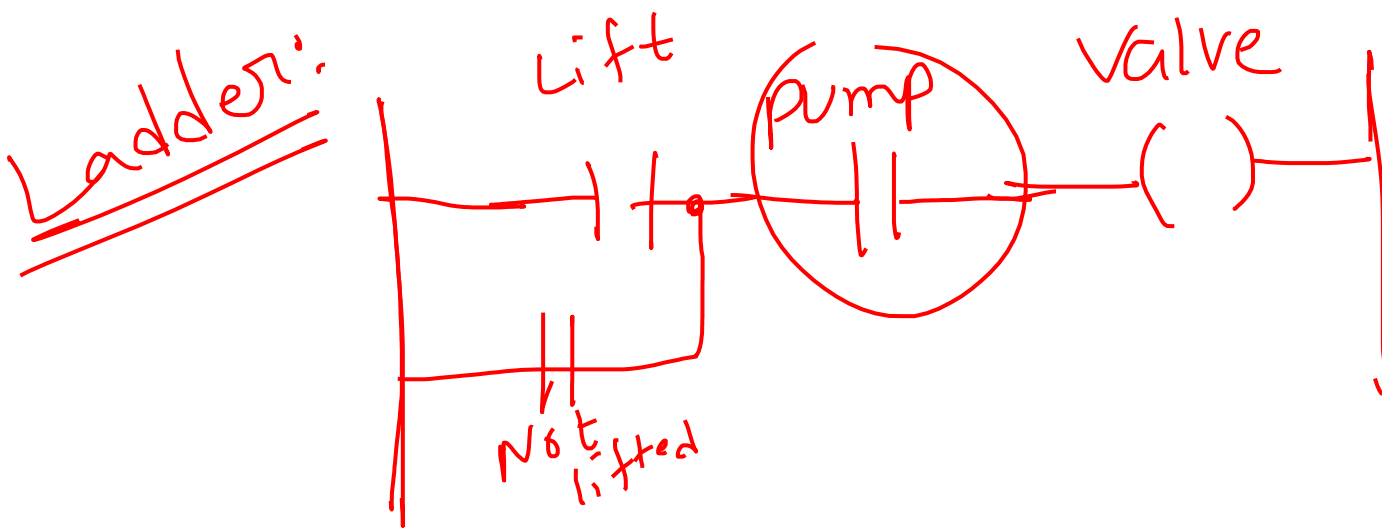
2. Consider a valve which is to be operated to lift a load when a pump is running and either the lift switch is operated or a switch operated indicating that the load has not already been lifted and is at the bottom of its lift channel.




Program examples

3. Consider a system where there has to be no output when any one of four sensors gives an output, otherwise there is to be an output.

Ladder:

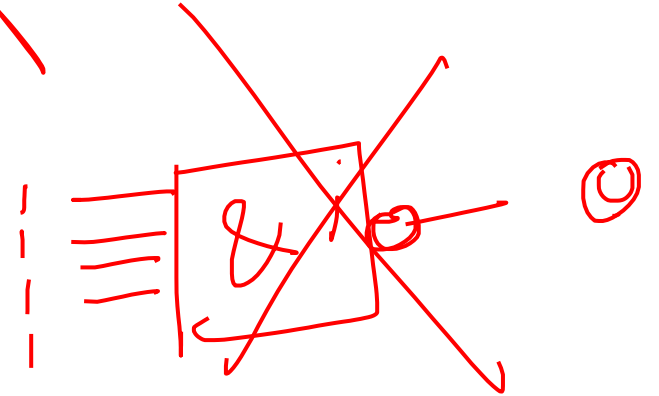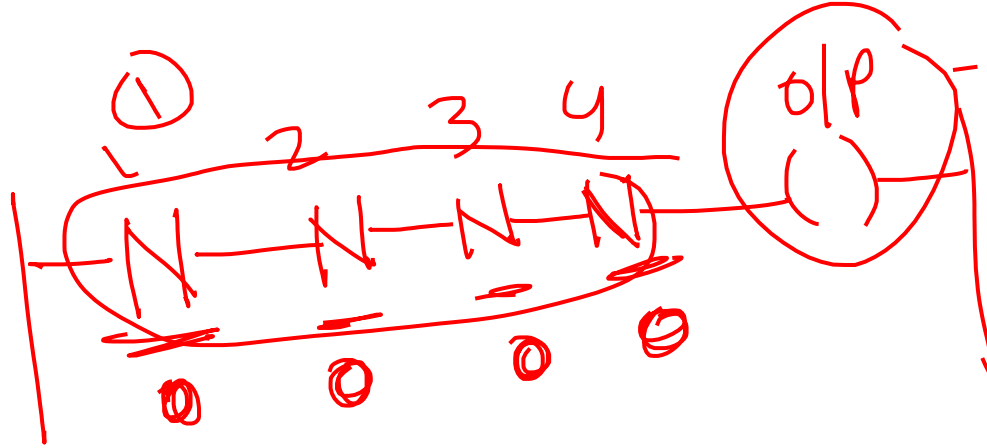

FBD

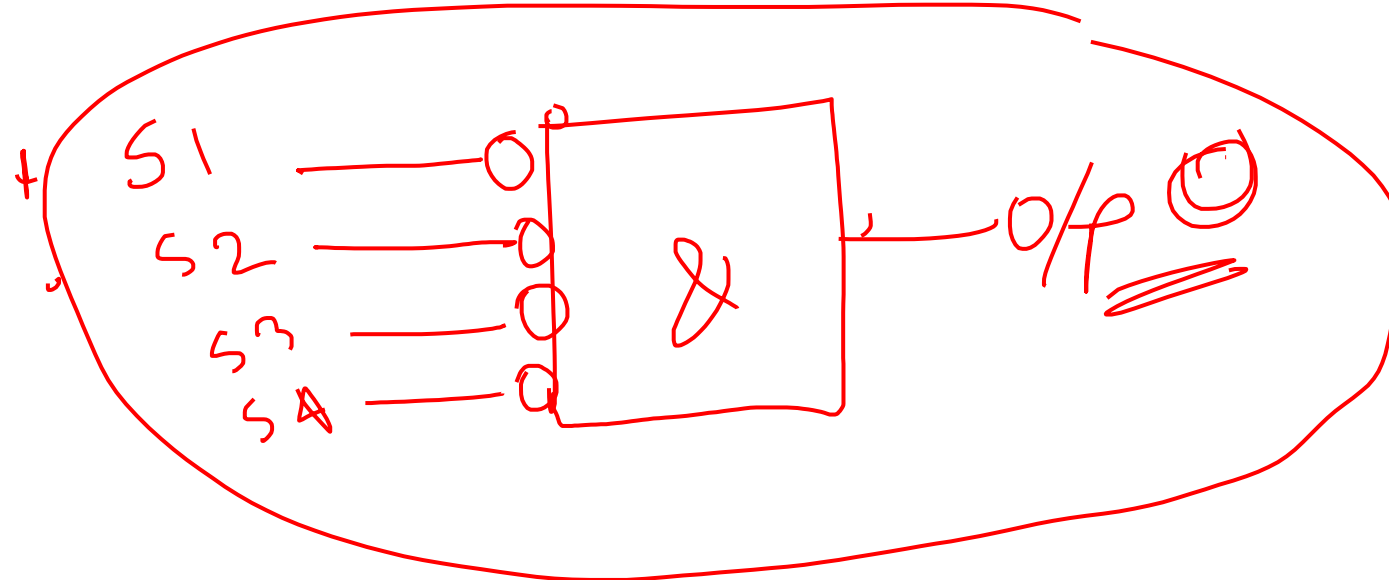


Internal Relays:

data (bits)

address



Security example.

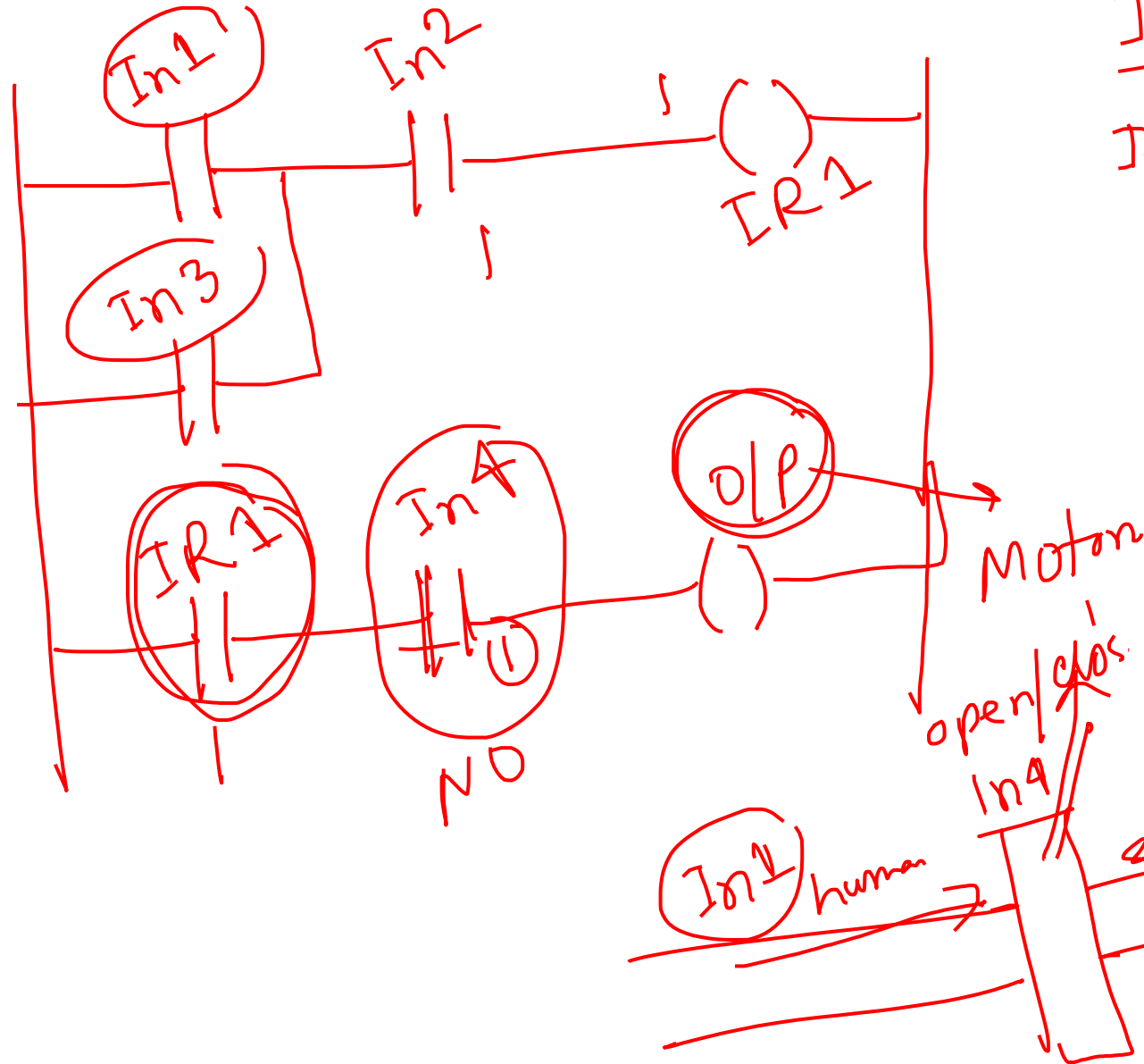

Inputs:

In1 = Sensor on one side



In2 = Enable switch


In3 = Sensor on other side

In4 = Limit switch

Latching
resetting

Latching

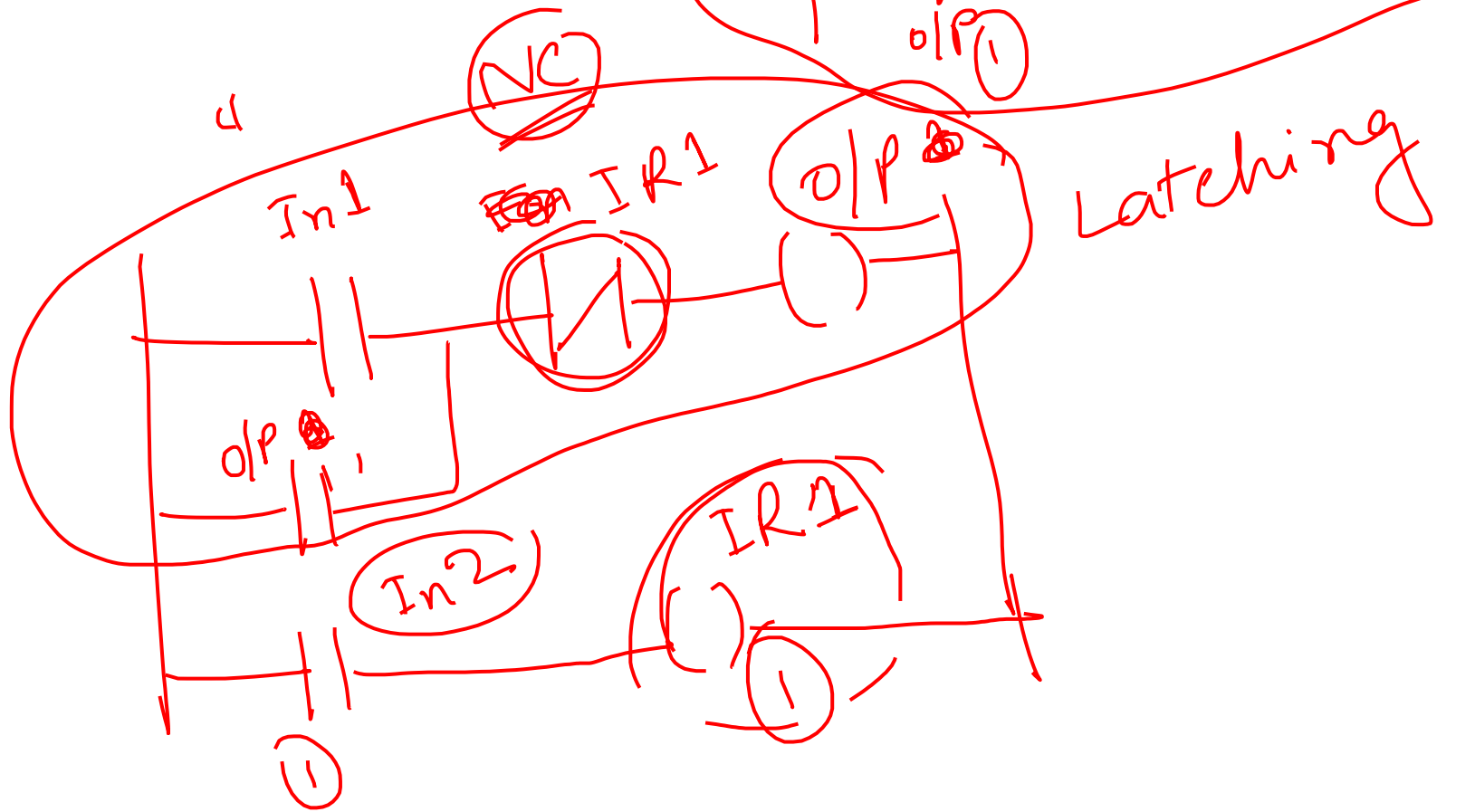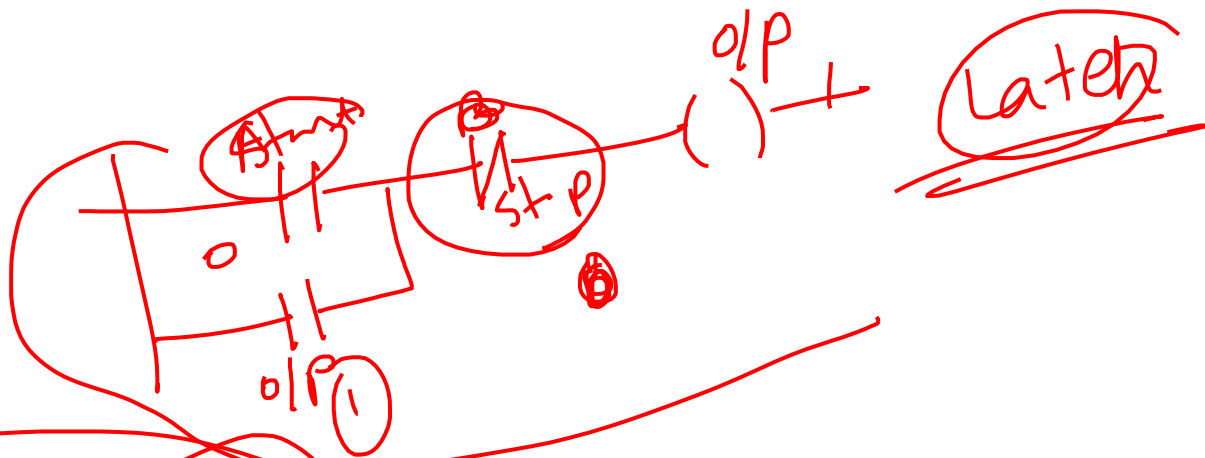

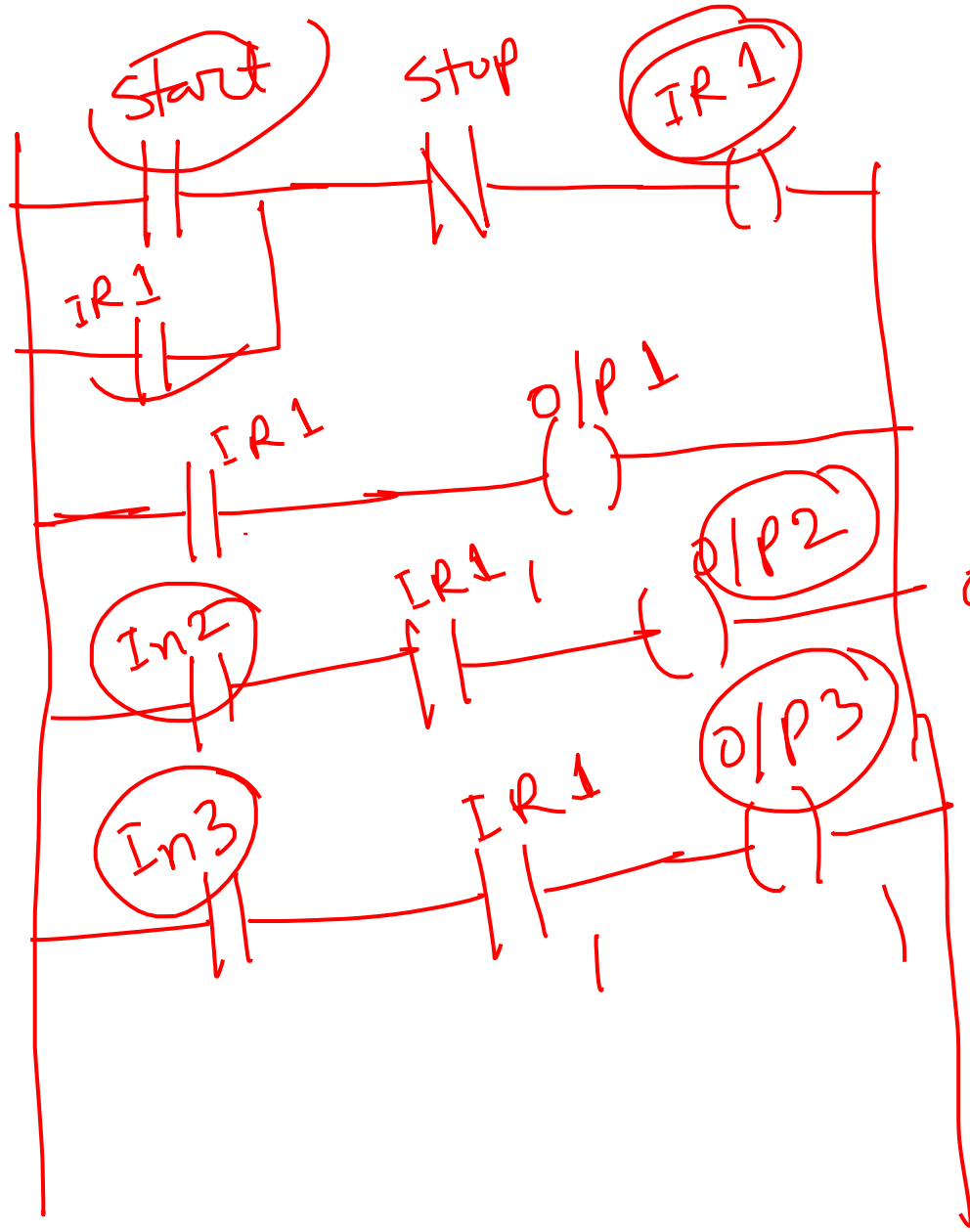


power on-off → on


O/P2 ✓

O/P3 ✓
Starting of
Multiple outputs

Battery Backed Relay


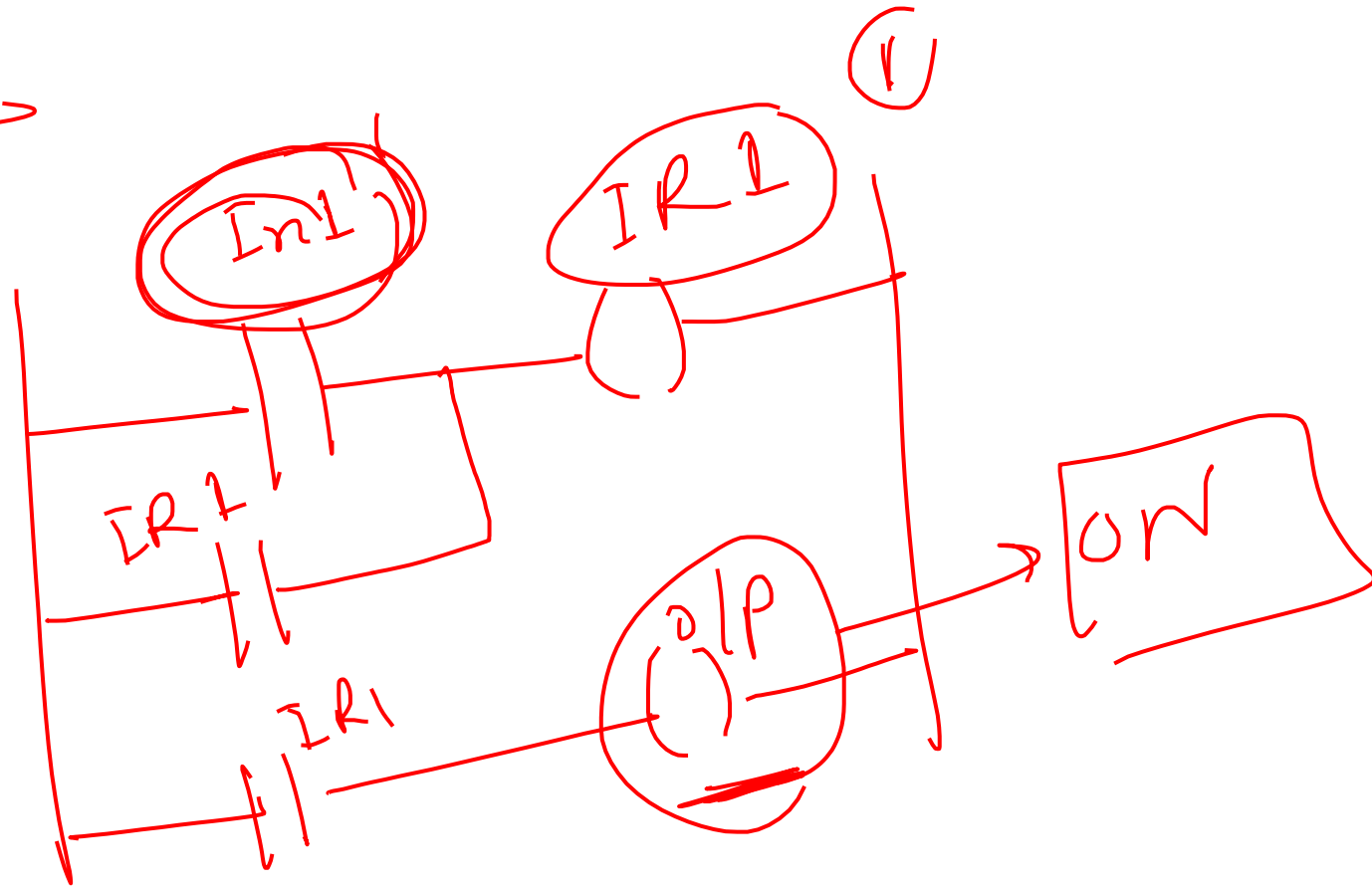



One-shot operation

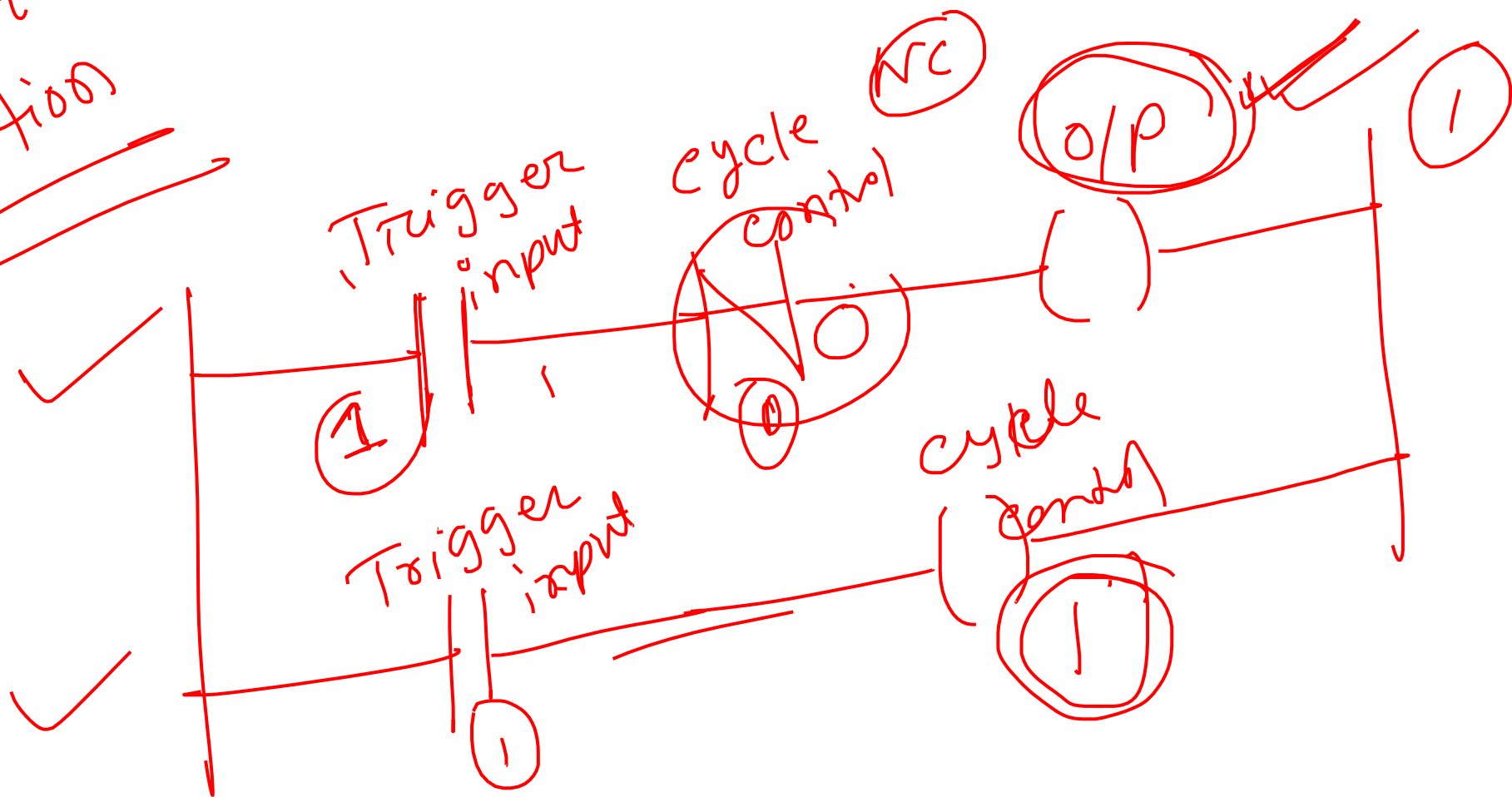

SET &
RESET

Flip-flop

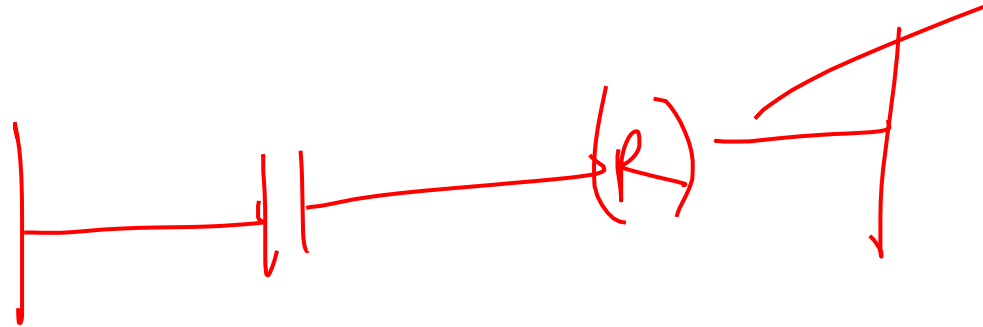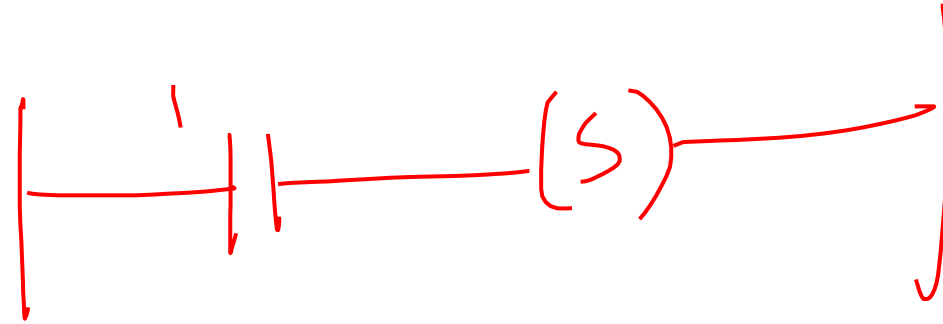

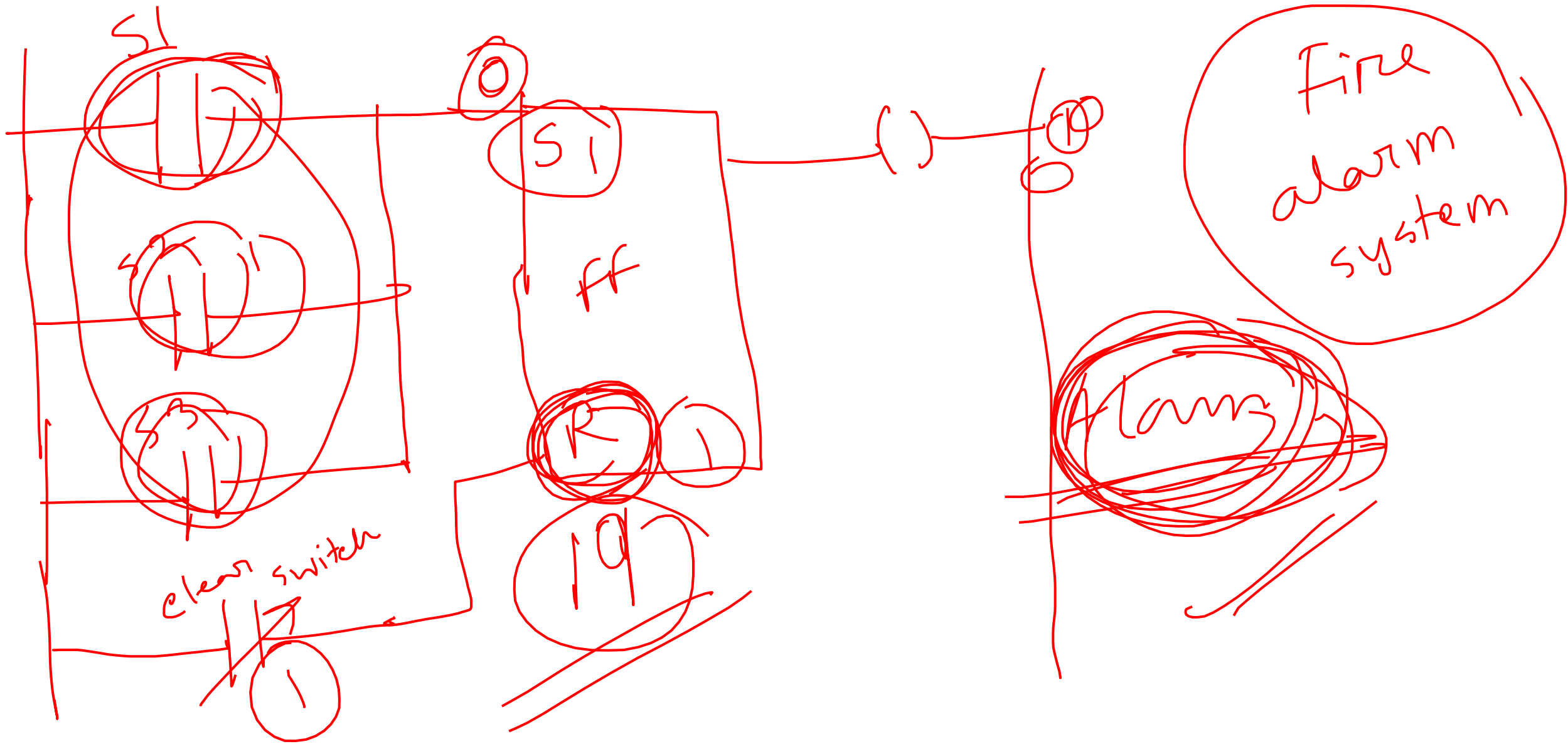

S-R flip-flop:

| S | R | clk | Q |
|---|---|-----|---------|
| | | ↑ | N.C |
| 0 | 0 | ↑ | 0 ✓ |
| 0 | 1 | ↑ | 1 ✓ |
| 1 | 0 | ↑ | Invalid |
| 1 | 1 | ↑ | Invalid |

①
0

J-K flip-flop
Toggle