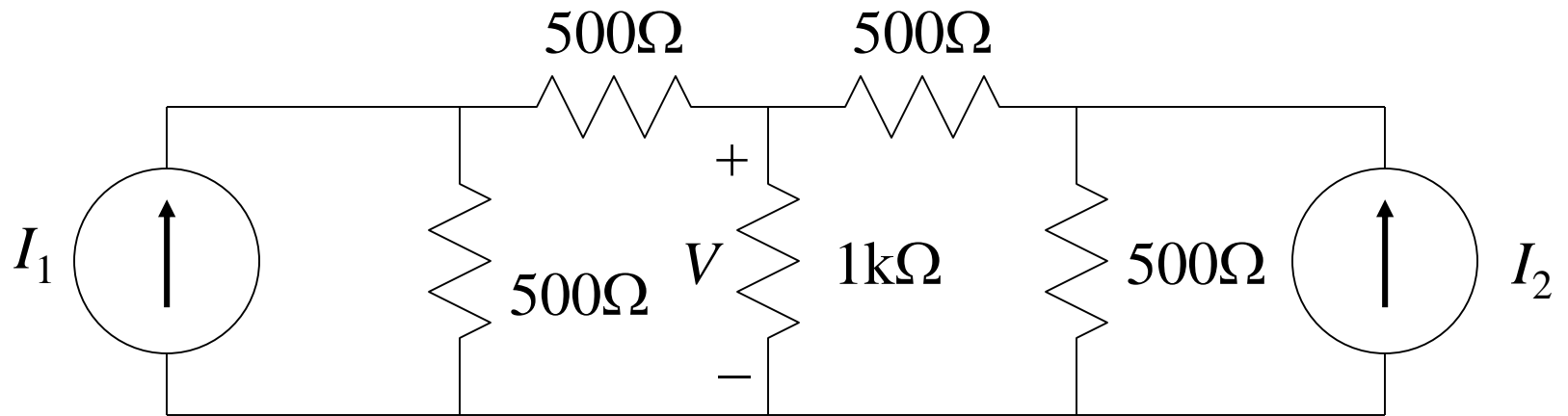


# Nodal Analysis

Ariful Islam

Assistant Professor, Dept. of EEE,  
University of Dhaka

# Summing Circuit



*Solution:*  $V = 167I_1 + 167I_2$

Can you analyze this circuit using  
the techniques of Chapter 2?

# Not This One!

- There are no series or parallel resistors to combine.
- We do not have a single loop or a double node circuit.
- We need a more powerful analysis technique:

## Nodal Analysis

# Why Nodal or Loop Analysis?

- The analysis techniques in Chapter 2 (voltage divider, equivalent resistance, etc.) provide an intuitive approach to analyzing circuits.
- They cannot analyze all circuits.
- They cannot be easily automated by a computer.


# Node and Loop Analysis

- Node analysis and loop analysis are both circuit analysis methods which are systematic and apply to most circuits.
- Analysis of circuits using node or loop analysis requires solutions of systems of linear equations.
- These equations can usually be written by inspection of the circuit.

# Steps of Nodal Analysis

- 1. Choose a reference node.**
2. Assign node voltages to the other nodes.
3. Apply KCL to each node other than the reference node; express currents in terms of node voltages.
4. Solve the resulting system of linear equations.

# Reference Node

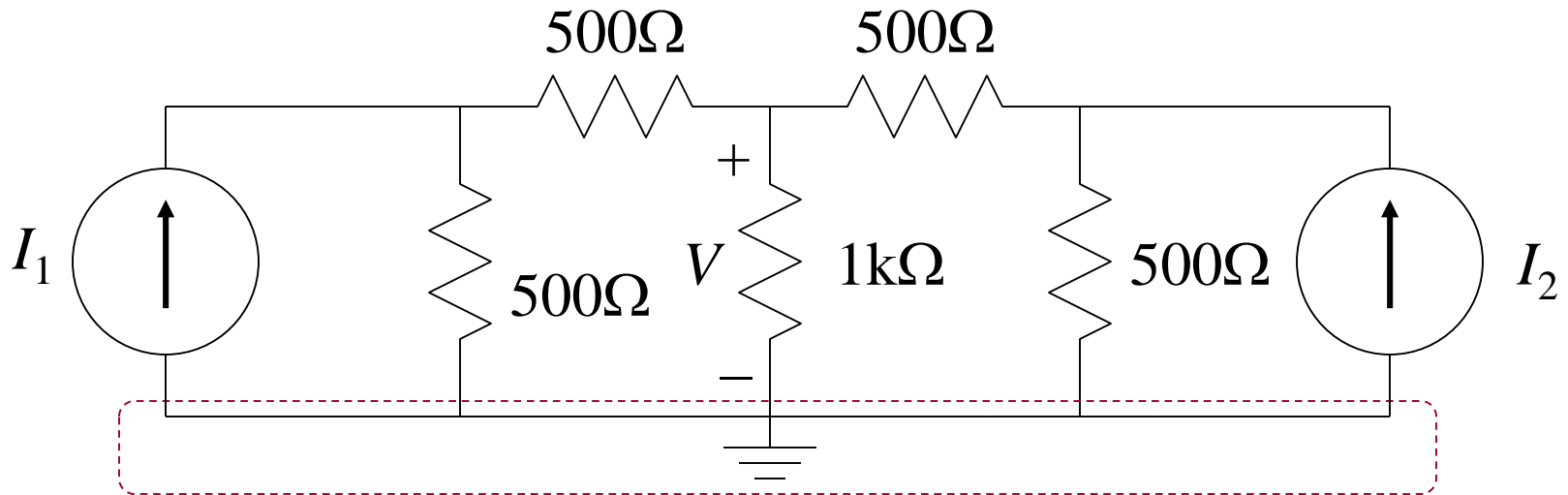


The reference node is called the *ground* node.



# Steps of Nodal Analysis

1. Choose a reference node.
- 2. Assign node voltages to the other nodes.**
3. Apply KCL to each node other than the reference node; express currents in terms of node voltages.
4. Solve the resulting system of linear equations.

# Node Voltages


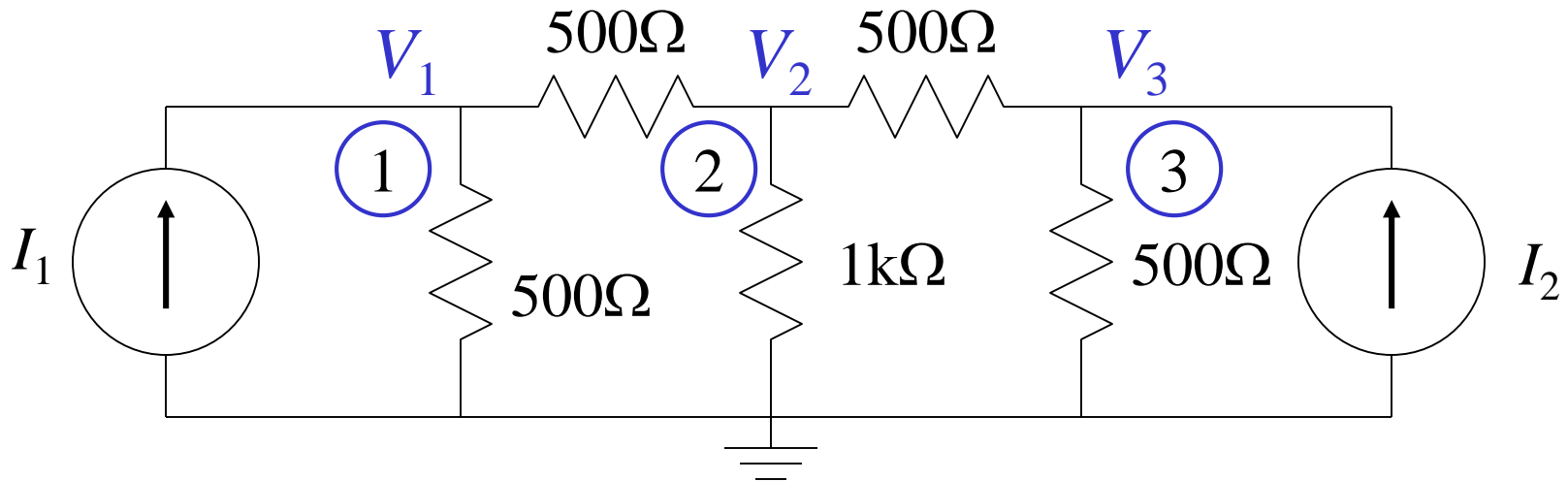


$V_1$ ,  $V_2$ , and  $V_3$  are unknowns for which we solve using KCL.


# Steps of Nodal Analysis

1. Choose a reference node.
2. Assign node voltages to the other nodes.
- 3. Apply KCL to each node other than the reference node; express currents in terms of node voltages.**
4. Solve the resulting system of linear equations.

# Currents and Node Voltages

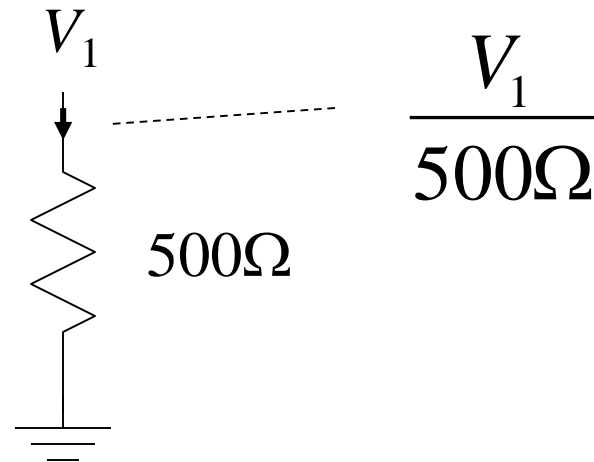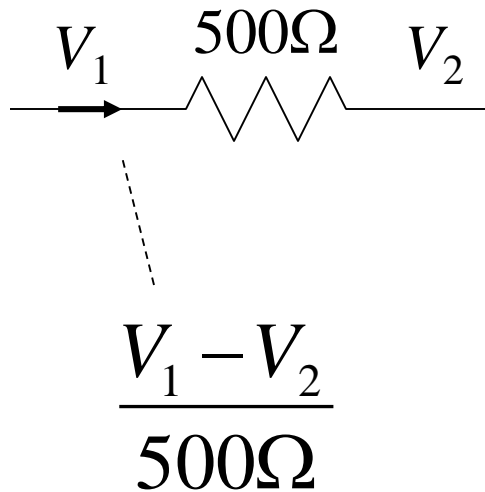


# KCL at Node 1

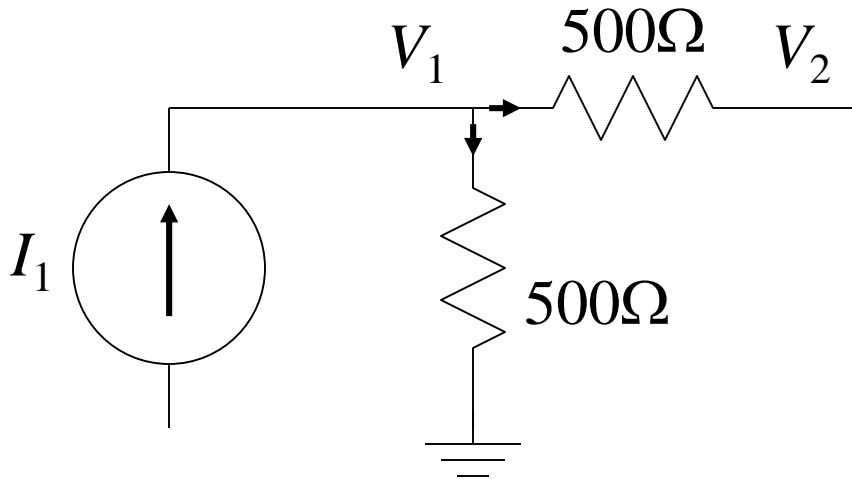


$$I_1 = \frac{V_1 - V_2}{500\Omega} + \frac{V_1}{500\Omega}$$

## KCL at Node 2

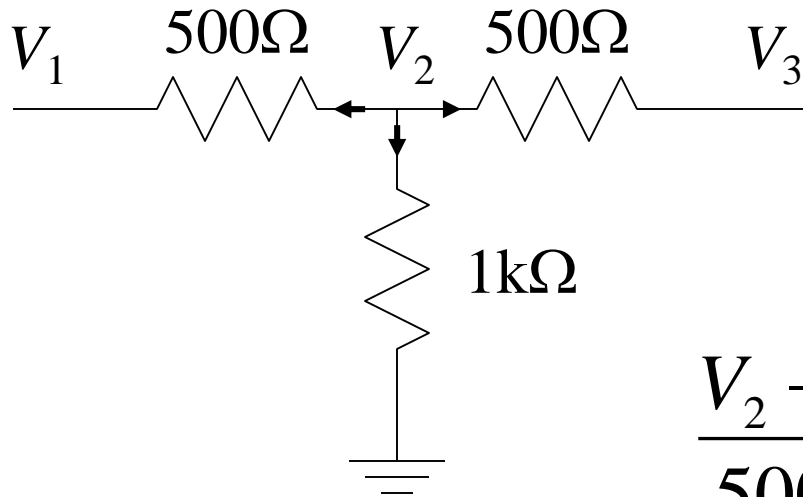

$$\frac{V_2 - V_1}{500\Omega} + \frac{V_2}{1\text{k}\Omega} + \frac{V_2 - V_3}{500\Omega} = 0$$

## KCL at Node 3

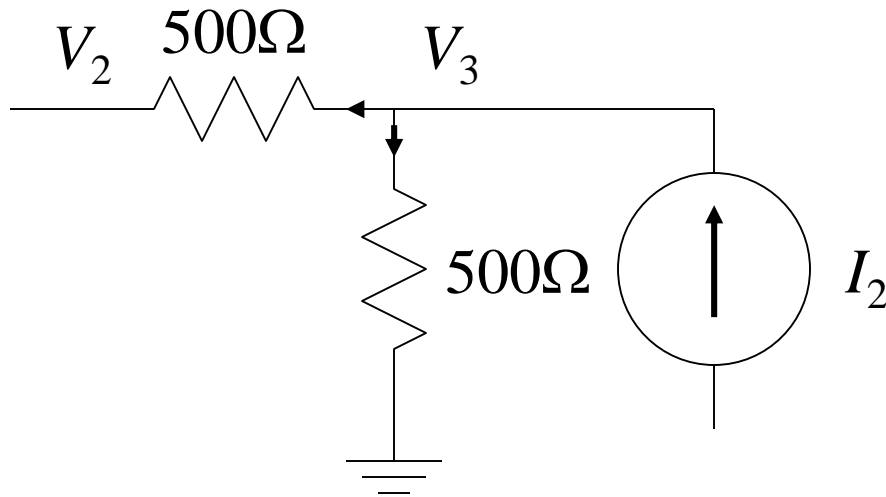

$$\frac{V_3 - V_2}{500\Omega} + \frac{V_3}{500\Omega} = I_2$$

# Steps of Nodal Analysis

1. Choose a reference node.
2. Assign node voltages to the other nodes.
3. Apply KCL to each node other than the reference node; express currents in terms of node voltages.
- 4. Solve the resulting system of linear equations.**



# System of Equations

- Node 1:

$$V_1 \left( \frac{1}{500\Omega} + \frac{1}{500\Omega} \right) - \frac{V_2}{500\Omega} = I_1$$

- Node 2:

$$-\frac{V_1}{500\Omega} + V_2 \left( \frac{1}{500\Omega} + \frac{1}{1k\Omega} + \frac{1}{500\Omega} \right) - \frac{V_3}{500\Omega} = 0$$

# System of Equations

- Node 3:

$$-\frac{V_2}{500\Omega} + V_3\left(\frac{1}{500\Omega} + \frac{1}{500\Omega}\right) = I_2$$

# Equations

- These equations can be written by inspection.
- The left side of the equation:
  - The node voltage is multiplied by the sum of *conductances* of all resistors connected to the node.
  - Other node voltages are multiplied by the conductance of the resistor(s) connecting to the node and subtracted.

# Equations

- The right side of the equation:
  - The right side of the equation is the sum of currents from sources entering the node.

# Matrix Notation

- The three equations can be combined into a single matrix/vector equation.

$$\begin{bmatrix} \frac{1}{500\Omega} + \frac{1}{500\Omega} & -\frac{1}{500\Omega} & 0 \\ -\frac{1}{500\Omega} & \frac{1}{500\Omega} + \frac{1}{1\text{k}\Omega} + \frac{1}{500\Omega} & -\frac{1}{500\Omega} \\ 0 & -\frac{1}{500\Omega} & \frac{1}{500\Omega} + \frac{1}{500\Omega} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ 0 \\ I_2 \end{bmatrix}$$

# Matrix Notation

- The equation can be written in matrix-vector form as

$$\mathbf{A}\mathbf{v} = \mathbf{i}$$

- The solution to the equation can be written as

$$\mathbf{v} = \mathbf{A}^{-1} \mathbf{i}$$

# Solving the Equation with MATLAB

$$I_1 = 3\text{mA}, I_2 = 4\text{mA}$$

```
>> A = [1/500+1/500  -1/500  0;  
        -1/500  1/500+1/1000+1/500  -1/500;  
        0  -1/500  1/500+1/500];  
>> i = [3e-3; 0; 4e-3];
```

# Solving the Equation

```
>> v = inv(A) * i
```

```
v =
```

```
1.3333
```


```
1.1667
```

```
1.5833
```

$$V_1 = 1.33\text{V}, V_2=1.17\text{V}, V_3=1.58\text{V}$$



**Nodal Analysis: Example 6.2, using circuit values.**

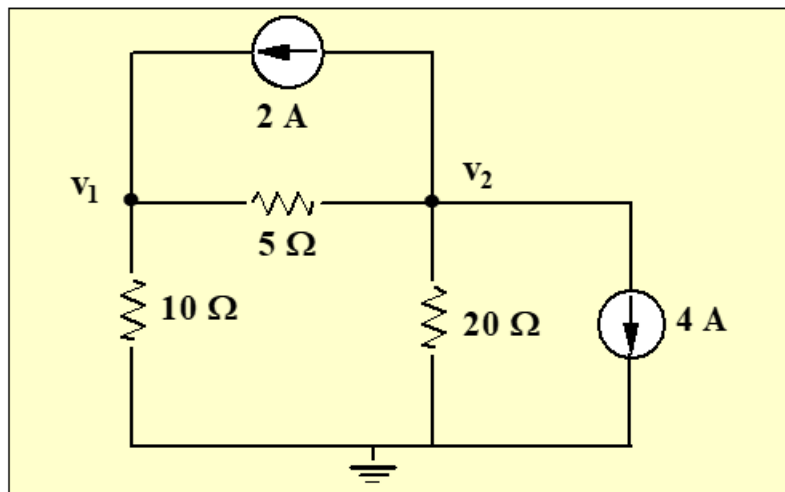


**Figure 6.3: Circuit for Example 6.2.**

**Find  $V_1$  and  $V_2$ .**

# Basic Circuits

**Nodal Analysis: Example 6.2, using circuit values.**

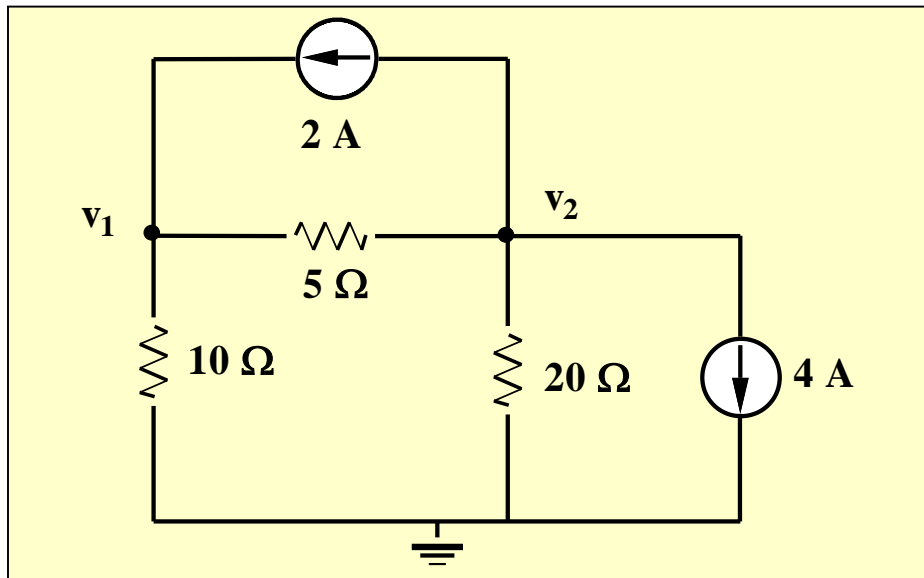

**Figure 6.3: Circuit for Example 6.2.**

**Find  $V_1$  and  $V_2$ .**

**At  $v_1$ :**

$$\frac{V_1}{10} + \frac{V_1 - V_2}{5} = 2$$

**Eq 6.7**

**At  $v_2$ :**

$$\frac{V_2 - V_1}{5} + \frac{V_2}{20} = -6$$

**Eq 6.8**

# Basic Circuits

## Nodal Analysis: Example 6.2: Clearing Equations;

From Eq 6.7:

$$V_1 + 2V_1 - 2V_2 = 20$$

or

$$3V_1 - 2V_2 = 20$$

Eq 6.9

From Eq 6.8:

$$4V_2 - 4V_1 + V_2 = -120$$

or

$$-4V_1 + 5V_2 = -120$$

Eq 6.10

$$\text{Solution: } V_1 = -20 \text{ V, } V_2 = -40 \text{ V}$$

# Basic Circuits

## Nodal Analysis: Example 6.3: With voltage source.

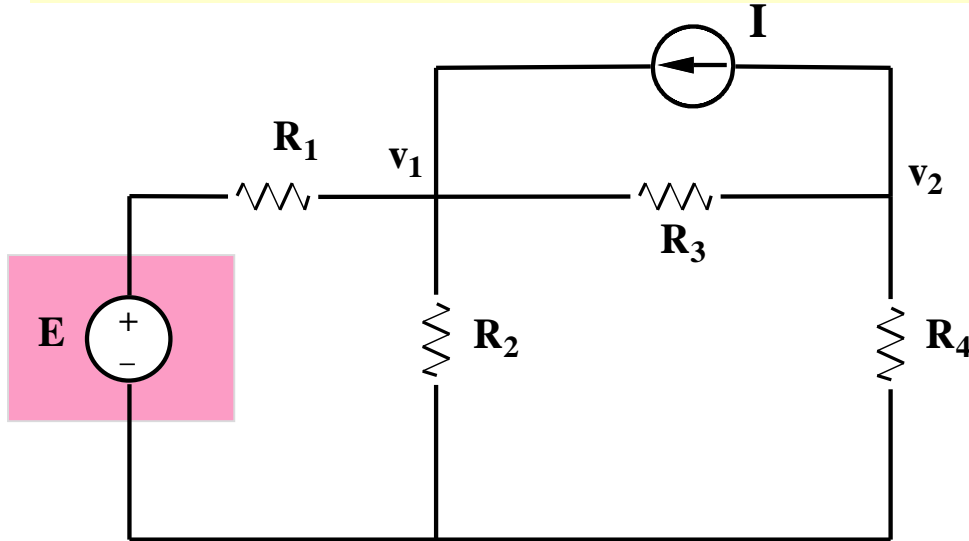


Figure 6.4: Circuit for Example 6.3.

At  $V_1$ :

$$\frac{V_1 - E}{R_1} + \frac{V_1}{R_2} + \frac{V_1 - V_2}{R_3} = I$$

Eq 6.11

At  $V_2$ :

$$\frac{V_2}{R_4} + \frac{V_2 - V_1}{R_3} = -I$$

Eq 6.12

# Basic Circuits

## Nodal Analysis: Example 6.3: Continued.


Collecting terms in Equations (6.11) and (6.12) gives

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)V_1 - \left(\frac{1}{R_3}\right)V_2 = I + \frac{E}{R_1} \quad \text{Eq 6.13}$$

$$-\left(\frac{1}{R_2}\right)V_1 + \left(\frac{1}{R_3} + \frac{1}{R_4}\right)V_2 = -I \quad \text{Eq 6.14}$$

# Basic Circuits

**Nodal Analysis: Example 6.4: Numerical example with voltage source.**

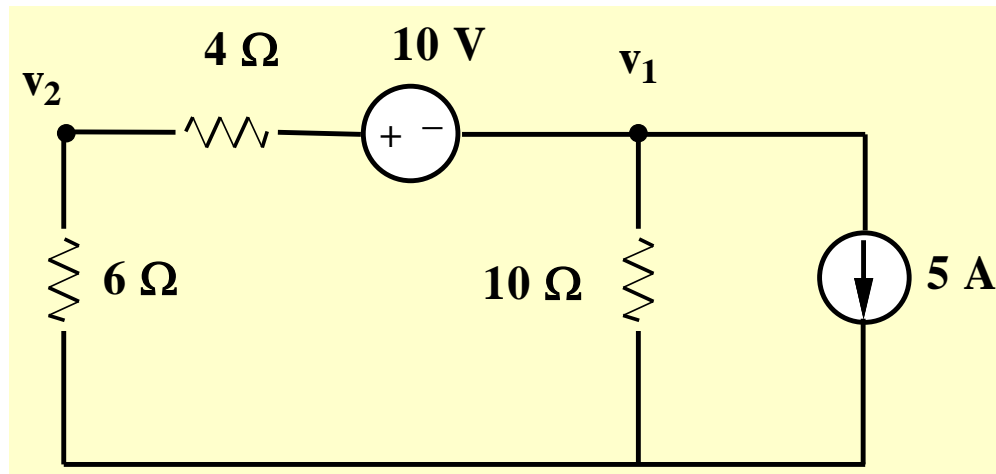


**Figure 6.5: Circuit for Example 6.4.**

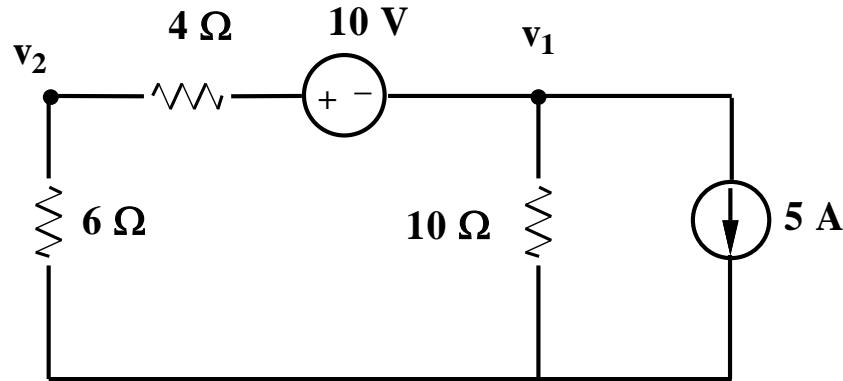What do we do first?

# Basic Circuits

## Nodal Analysis: Example 6.4: Continued



At  $v_1$ :

$$\frac{V_1}{10} + \frac{V_1 + 10 - V_2}{4} = -5 \quad \text{Eq 6.15}$$

At  $v_2$ :

$$\frac{V_2}{6} + \frac{V_2 - 10 - V_1}{4} = 0 \quad \text{Eq 6.16}$$

# Basic Circuits

## Nodal Analysis: Example 6.4: Continued

Clearing Eq 6.15

$$4V_1 + 10V_1 + 100 - 10V_2 = -200$$

or

$$14V_1 - 10V_2 = -300$$

Eq 6.17

Clearing Eq 6.16

$$4V_2 + 6V_2 - 60 - 6V_1 = 0$$

or

$$-6V_1 + 10V_2 = 60$$

Eq 6.18

$$V_1 = -30 \text{ V}, V_2 = -12 \text{ V}, I_1 = -2 \text{ A}$$



# Basic Circuits

## Nodal Analysis: Example 6.5: Voltage super node.

Given the following circuit. Solve for the indicated nodal voltages.


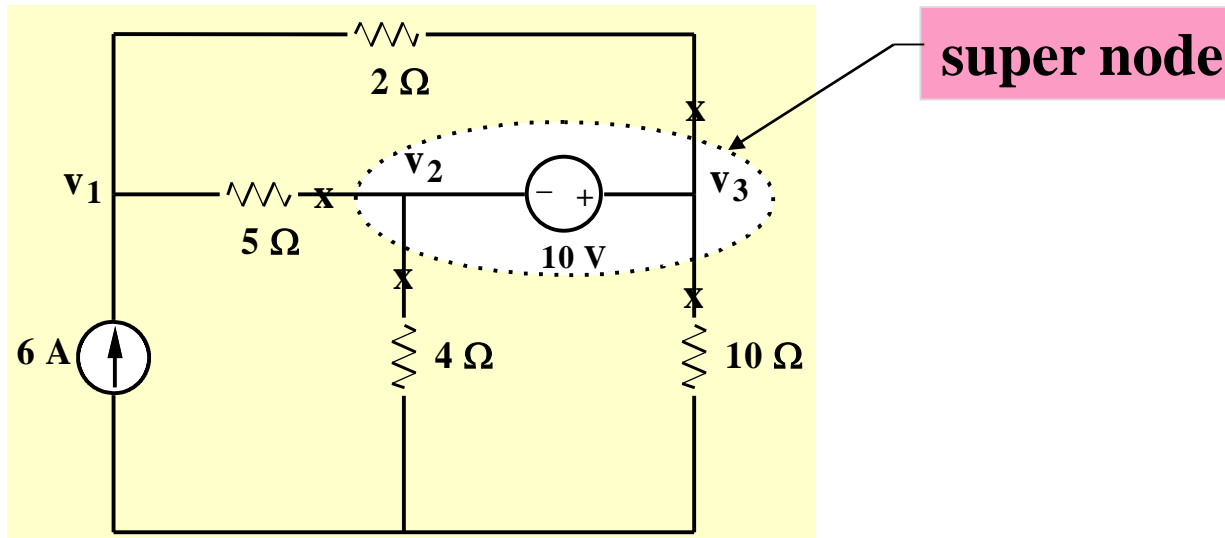


Figure 6.6: Circuit for Example 6.5.

When a voltage source appears between two nodes, an easy way to handle this is to form a super node. The super node encircles the voltage source and the tips of the branches connected to the nodes.

# Basic Circuits
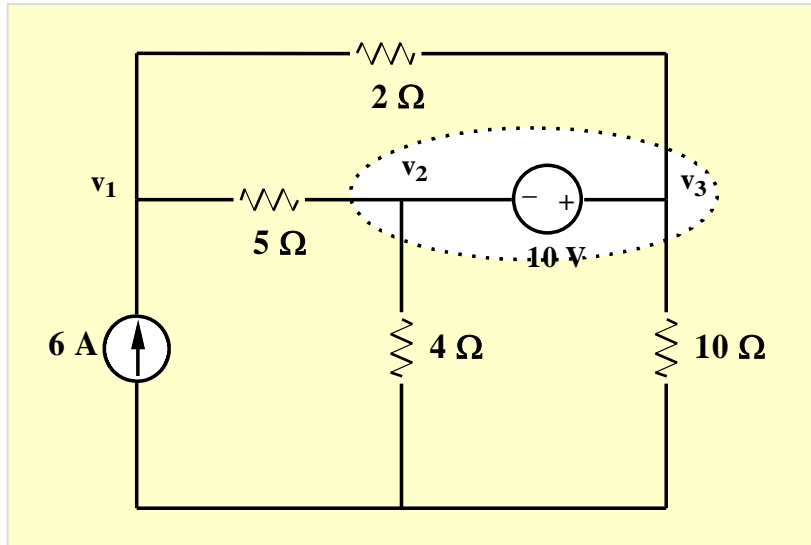
## Nodal Analysis: Example 6.5: Continued.



Constraint Equation

$$V_2 - V_3 = -10 \quad \text{Eq 6.19}$$

At  $V_1$

$$\frac{V_1 - V_2}{5} + \frac{V_1 - V_3}{2} = 6$$

Eq 6.20

At super  
node

$$\frac{V_2 - V_1}{5} + \frac{V_2}{4} + \frac{V_3}{10} + \frac{V_3 - V_1}{2} = 0$$

Eq 6.21

# Basic Circuits

## Nodal Analysis: Example 6.5: Continued.

Clearing Eq 6.19, 6.20, and 6.21:

$$7V_1 - 2V_2 - 5V_3 = 60$$

Eq 6.22

$$-14V_1 + 9V_2 + 12V_3 = 0$$

Eq 6.23

$$V_2 - V_3 = -10$$

Eq 6.24


Solving gives:

$$V_1 = 30 \text{ V}, \quad V_2 = 14.29 \text{ V}, \quad V_3 = 24.29 \text{ V}$$

# Basic Circuits

## Nodal Analysis: Example 6.6: With Dependent Sources.

Consider the circuit below. We desire to solve for the node voltages

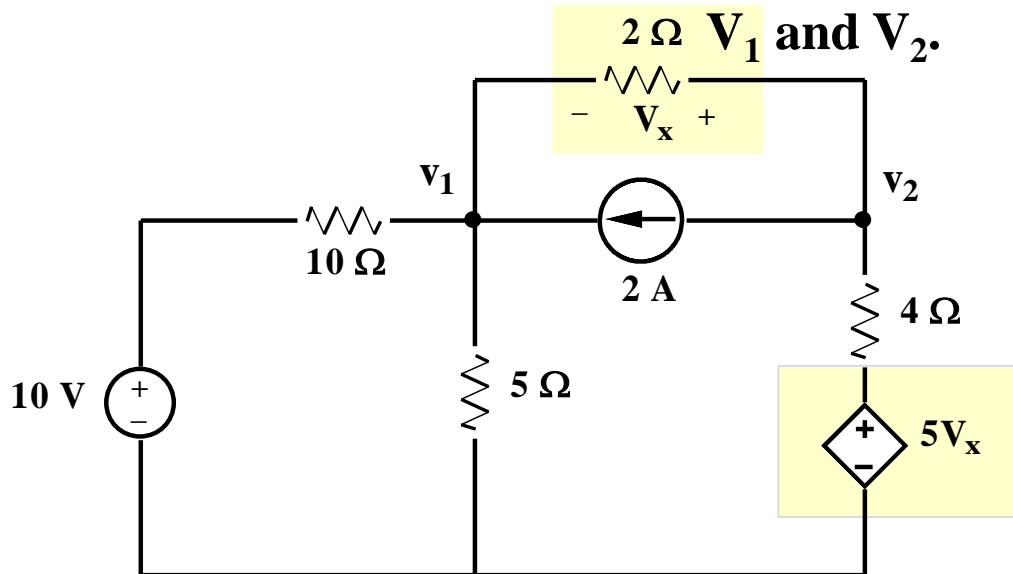

**Figure 6.7: Circuit for Example 6.6.**


In this case we have a dependent source,  $5V_x$ , that must be reckoned with. Actually, there is a constraint equation of

$$V_2 - V_x - V_1 = 0$$

Eq 6.25

# Basic Circuits
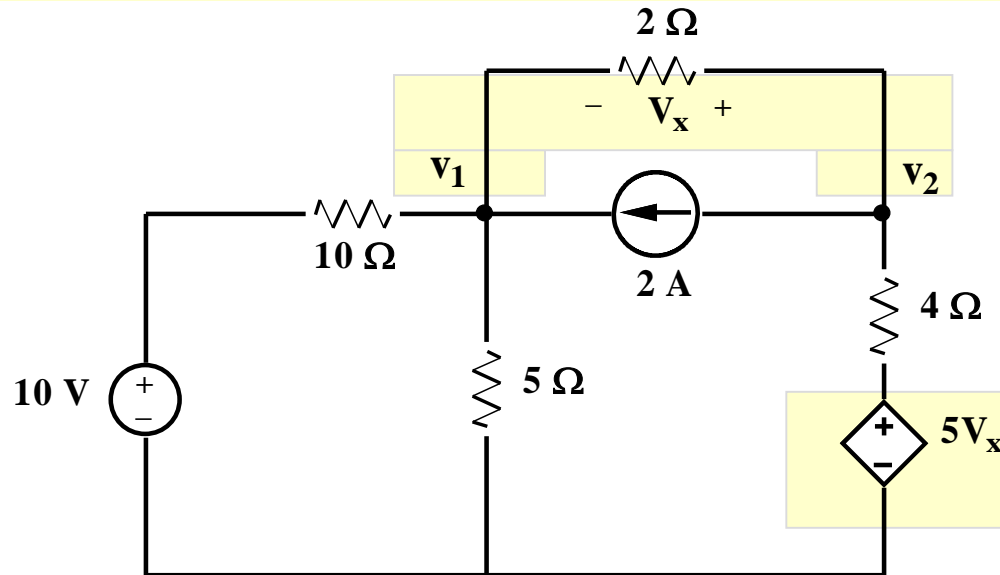
## Nodal Analysis: Example 6.6: With Dependent Sources.



At node  $V_1$  
$$\frac{V_1 - 10}{10} + \frac{V_1}{5} + \frac{V_1 - V_2}{2} = 2$$

At node  $V_2$  
$$\frac{V_2 - V_1}{2} + \frac{V_2 - 5V_x}{4} = -2$$

The constraint equation: 
$$V_x = V_1 - V_2$$

# **Basic Circuits**

## **Nodal Analysis: Example 6.6: With Dependent Sources.**

Clearing the previous equations and substituting the constraint  $V_X = V_1 - V_2$  gives,

$$8V_1 - 5V_2 = 30 \quad \text{Eq 6.26}$$


$$-7V_1 + 8V_2 = -8 \quad \text{Eq 6.27}$$

which yields,


$$V_1 = 6.9V, \quad V_2 = 5.03V$$

# NODAL ANALYSIS (GENERAL APPROACH)

## Supernode

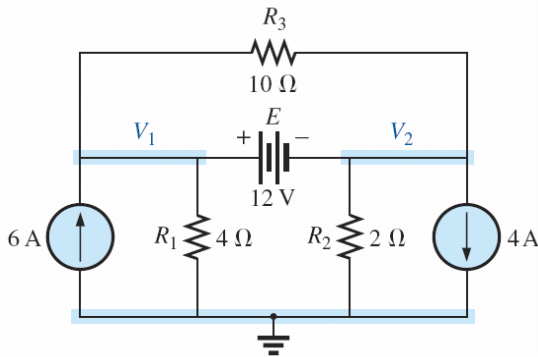

**FIG. 8.53** Example 8.22.

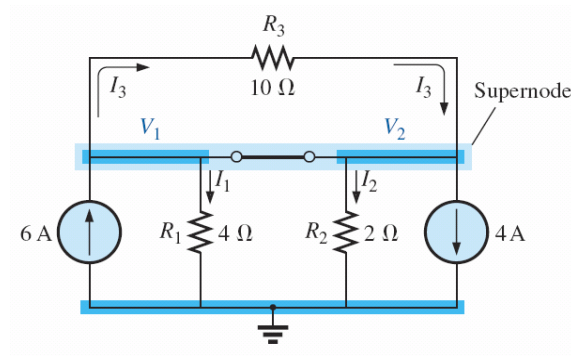

**FIG. 8.54** Defining the supernode for the network in Fig. 8.53.