


Bridge Rectifier

Electronic Devices and Circuit Theory
Boylestad

© 2013 by Pearson Higher Education, Inc
Upper Saddle River, New Jersey 07458 • All Rights Reserved

Full wave rectifier

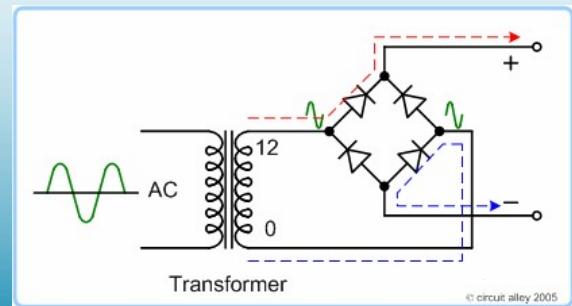Suitable for applications where large powers are required




Electronic Devices and Circuit Theory
Boylestad

© 2013 by Pearson Higher Education, Inc
Upper Saddle River, New Jersey 07458 • All Rights Reserved


The Bridge Full-wave rectifiers

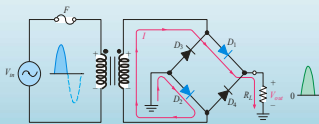- ❖ The Bridge Full-Wave rectifier uses four diodes connected across the entire secondary as shown.



Conduction path for the positive half-cycle.

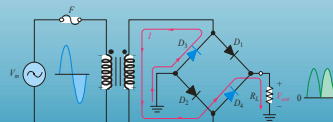
Conduction path for the negative half-cycle.



Electronic Devices and Circuit Theory
Boylestad

© 2013 by Pearson Higher Education, Inc
Upper Saddle River, New Jersey 07458 • All Rights Reserved


Full-Wave Bridge Rectification

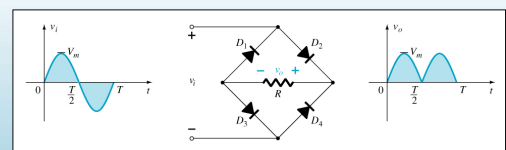

Bridge Rectifier

A full-wave rectifier with four diodes that are connected in a bridge configuration

$$V_{DC} = 0.636V_m$$

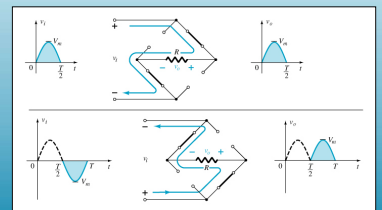

Electronic Devices and Circuit Theory
Boylestad

© 2013 by Pearson Higher Education, Inc
Upper Saddle River, New Jersey 07458 • All Rights Reserved

Summary of Rectifier Circuits

In the center tapped transformer rectifier circuit, the peak AC voltage is the transformer secondary voltage to the tap.

Rectifier	Ideal V_{DC}	Realistic V_{DC}
Half Wave Rectifier	$V_{DC} = 0.318V_m$	$V_{DC} = 0.318V_m - 0.7$
Bridge Rectifier	$V_{DC} = 0.636V_m$	$V_{DC} = 0.636V_m - 2(0.7 \text{ V})$
Center-Tapped Transformer Rectifier	$V_{DC} = 0.636V_m$	$V_{DC} = 0.636V_m - 0.7 \text{ V}$

V_m = the peak AC voltage

The Bridge Full-Wave Rectifier

Example:

Determine the peak output voltage and current in the $3.3 \text{ k}\Omega$ load resistor if $V_{sec} = 24 \text{ V}_{rms}$. Use the practical diode model.

Solution:


The peak output voltage is:

$$V_{p(sec)} = 1.41V_{rms} = 33.9 \text{ V}$$

$$V_{p(out)} = V_{p(sec)} - 1.4 \text{ V} \\ = 32.5 \text{ V}$$

Applying Ohm's law,

$$I_{p(out)} = 9.8 \text{ mA}$$

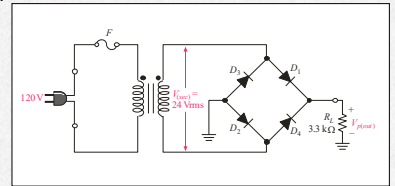

Power Supply Filters

Objective:


- Explain & Analyze the operation & characteristic of power supply filters & Regulators
- Explain the purpose of a filter
- Describe the capacitor-input filter
- Define ripple voltage & calculate the ripple voltage
- Discuss surge current in capacitor-input filter
- Discuss voltage regulation & integrated circuit regulator

Power Supply Filters

- To reduce the fluctuations in the output voltage of half / full-wave rectifier – **produces constant-level dc voltage.**
- It is necessary – electronic circuits require a constant source to provide power & biasing for proper operation.
- Filters are implemented with *capacitors*.

Power Supply Filters

- In most power supply – 60 Hz ac power line voltage is converted to constant dc voltage.
- 60Hz pulsating dc output must be filtered to reduce the large voltage variation.
- Small amount of fluctuation in the filter o/p voltage - ripple

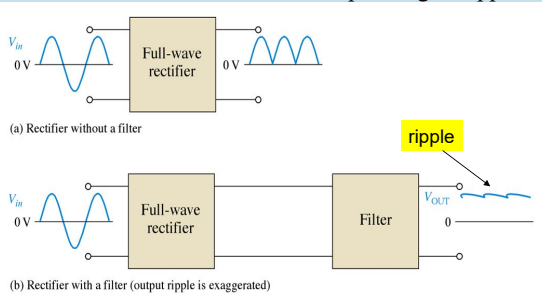Electronic D
BoylestadEducation, Inc
Rights Reserved


Power Supply Filters

Capacitive Filter

Capacitive filter is simply a **capacitor** connected in **parallel** with the **load** R_L . During the **positive first quarter-cycle** of the input, the diode is forward-biased, allowing the capacitor **charges rapidly**.

When the input begins to go **negative**, the diode is reverse-biased, and the capacitor **slowly discharges** through the load resistance. As the output from the rectifier drops below the charged voltage of the capacitor, the capacitor acts as the **voltage source** for the load.

During first **quarter** of the next cycle, as illustrated in part (c), the diode will again become forward-biased when the input voltage exceeds the capacitor voltage.

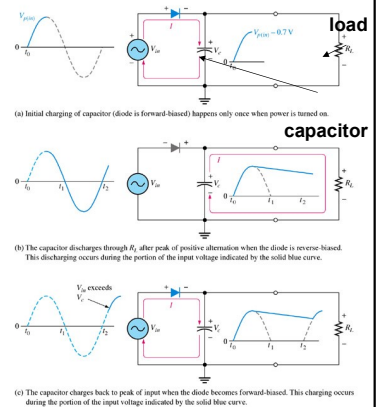© 2013 by Pearson Higher Education, Inc
Upper Saddle River, New Jersey 07458 • All Rights Reserved

Ripple

Ripple voltage is the **fluctuation** in the **capacitor voltage** due to the difference between the charge and discharge times. The difference between the charge and discharge times is caused by two distinct **RC time constant** in the circuit. One time constant is found as:

$$\tau = RC$$


where R and C are the total circuit resistance and capacitance, respectively.

Since it takes **five** time constants for a capacitor to charge or discharge fully, this time period (T) can be found as:


$$T = 5RC = 5\tau$$

Electronic Devices and Circuit Theory
Boylestad© 2013 by Pearson Higher Education, Inc
Upper Saddle River, New Jersey 07458 • All Rights Reserved

Power Supply Filters

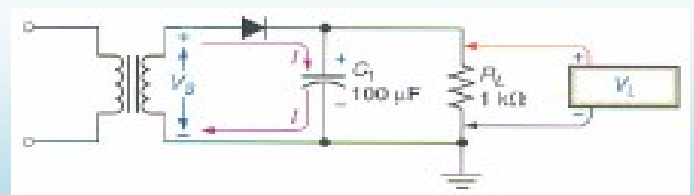

(a) Charge circuit

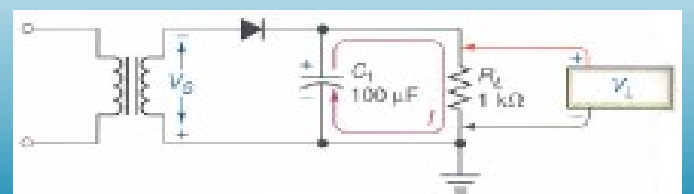


(b) Discharge circuit

Electronic Devices and Circuit Theory
Boylestad© 2013 by Pearson Higher Education, Inc
Upper Saddle River, New Jersey 07458 • All Rights Reserved

Ripple Voltage: the variation in capacitor voltage due to the charging and discharging times.

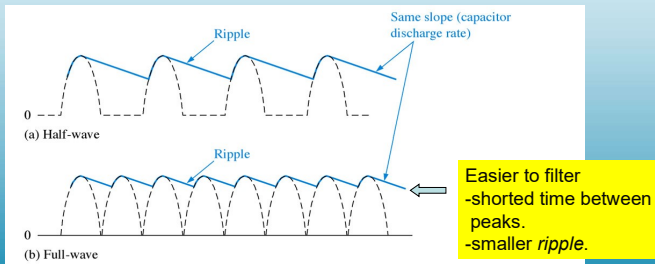The advantage of a full-wave rectifier over a half-wave is quite clear. The capacitor can more effectively reduce the *ripple* when the time between peaks is *shorter*.




Power Supply Filters

Ripple factor: indication of the effectiveness of the filter

$$r = \frac{V_{r(pp)}}{V_{DC}} \quad [\text{half-wave rectifier}]$$

$V_{r(pp)}$ = peak to peak ripple voltage; $V_{DC} = V_{AVG}$ = average value of filter's output voltage.

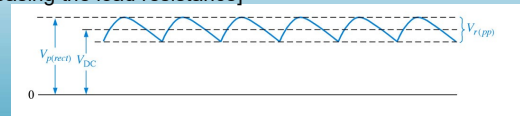- Lower ripple factor \rightarrow better filter
[can be lowered by increasing the value of filter capacitor or increasing the load resistance]



- For the full-wave rectifier:

$$V_{r(pp)} \cong \left(\frac{1}{fR_L C} \right) V_{p(rect)}$$

$V_{p(rect)}$ = unfiltered peak.

$$V_{DC} = V_{AVG} = \left(1 - \frac{1}{2fR_L C} \right) V_{p(rect)}$$