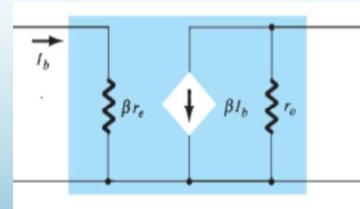


## Small Signal Model & Analysis.....

### Example



Given  $\beta = 120$  and  $I_E = 3.2$  mA for a common-emitter configuration with  $r_o = \infty \Omega$ , determine:

- (a)  $Z_i$ .  
 (b)  $A_v$  if a load of  $2 \text{ k}\Omega$  is applied.  
 (c)  $A_i$  with the  $2 \text{ k}\Omega$  load.


$$Z_i = \beta r_e \quad r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{3.2 \text{ mA}} = 8.125 \Omega$$

$$A_v = -\frac{R_L}{r_e}$$

$$A_i = \frac{I_o}{I_i} = \beta = 120$$

## Hybrid Equivalent Model
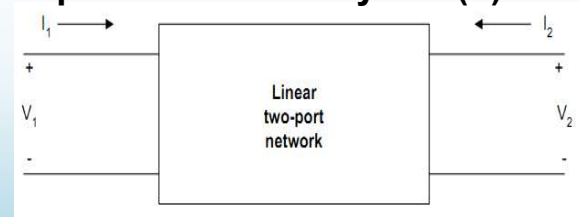
### Two-port Network & Hybrid (h) Parameter



A two-port network can be represented using the h-parameters.

$I_1$  and  $V_2$  are independent variables and  
 $V_1$  and  $I_2$  are dependent variables.

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

The h-parameters can be found as follows:

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$


$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

The term hybrid was chosen because the mixture of variables (V and I) in each equation results in a "hybrid" set of units

## h-parameter for BJT

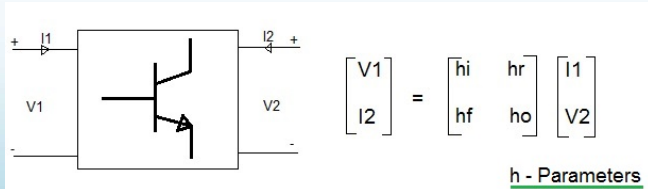

The hybrid parameters:

$$h_{11} = h_i$$


$$h_{12} = h_r$$

$$h_{21} = h_f$$

$$h_{22} = h_o$$

are developed and used to model the transistor. These parameters can be found in a specification sheet for a transistor.
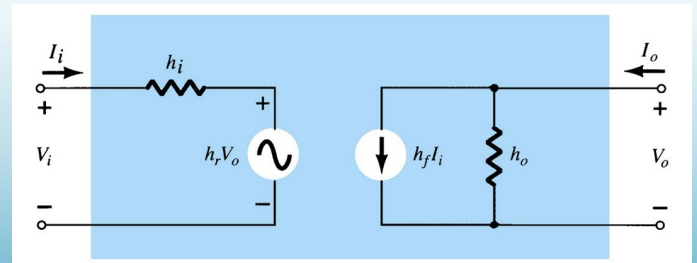
## General h-Parameters for any Transistor Configuration




$h_i$  = input resistance

$h_r$  = reverse transfer voltage ratio ( $V_i/V_o$ )

$h_f$  = forward transfer current ratio ( $I_o/I_i$ )

$h_o$  = output conductance


## CE and CB hybrid model

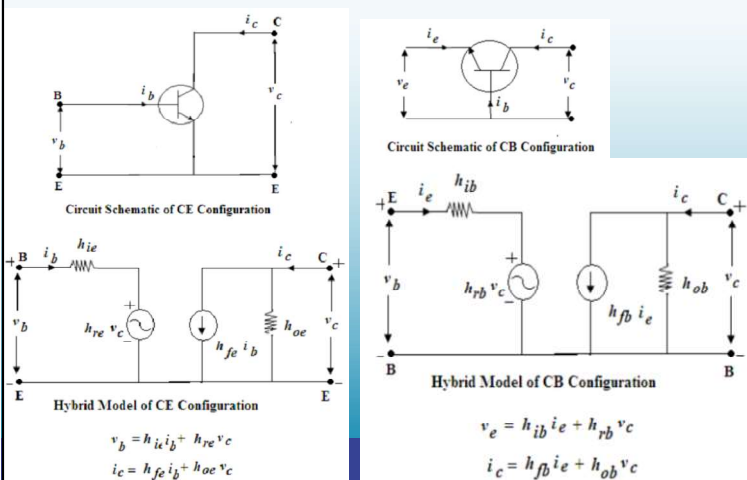

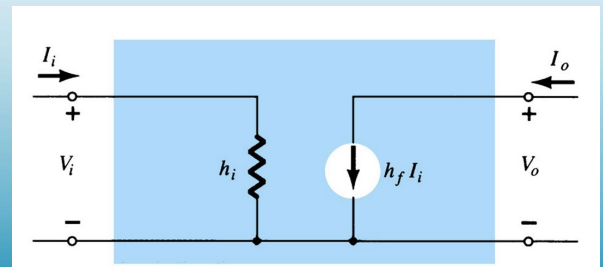
## Simplified General h-Parameter Model

The above model can be simplified based on these approximations:

$h_r \approx 0$  therefore  $h_r V_o = 0$  and  $h_o \approx \infty$


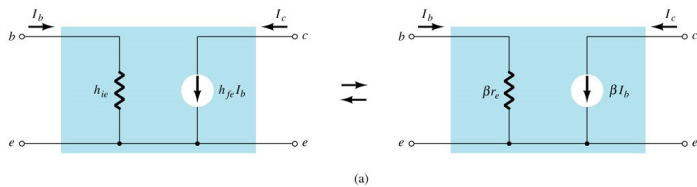
### Common-Emitter $r_e$ vs. $h$ -Parameter Model




$$\begin{aligned} h_{ie} &= \beta r_e \\ h_{fe} &= \beta \\ h_{oe} &= 1/r_o \end{aligned}$$

### Common-Emitter $h$ -Parameters

$$h_{ie} = \beta r_e \quad [\text{Formula 7.28}]$$

$$h_{fe} = \beta_{ac} \quad [\text{Formula 7.29}]$$
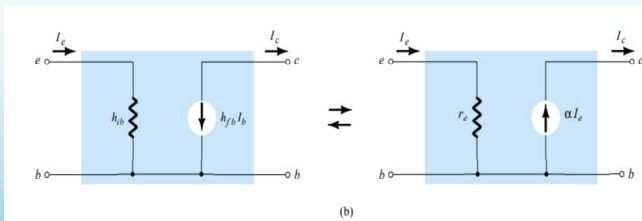
### Common-Base $r_e$ vs. $h$ -Parameter Model



$$\begin{aligned} h_{ib} &= r_e \\ h_{fb} &= -\alpha \end{aligned}$$

### Common-Base $h$ -Parameters


$$h_{ib} = r_e \quad [\text{Formula 7.30}]$$

$$h_{fb} = -\alpha \cong -1 \quad [\text{Formula 7.31}]$$
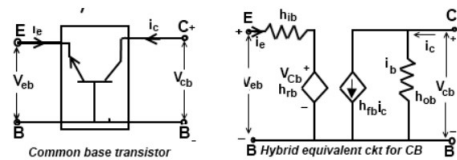
## Assignment

$$V_{be} = h_{ib} \cdot i_b + h_{rb} \cdot V_c$$

$$i_e = h_{fb} \cdot i_b + h_{ob} \cdot V_c$$



## Example

A transistor used in a common base amplifier has the following values of h-parameters:

$$h_{ib} = 28 \Omega, h_{fb} = -0.98, h_{rb} = 5 \times 10^{-4} \text{ and } h_{ob} = 0.34 \times 10^{-6} \text{ S}$$

Calculate the values of input resistance, output resistance, current gain and voltage gain, if the load resistance is  $1.2 \text{ k}\Omega$ . Assume source resistance as zero.

## Example: CE hybrid equivalent ckt

Given  $I_E = 2.5 \text{ mA}$ ,  $h_{fe} = 140$ ,  $h_{oe} = 20 \mu\text{S}$  ( $\mu\text{mho}$ ), and  $h_{ob} = 0.5 \mu\text{S}$ , determine:


- The common-emitter hybrid equivalent circuit.
- The common-base  $r_e$  model.

### Solution

$$(a) r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{2.5 \text{ mA}} = 10.4 \Omega$$

$$h_{ie} = \beta r_e = (140)(10.4 \Omega) = 1.456 \text{ k}\Omega$$
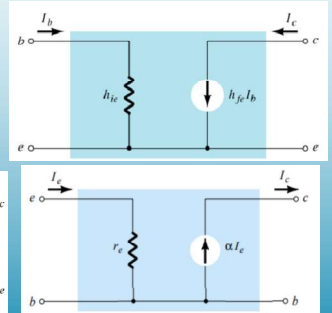
$$r_o = \frac{1}{h_{oe}} = \frac{1}{20 \mu\text{S}} = 50 \text{ k}\Omega$$



## Example: Common-Base $r_e$ model

$$(b) r_e = 10.4 \Omega$$

$$\alpha \cong 1, \quad r_o = \frac{1}{h_{ob}} = \frac{1}{0.5 \mu\text{S}} = 2 \text{ M}\Omega$$

