

## Single Stage BJT Amplifier

## AMPLIFIER GAIN

- Amplifier
  - Ratio of output signal to input signal
    - Ratio < 1: attenuator
    - Ratio = 1: buffer
    - Ratio > 1: amplifier
- 3 types of gains associated with an amplifier
  - Voltage gain
  - Current gain
  - Power gain

## VOLTAGE GAIN

- ⑩ Defined as the ratio of ac output voltage to ac input voltage

Or, the mathematical expression:

$$A_V = \frac{V_{Out}}{V_{In}}$$

## CURRENT GAIN

- ⑩ Defined as the ratio of ac output current to ac input current

Mathematically, expressed as:

$$A_I = \frac{I_{Out}}{I_{In}}$$

## AMPLIFIER IMPEDANCE

□ When a signal (current or voltage) is fed into the input, a portion of it will not get through the amplifier. This is due to external resistance effects.

□ 2 types of impedances associated with an amplifier:

- Input impedance
- Output impedance

## BJT Transistor Modeling

A model is an equivalent circuit that represents the AC characteristics of the transistor.

A model uses circuit elements that approximate the behavior of the transistor.


There are two models commonly used in small signal AC analysis of a transistor:

**$r_e$  model**

**Hybrid equivalent model**
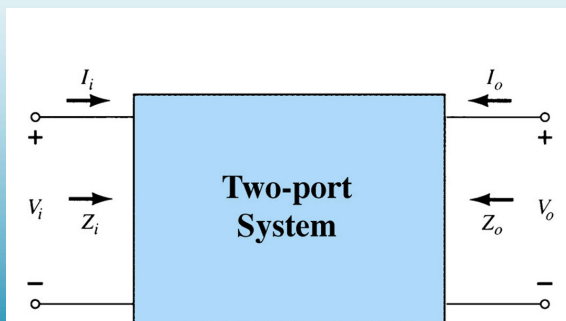
## Important Parameter

$Z_i$ ,  $Z_o$ ,  $A_v$ ,  $A_i$  are important parameters for the analysis of the AC characteristics of a transistor circuit.




## Input Impedance, $Z_i$

To determine  $I_i$ : insert a “sensing resistor”

[Formula 7.1]

$$Z_i = \frac{V_i}{I_i}$$

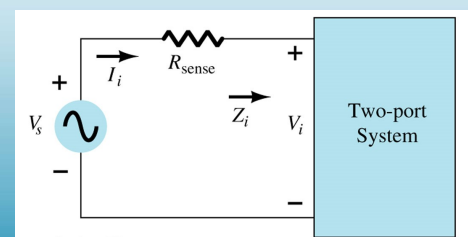


then calculate  $I_i$ :  
[Formula 7.2] 
$$I_i = \frac{V_s - V_i}{R_{sense}}$$

Copyright © 2002 by Pearson Education, Inc.  
Upper Saddle River, New Jersey 07083  
All Rights Reserved.
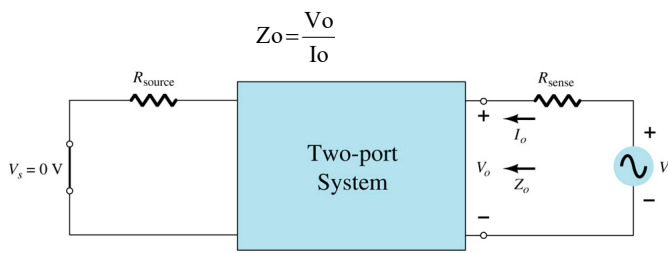
## Output Impedance, $Z_o$

[Formula 7.5]

To determine  $I_o$ : insert a "sensing resistor"



then calculate  $I_o$ :

[Formula 7.4] 
$$I_o = \frac{V - V_o}{R_{sense}}$$


## Voltage Gain, $A_v$

[Formula 7.6]

For an amplifier with no load:

$$A_v = \frac{V_o}{V_i}$$

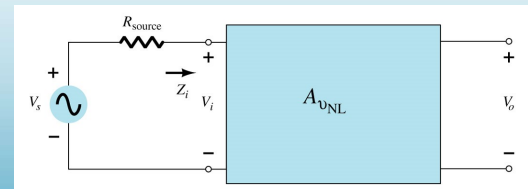
$$A_{vNL} = \frac{V_o}{V_i} \bigg/ R_L = \infty \Omega (\text{opencircuit})$$



**Note:** the no-load voltage gain ( $A_{vNL}$ ) is always greater than the loaded voltage gain ( $A_v$ ).

## Current Gain, $A_i$

$$A_i = \frac{I_o}{I_i}$$

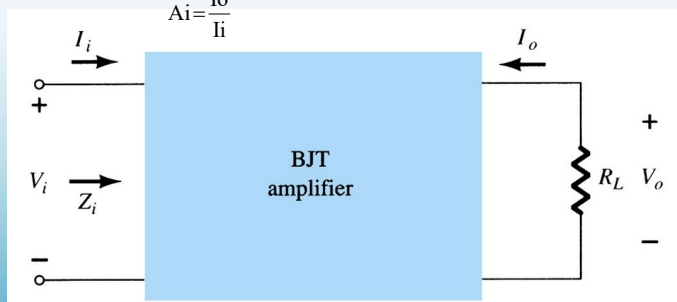

$$A_i = -A_v \frac{Z_i}{R_L}$$

## Phase Relationship

The phase relationship between input and output depends on the amplifier configuration circuit.

Common – Emitter ~ 180 degrees

Common - Base ~ 0 degrees

Common – Collector ~ 0 degrees

### The $r_e$ Transistor Model

BJTs are basically current-controlled devices; therefore the  $r_e$  model uses a diode and a current source to duplicate the behavior of the transistor.

One disadvantage to this model is its sensitivity to the DC level. This model is designed for specific circuit conditions.

### The $r_e$ Model

Small  $r_e$  is the resistance looking into the emitter terminal of a transistor. As there is a voltage on the base of a transistor and a current flowing in the emitter, then from ohm's law

$$r_e = v/i$$


$$= v_{BE}/I_E$$

$$r_e = \frac{KT}{qI_E}$$

$K$  is Boltzman's constant  $1.38 \times 10^{-23}$  joule/K

$$r_e = \frac{25}{I_E} \quad @ 20^\circ \text{C}$$
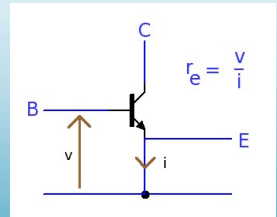
$$r_e = \frac{26}{I_E} \quad @ 25^\circ \text{C}$$




### Equivalent Circuit of BJT

We know,


$$i_c = \beta_{ac} i_b$$

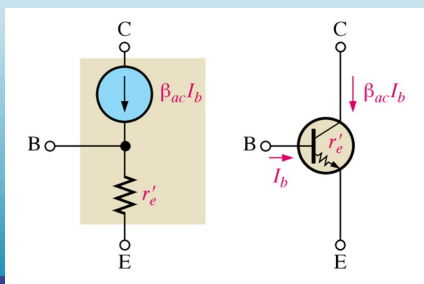Thus  $\beta_{ac} i_b$  can be thought of as a **constant current generator**. The equivalent circuit is shown below:



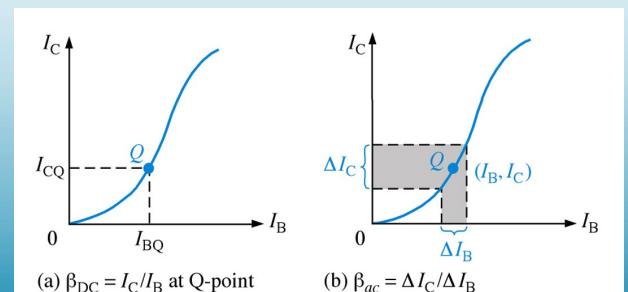
### Transistor Equivalent Circuits


The two graphs best illustrate the difference between  $\beta_{DC}$  and  $\beta_{ac}$ . The two only differ slightly.



## Linear analog amplifier

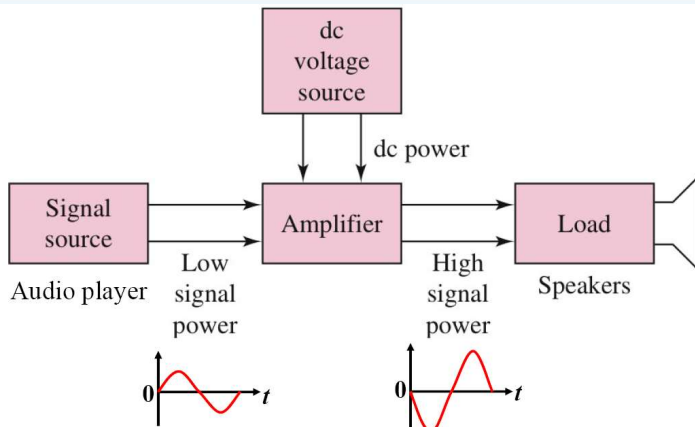

## Basic characteristics of an amplifier

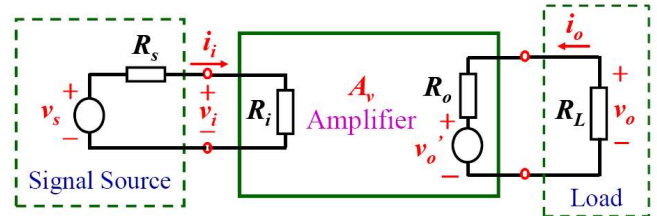

- **Amplifier Gain:**  $A_v = \frac{v_o}{v_s}$
- **Input Resistance:**  $R_i = \frac{v_i}{i_i}$
- **Output Resistance:**  $R_o = \frac{v_o}{i_o} \bigg|_{v_s=0 \text{ (a short circuit)}, R_L = \infty \text{ (an open circuit)}}$