

## Experiment No. 05


**Name of the Exp:** Verification of Norton's theorem.

**Objective:** To verify Norton's theorem with reference to a given circuit theoretically as well as experimentally.

### **Theory:**

The Norton's theorem states that any two terminal linear bilateral network containing sources and passive elements can be replaced by an equivalent circuit consisting of a current source  $I_N$  in parallel with a resistor  $R_N$  where

- $I_N$  = The short circuit current (ISC) at the two terminals A & B.
- $R_N$  = The resistance looking into the terminals A and B of the network with all sources removed.

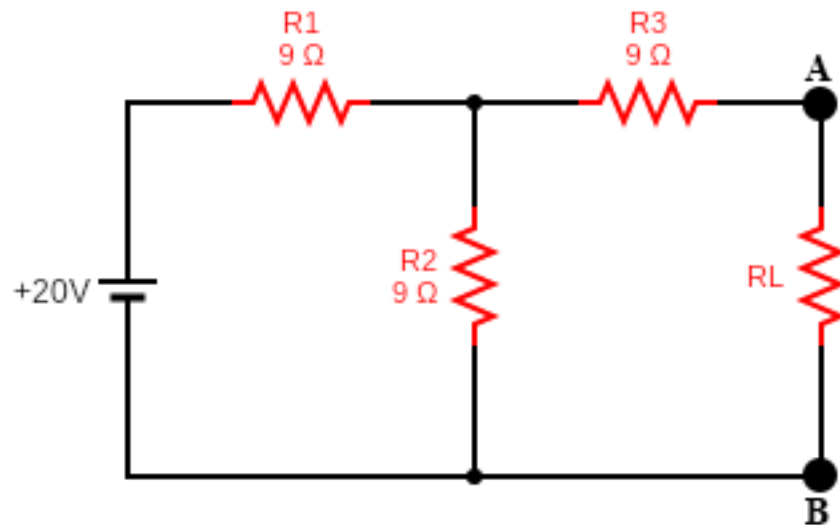

*Fig-1. Circuit diagram for Norton's theorem.*

### **Apparatus:**

1. DC power supplies
2. Resistors
3. Multi meter
4. Bread board
5. Connecting wires


### Procedure:

1. Check the values of the resistor using multi-meter (ohm section of multi-meter). Record the values in Table -1.
2. Give the connection as per the circuit diagram shown in Fig.1.


### Finding $I_N$ & $R_N$ :

1. Short the load resistance  $R_L$  and find the short circuit current between terminals A & B. This current is Norton current i.e.,  $I_N = I_{SC}$ .
2. Replace the voltage sources with short circuits and current sources with open circuit. With  $R_L$  removed from the circuit, measure  $R_N$  using a multimeter (Ammeter).
3. Record the results in Table 2.


### Circuit Diagram:

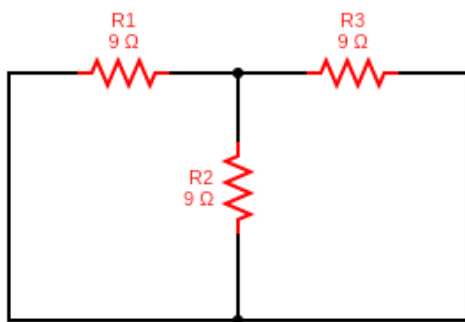


*Fig-2. For measuring  $R_N$*

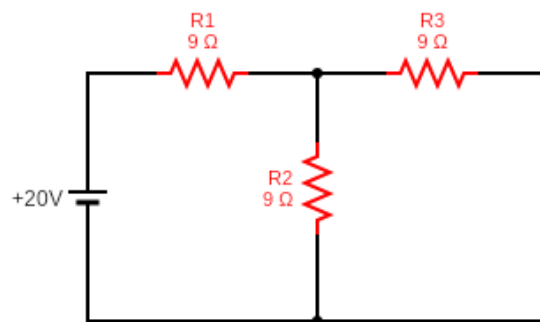

*Fig-3. For measuring  $I_N$*

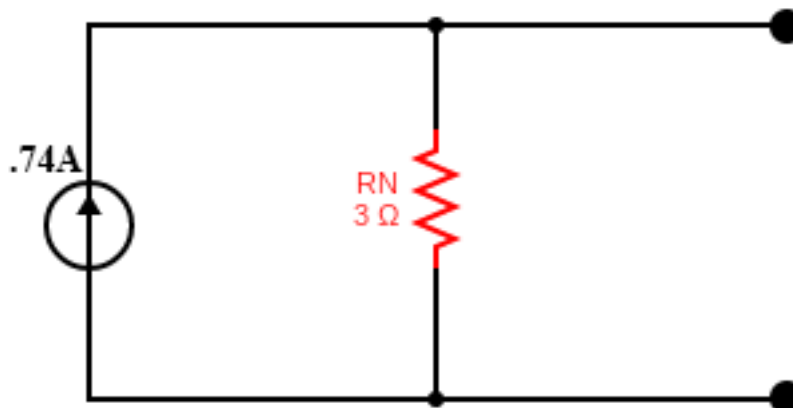

*Fig-4. Norton's equivalence circuit*

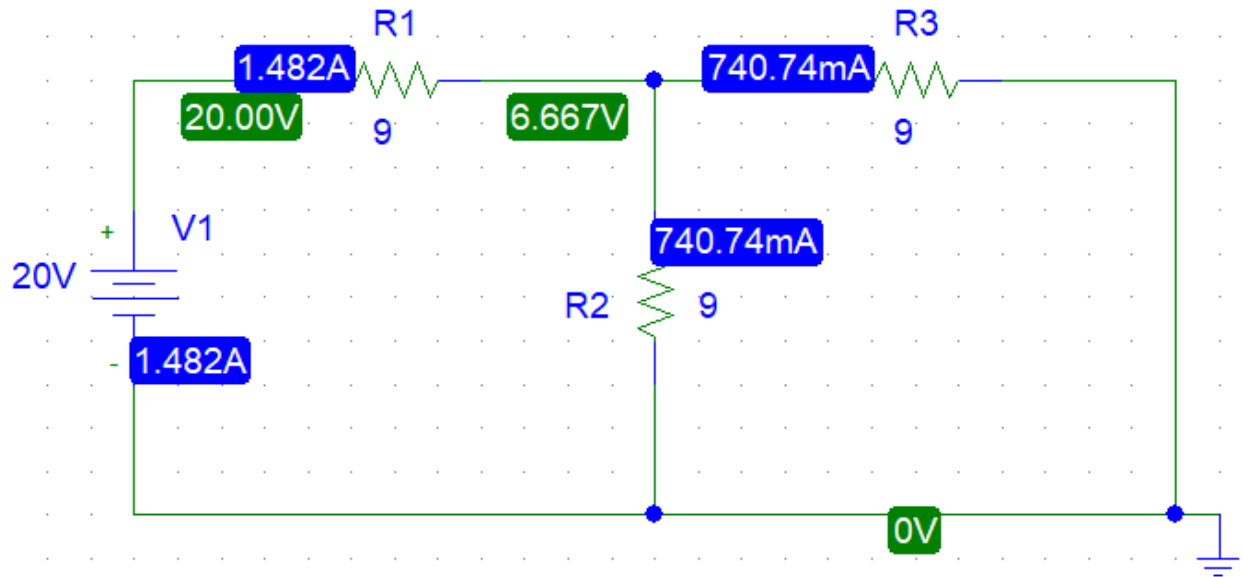

*Fig-5. practical value of measuring  $I_N$*

**Model calculation:**

First, we are going to determine the value of  $R_N$  from fig-2

$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9} = 3\Omega$$

So,  $R_N = 3\Omega$

Now we are going to measure the value of  $I_N$  from fig-3

Just because the  $R_3$  resistance is in series with the point A & B terminal so the current through  $R_3$  is going to be equal to  $I_N$ .

$$\frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{9} + \frac{1}{9} = 4.5\Omega$$

$$R_{(2+3)} + R_1 = 13.5\Omega$$

$$I = \frac{V}{R} = \frac{20}{13.5} = 1.481A$$

Using current divider rule we get,

$$I_N = \frac{I \times R_2}{R_2 + R_3} = \frac{1.481 \times 9}{9 + 9} = .74A$$

**Observation:****Table-1. Resistor value**

Resistors( $\Omega$ )	$R_1$	$R_2$	$R_3$
Ohm meter reading	9	9	9

**Table-2. Result for theoretical & measured value**

No. of Observation	$V_s$ (V)	$R_N$ ( $\Omega$ )		$I_N$ (A)	
		TV	MV	TV	MV
	20	3	3	0.74	0.74

**Result:**

The theoretical & measured values of the circuit are same so it's safe to say that our measurements are correct.

**Precautions:**

1. Check for proper connections before switching ON the supply.
2. Take care of the reading of the apparatus.
3. The terminal of the resistance should be properly connected.