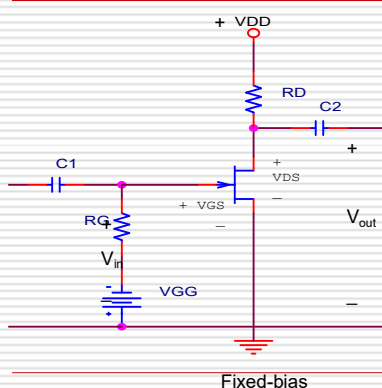


Field Effect Transistor

DC JFET Biasing

- Just as we learned that the BJT must be biased for proper operation, the JFET also must be biased for operation point (I_D , V_{GS} , V_{DS})
- In most cases the ideal Q-point will be at the **middle** of the transfer characteristic curve, which is **about half of the I_{DSS}** .
- 3 types of DC JFET biasing configurations :
 - Fixed-bias
 - Self-bias
 - Voltage-Divider Bias

Fixed-bias




- Use two voltage sources: V_{GG} , V_{DD}
- V_{GG} is reverse-biased at the Gate – Source (G-S) terminal,
- what's the value of I_G , V_{RG} and V_{GS} ?

no current flows through R_G ($I_G = 0$),
 $V_{RG} = 0$ & $V_{GS} = V_{GG}$.

Fixed-bias..

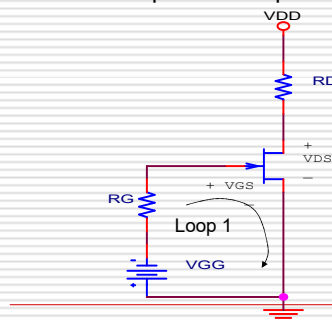- DC analysis
 - All capacitors replaced with open-circuit



Fixed-bias...

1. Input Loop

□ By using KVL at loop 1:

$$V_{GG} + V_{GS} = 0$$

$$V_{GS} = -V_{GG}$$

- For graphical solution, use $V_{GS} = -V_{GG}$ to draw the load line
- For mathematical solution, replace $V_{GS} = -V_{GG}$ in Shockley's Eq., therefore:

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = I_{DSS} \left(1 + \frac{V_{GG}}{V_{GS(off)}} \right)^2$$


2. Output loop

$$-V_{DD} + I_D R_D + V_{DS} = 0$$

$$V_{DS} = V_{DD} - I_D R_D$$

3. Then, plot transfer characteristic curve by using Shockley's Equation

Example : Fixed-bias

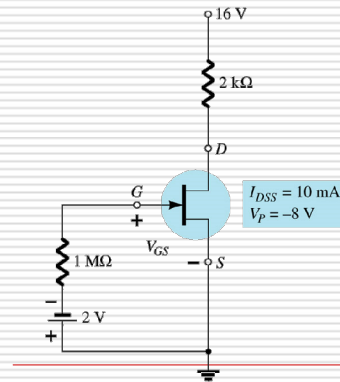


Determine the following network:

1. V_{GSQ}
2. I_{DQ}
3. V_D
4. V_G
5. V_S

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

Mathematical Solutions

$$V_{GSQ} = -V_{GG} = -2$$

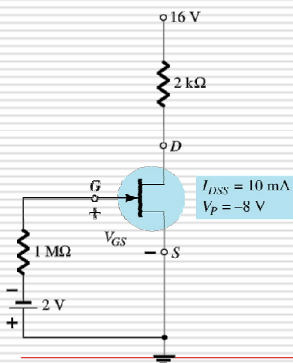

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 10 \text{ mA} \left(1 - \frac{-2}{-8} \right)^2$$

$$= 10 \text{ mA} (0.75)^2 = 5.625 \text{ mA}$$

$$V_{DS} = V_{DD} - I_{DQ} R_D = 16 - (5.625 \text{ mA})(2 \text{ k}\Omega)$$


$$= 16 \text{ V} - 11.25 \text{ V} = 4.75 \text{ V}$$

$$V_D = V_{DS} = 4.75 \text{ V}$$

$$V_G = V_{GS} = -2 \text{ V}$$

$$V_S = 0 \text{ V}$$

Graphical solution for the network

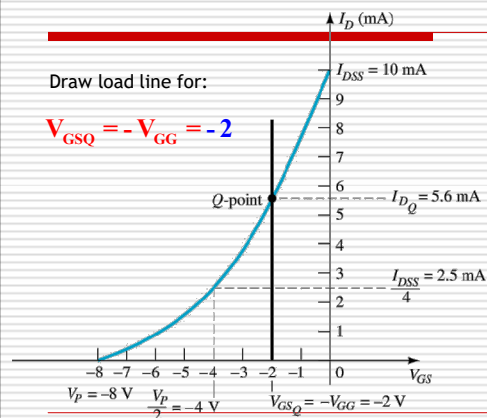

Draw load line for:

$$V_{GSQ} = -V_{GG} = -2$$

$$I_{DQ} = 5.6 \text{ mA}$$

$$V_{DS} = 4.75 \text{ V}$$


$$V_D = 4.75 \text{ V}$$

$$V_G = -2 \text{ V}$$


$$V_S = 0 \text{ V}$$

Self-bias

□ Using only one voltage source

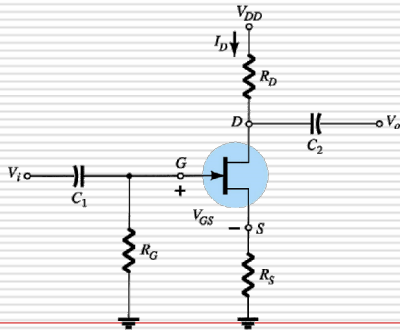

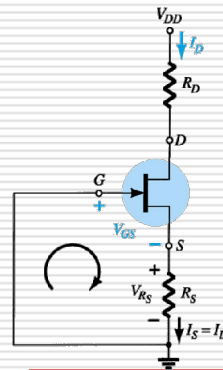DC analysis of the self-bias configuration.



Since $I_G \approx 0A$, $V_{RG} = I_G R_G$
thus $V_{RG} = 0A$,


$$V_{RS} = I_D R_S$$

$$V_{GS} + V_{RS} = 0$$

$$V_{GS} = -V_{RS} \\ = -I_D R_S$$

Q point for V_{GS}


Example : Self-bias configuration

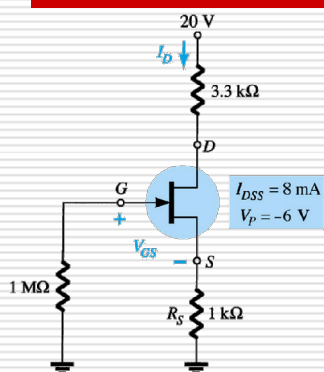

Determine the following for the network

1. V_{GSQ}
2. I_{DQ}
3. V_D
4. V_G
5. V_S

Graphical Solutions:

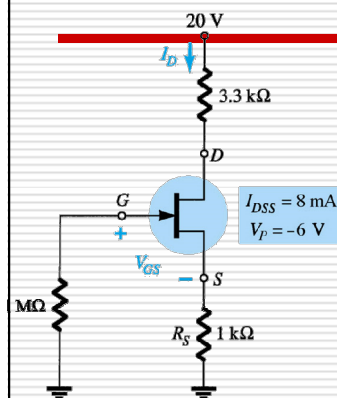

$$V_{GS} = -I_D R_S$$


When $I_D = 4mA$,

$$V_{GS} = -I_D R_S \\ = -(4mA)(1k\Omega) = -4V$$

When $I_D = 8mA$, $V_{GS} = -I_D R_S$

$$V_{GS} = -I_D R_S \\ = -8 \text{ mA } (1k\Omega) = -8V$$

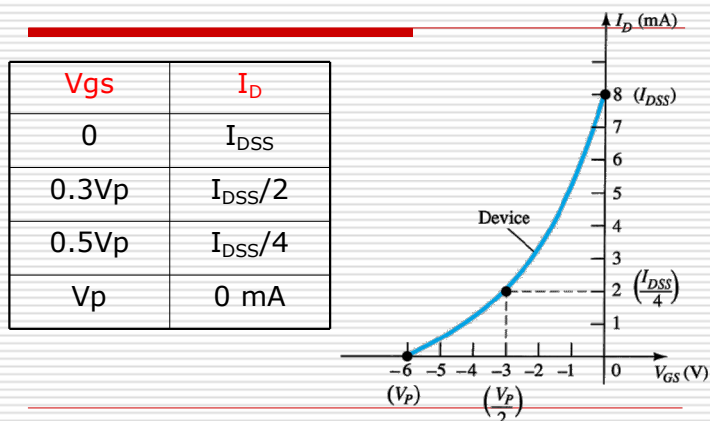Sketching the transfer characteristics curve



Mathematical Solutions

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \quad \text{recall } V_{GS} = -I_D R_S$$

$$= I_{DSS} \left(1 - \frac{(-I_D R_S)}{V_P} \right)^2$$

$$I_D = 8m \left(1 + \frac{I_D(1k)}{-6} \right)^2 = 8m \left(\frac{-6 + I_D(1k)}{-6} \right)^2$$

$$= \frac{8m}{36} (36 - 6kI_D - 6kI_D + 1M I_D^2)$$

$$36 I_D = 0.288 - 96 I_D + 8k I_D^2$$

$$8k I_D^2 - 132 I_D + 0.288 = 0$$

$$I_{D1} = 13.9mA$$

$$I_{D21} = 2.588mA$$

$$V_{GS} = -I_D R_S$$

$$V_{GS} = -I_D R_S$$

$$= -13.9mA(1k)$$

$$= -2.588mA(1k)$$

$$= -13.9V$$

$$= -2.6V$$

therefore ; choose $I_D = 2.588mA$ and $V_{GS} = -2.6V$

Solutions

$$V_{GSQ} = -2.6V$$

$$I_{DQ} = 2.6mA$$

$$I_D = I_S$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$= 20V - 2.6mA(4.3k\Omega)$$

$$= 8.82V$$


$$V_S = I_S R_S = (2.6mA)(1k\Omega)$$

$$= 2.6V$$


$$V_G = V_{GS} + V_S = 0V$$

$$V_D = V_{DS} + V_S \text{ or } V_D = V_{DD} - I_D R_D$$

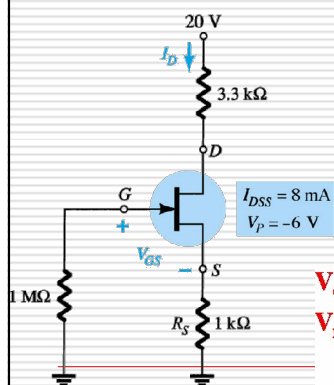
$$= V_{DS} + V_S = 8.82V + 2.6V = 11.42V$$




Voltage-divider bias

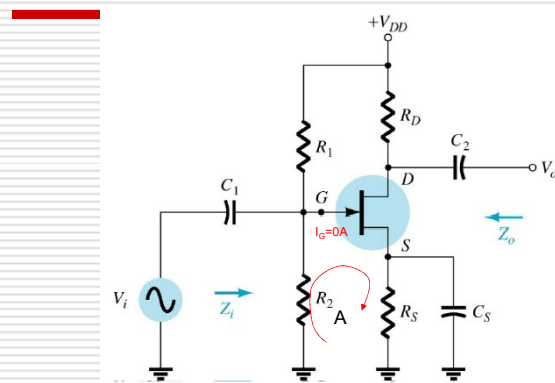


Redrawn network

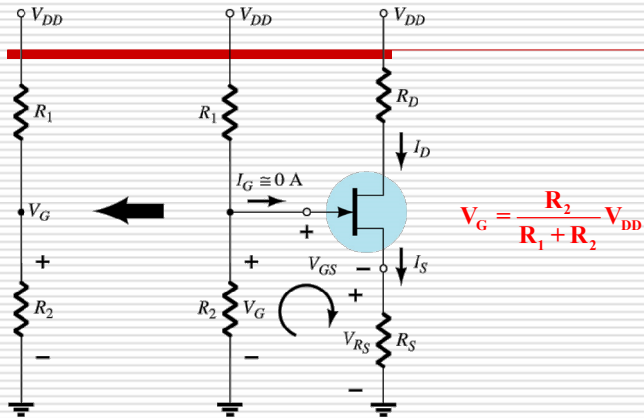

Example : Voltage-divider bias

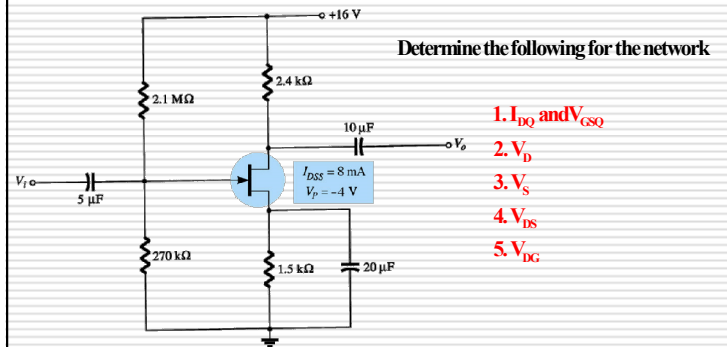

Solutions

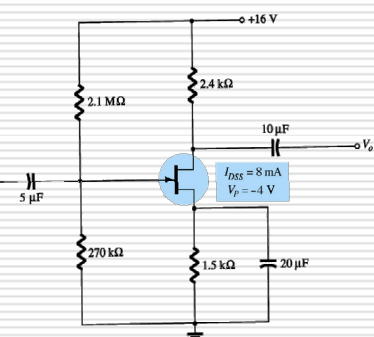

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$

$$= \frac{(270\text{k}\Omega)(16\text{V})}{2.1\text{M}\Omega + 0.27\text{M}\Omega_2} V_{DD}$$

$$= 1.82\text{V}$$

$$V_{GS} = V_G - I_D R_S$$

$$= 1.82\text{V} - I_D (1.5\text{k}\Omega)$$

$$\text{When } I_D = 0\text{mA}, V_{GS} = +1.82\text{V}$$

$$\text{When } V_{GS} = 0\text{V}, I_D = \frac{+1.82\text{V}}{1.5\text{k}\Omega} = 1.21\text{mA}$$

Determining the Q-point for the network


$$V_{GS} = 1.82\text{V} - I_D (1.5\text{k}\Omega)$$

$$V_{DS} = V_{DD} + V_{SS} - I_D (R_S + R_D)$$


$$= V_{DS} + V_S = 8.82\text{V} + 2.6\text{V} = 11.42\text{V}$$

$$I_{DQ} = 2.4\text{mA}$$

$$V_{GSQ} = -1.8\text{V}$$

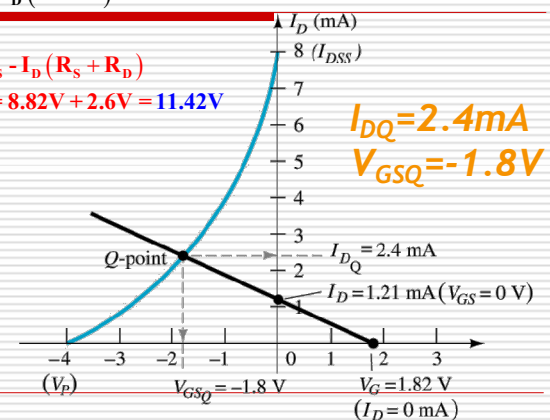

Exercise 3:

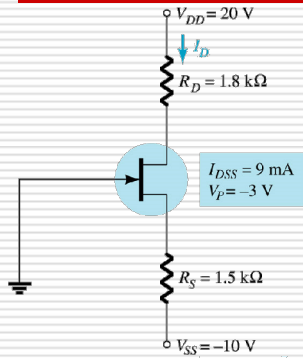

Determine the following for the network

1. I_{DQ} and V_{GSQ}
2. V_{DS}
3. V_D
4. V_S


Drawing the self bias line

$$V_{GS} + I_D R_S - 10V = 0$$

$$V_{GS} = 10V - I_D (1.5k\Omega)$$

When $I_D = 0\text{mA}$, $V_{GS} = 10V$

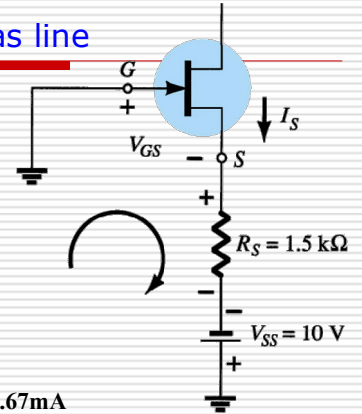
When $V_{GS} = 0V$, $I_D = \frac{10V}{1.5k\Omega} = 6.67\text{mA}$



Determining the Q-point

$$I_{DQ} = 6.9\text{mA}$$

$$V_{GSQ} = -0.35V$$

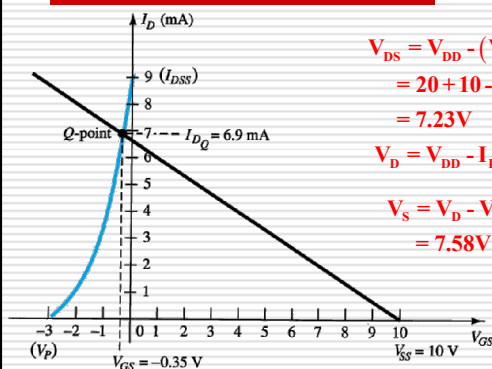

$$V_{DS} = V_{DD} - (V_{SS}) - I_D (R_S + R_D)$$

$$= 20 + 10 - (6.9\text{mA})(1.8k\Omega + 1.5k\Omega)$$


$$= 7.23V$$

$$V_D = V_{DD} - I_D (R_D) = 7.58V$$

$$V_S = V_D - V_{DS}$$


$$= 7.58V - 7.23V = 0.35V$$

Exercise 4

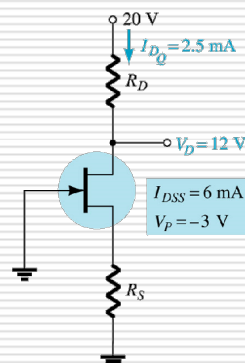

Determine the required values of R_D and R_S


Determining V_{GSQ} for the network

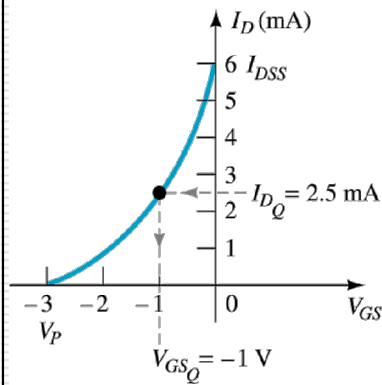

$$R_D = \frac{V_{RD}}{I_{DQ}} = \frac{V_{DD} - V_{DQ}}{I_{DQ}} = \frac{20V - 12V}{2.5mA} = 3.2k\Omega$$

$$R_S = \frac{-(V_{GSQ})}{I_{DQ}} = \frac{-(-1)}{2.5mA} = 0.4k\Omega$$

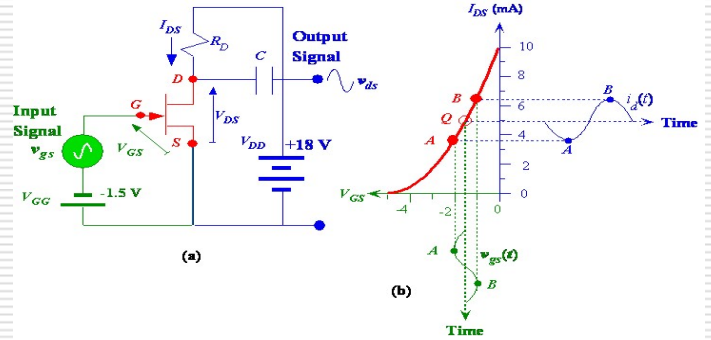A Simple CS Amplifier and Variation in I_{DS} with V_{gs}



(a) Common source (CS) ac amplifier using a JFET.

(b) Explanation of how I_D is modulated by the signal v_{gs} in series with the dc bias voltage V_{GG}