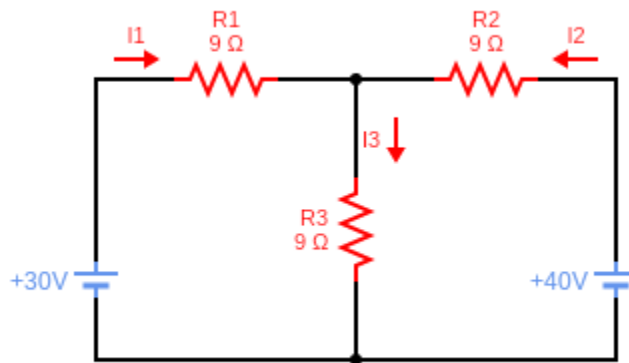


Experiment No. 03

Name of the Exp: Verification of superposition theorem.

Objective: Our objective is to find the total current through the resistors in the following circuit using superposition theorem.



Circuit Diagram 1.0

Theory: In this experiment we are verifying the superposition theory which states that *“The current through, or voltage across, any element of a network is equal to the algebraic sum of the currents or voltages produced independently by each source”*.

Apparatus:

1. DC power supply
2. Resistors
3. Digital multi meter
4. Bread board
5. Connection wire


Procedure:

1. For the 1st step of superposition theorem, we must disconnect one of the voltage sources and replace it with a short circuit.
2. Then determine the current through each resistor for the 1st voltage source.
3. As for the 2nd step of superposition theorem, we are going to disconnect the other voltage source from the circuit and replace it with a short circuit.
4. Then determine the current through each resistor for the 2nd voltage source.


5. Now we sum up the currents for 1st & 2nd voltage source and match with the total current value that we got practically.

Circuit Diagram:

1. For theoretical calculations

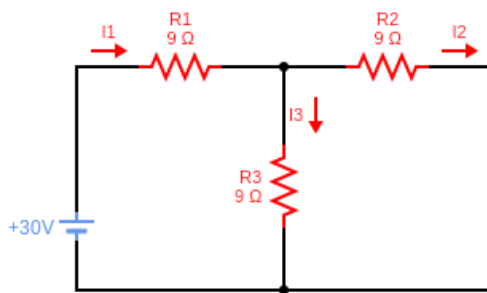


Circuit Diagram 2.0

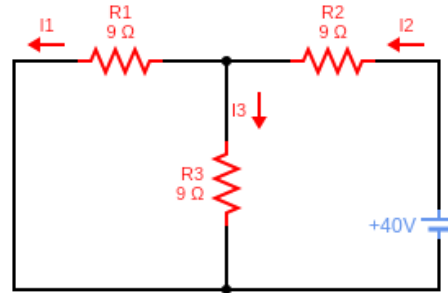


Circuit Diagram 3.0


2. Measured Value

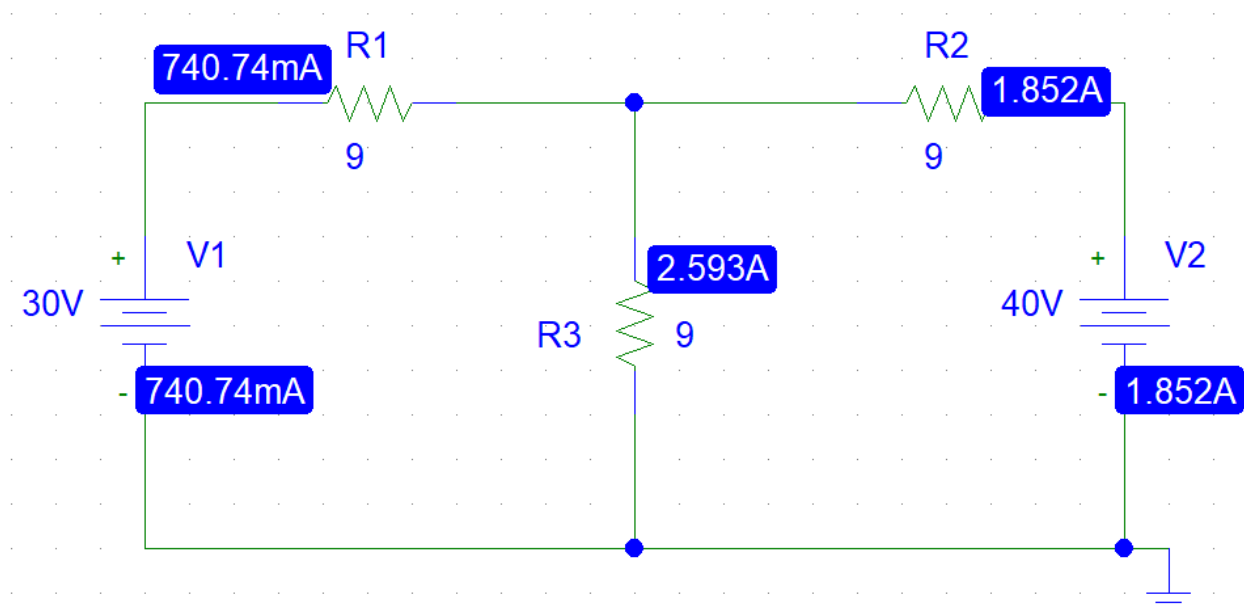

Circuit Diagram 1.1

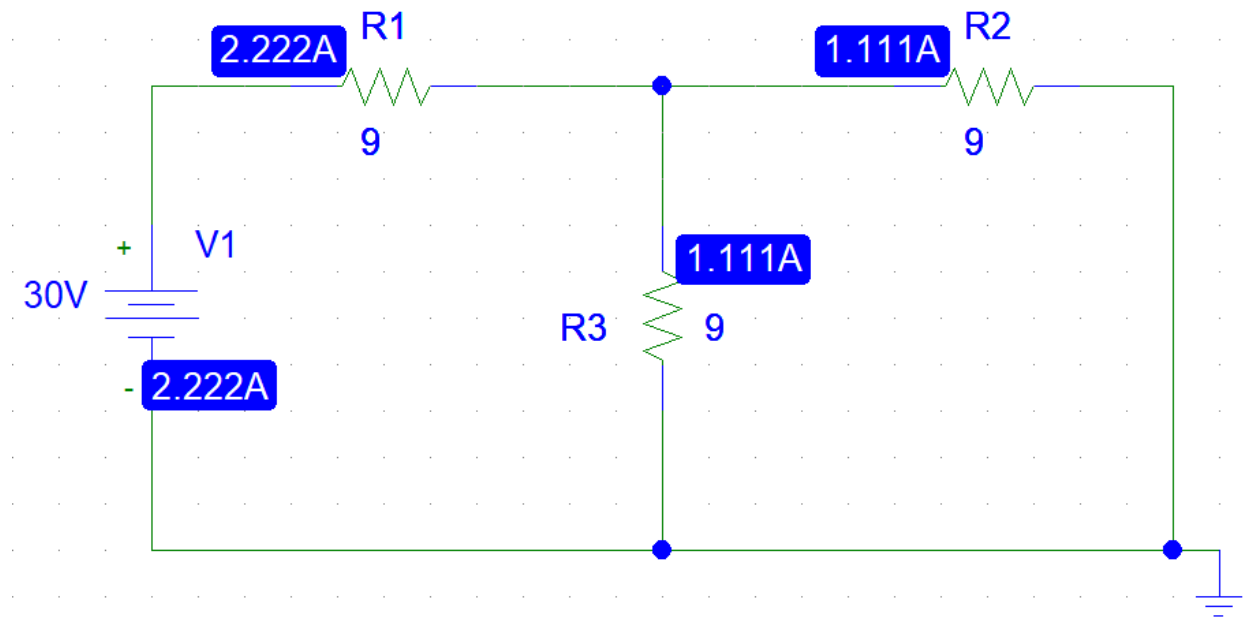

Circuit Diagram 2.2

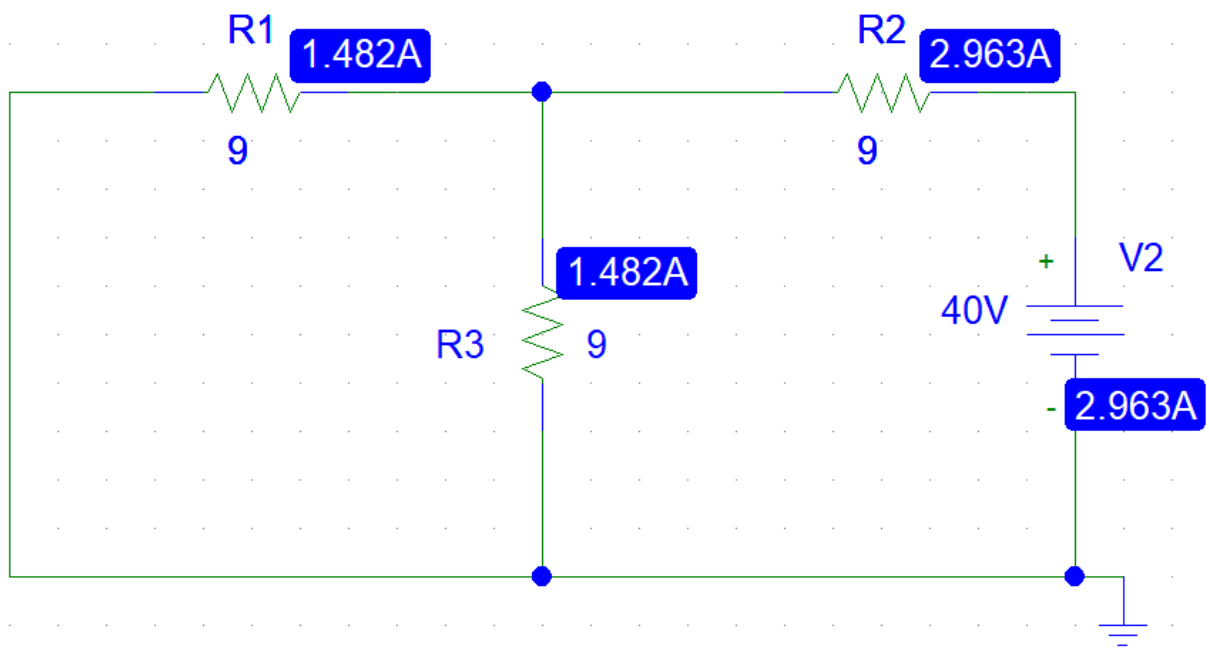

Circuit Diagram 3.3

Model Calculation: (For theoretical & measured value).

Theoretical:

Let's say, $R_1 = R_2 = R_3 = 9\Omega$, $E_1 = 30V$, $E_2 = 40V$

For E_1 in circuit diagram 2.0 we get,

$$\frac{1}{R_{(2+3)}} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{9} + \frac{1}{9} = \frac{2}{9} = \frac{1}{4.5}$$

or, $R_{(2+3)} = 4.5\Omega$ Now,

$$R_T = R_1 + R_{(2+3)} = 9 + 4.5 = 13.5$$

$$\text{or, } R_{T_1} = 13.5\Omega$$

For E_1

$$I_{T_1} = \frac{E_1}{R_{T_1}} = \frac{30}{13.5} = 2.22A$$

$I'_1 = I_{T_1}$ & Using current divider rule we get,

$$I'_3 = \frac{I_{T_1} \cdot R_2}{R_2 + R_3} = \frac{2.22 \times 9}{18} = 1.11A \quad I'_2 = \frac{I_{T_1} \cdot R_3}{R_2 + R_3} = \frac{2.22 \times 9}{18} = 1.11A$$

For E_2 in circuit diagram 3.0 we get,

$$\frac{1}{R_{(1+3)}} = \frac{1}{R_1} + \frac{1}{R_3} = \frac{1}{9} + \frac{1}{9} = \frac{2}{9}$$

or, $R_{(1+3)} = 4.5\Omega$ Now,

$$R_{T_2} = R_{(1+3)} + R_2 = 4.5 + 9 = 13.5\Omega$$

For E_2

$$I_{T_2} = \frac{E_2}{R_{T_2}} = \frac{40}{13.5} = 2.963A$$

$I''_2 = I_{T_2}$ & Using current divider rule we get,

$$I_3'' = \frac{I_{T_2} \cdot R_1}{R_1 + R_3} = \frac{2.963 \times 9}{18} = 1.481A \quad I_1'' = \frac{I_{T_2} \cdot R_3}{R_1 + R_3} = \frac{2.963 \times 9}{18} = 1.481A$$

Now according to superposition theorem, we are going to do the algebraical sum of the current for E_1 & E_2 and see if the sum matches out for total current.

Since the direction of I_1' & I_1'' is opposite so,

$$I_1 = I_1' - I_1'' = 2.22 - 1.481 = 0.738A$$

It means the direction of I_1 is the same direction of I_1' .

And the direction of I_2' & I_2'' is also opposite so,

$$I_2 = I_2' - I_2'' = 1.11 - 2.963 = -1.853A = 1.853A$$

The negative sign means the direction of I_2 is in the direction of I_2'' .

The direction of I_3' & I_3'' is in the same direction so,

$$I_3 = I_3' + I_3'' = 1.11 + 1.481 = 2.591A$$

Since both current is in the same direction so the current I_3 will flow the same way as I_3' & I_3'' .

Result: The result for theoretical (TV) and measured (MV) value is given below

For E_1

Current (A)	I_{T_1}		I_1'		I_2'		I_3'	
Values	TV	MV	TV	MV	TV	MV	TV	MV
(TV)&(MV)	2.22	2.222	2.22	2.222	1.11	1.111	1.11	1.111

For E_2

Current (A)	I_{T_2}		I_1''		I_2''		I_3''	
Values	TV	MV	TV	MV	TV	MV	TV	MV
(TV)&(MV)	2.963	2.963	1.481	1.482	2.963	2.963	1.481	1.482

For E_1 & E_2

Current (A)	I_1		I_2		I_3	
Values (TV)&(MV)	TV	MV	TV	MV	TV	MV
	0.738	0.740	1.853	1.852	2.591	2.593

Conclusion: The theoretical and measured value of this circuit matches up. So, we can say the superposition theorem, was applied & verified successfully.

Precautions:

1. Check for proper connections before switching ON the power supply.
2. Take care of the reading the apparatus.
3. The terminal of the resistance should be properly connected.