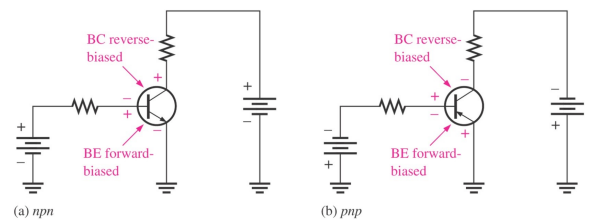


## BJT OPERATION


## 2. BJT OPERATION

- To operate the transistor properly, the two pn junction must be correctly biased with external dc voltages.
- The figure shows the proper bias arrangement for both *npn* and *pnp* transistor for its operation as an amplifier.



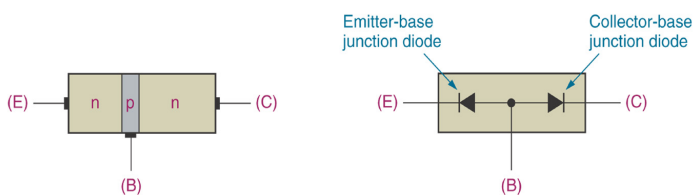
## 2. BJT OPERATION

- Transistor is made of 3 separate semiconductor materials that joined together to form two pn junction.
- Point at which emitter and base are joined forms a single pn junction → **base-emitter junction**
- Collector-base junction → **point where base and collector meet.**



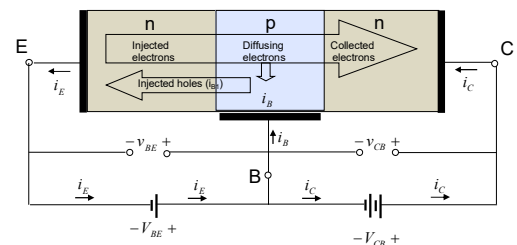
## 2. Operation of the npn Transistor in the Active Mode


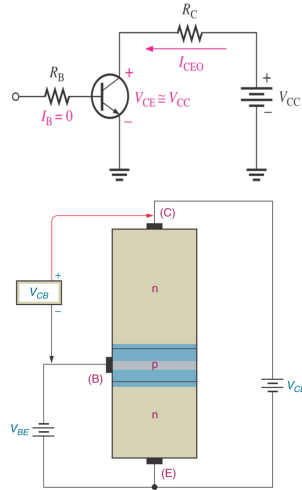
## 2. BJT OPERATION


- **Cutoff region**
- Both transistor junctions are reverse biased.
- With large depletion region between C-B and E-B, very small amount of reverse current,  $I_{CEO}$  passes from emitter to collector and can be neglected.
- So,  $V_{CE} = V_{CC}$



## 2. BJT OPERATION


- **Saturation region**

$$I_c = \frac{V_{CC}}{R_C}$$

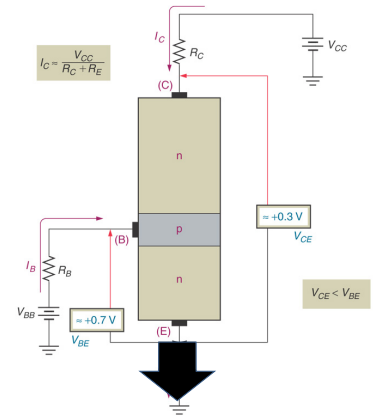
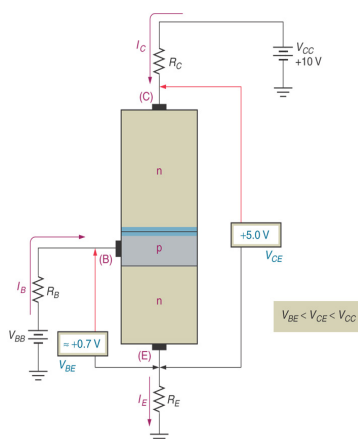
## 2. BJT OPERATION

- **Active region**
- $BE$  junction is forward biased and the  $BC$  junction is reverse biased.
- All terminal currents have some measurable value.
- The magnitude of  $I_C$  depends on the values of  $\beta$  and  $I_B$ .
- $V_{CE}$  is approximately near to 0.7V and  $V_{CE}$  falls in ranges  $V_{BE} < V_{CE} < V_{CC}$ .




## 2. BJT OPERATION

### Transistor Operating Regions:
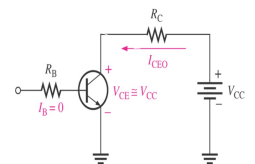
#### 1. Cutoff region:

- Both transistor junctions are reverse biased
- All terminal currents are approximately equal to zero. Since  $I_{CEO}$  neglected,  $V_{CE} = V_{CC}$




#### 2. Active region:

- The  $BE$  junction is forward biased and the  $BC$  junction is reverse biased
- All terminal currents have some measurable value
- The magnitude of  $I_C$  depends on the values of  $\beta$  and  $I_B$
- $V_{CE}$  is approximately near to 0.7V and  $V_{CE}$  falls in ranges  $V_{BE} < V_{CE} < V_{CC}$
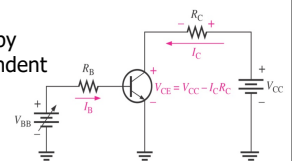
#### 3. Saturation:

- Both transistor junctions are forward biased
- $I_C$  reaches its maximum values- determine by the component in the CE circuit, and independent of the values of  $\beta$  and  $I_B$
- $V_{BE}$  is approximately 0.7V and  $V_{CE} < V_{BE}$



### 3. BJT CHARACTERISTICS & PARAMETERS

### 3. BJT CHARACTERISTICS & PARAMETERS

#### DC Beta ( $\beta_{DC}$ ) and DC Alpha ( $\alpha_{DC}$ ):

➤ The ratio of the dc collector current ( $I_C$ ) to the dc base current ( $I_B$ ) is the dc beta

( $\beta_{DC}$ ) = dc current gain of transistor

➤ Range value :  $20 < \beta_{DC} < 200$

➤ Usually designed as an equivalent hybrid ( $h$ ) parameter,  $h_{FE}$  on transistor data sheet –  $h_{FE} = \beta_{DC}$

$$\beta_{DC} = \frac{I_C}{I_B}$$

➤ The ratio of the dc collector current ( $I_C$ ) to the dc emitter current ( $I_E$ ) is the dc alpha ( $\alpha_{DC}$ ) – less used parameter in transistor circuits

➤ Range value- $\rightarrow 0.95 < \alpha_{DC} < 0.99$  or greater, but  $< 1$  ( $I_C < I_E$ )

$$\alpha_{DC} = \frac{I_C}{I_E}$$

### 3. BJT CHARACTERISTICS & PARAMETERS

#### Current and Voltage Analysis:

➤ The current and voltage can be identified as follow:

➤ Current:

dc base current,  $I_B$

dc emitter current,  $I_E$

dc collector current,  $I_C$


Voltage:

dc voltage at base with respect to emitter,  $V_{BE}$

dc voltage at collector with respect to base,  $V_{CB}$

dc voltage at collector with respect to emitter,  $V_{CE}$

forward-biased the base-emitter junction

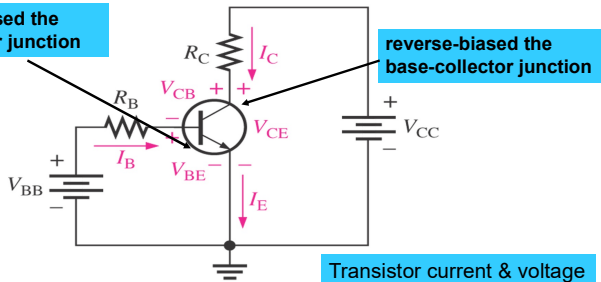

### 3. BJT CHARACTERISTICS & PARAMETERS

#### Current and Voltage Analysis:

➤ When the  $BE$  junction is forward-biased, like a forward biased diode and the voltage drop is  $V_{BE} \cong 0.7V$

➤ Since the emitter is at ground (0V), by Kirchhoff's voltage law, the voltage across  $R_B$  is:  $V_{R_B} = V_{BB} - V_{BE}$  .....(1)


➤ Also, by Ohm's law:

➤  $V_{R_B} = I_B R_B$  .....(2)

➤ From (1)  $\rightarrow$  (2):  $V_{BB} - V_{BE} = I_B R_B$

Therefore, the dc base current is:

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

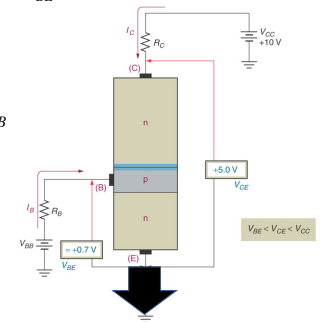

### 3. BJT CHARACTERISTICS & PARAMETERS

#### Current and Voltage Analysis:

➤ The voltage at the collector with respect to the grounded emitter is:  
 $V_{CE} = V_{CC} - V_{R_C}$

➤ Since the drop across  $R_C$  is:  $V_{R_C} = I_C R_C$

➤ The dc voltage at the collector with respect to the emitter is:

$$V_{CE} = V_{CC} - I_C R_C$$

where


$$I_C = \beta_{DC} I_B$$

➤ The dc voltage at the collector with respect to the base is:

$$V_{CB} = V_{CE} - V_{BE}$$
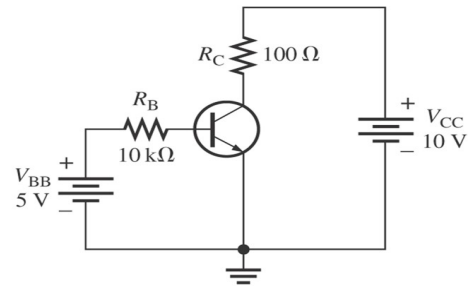
#### Example 1

- Determine  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{CE}$  and  $V_{CB}$  in the circuit below. The transistor has a  $\beta_{DC} = 150$ .



#### Solution Example 1

When BE junction is FB, act as normal diode. So,  $V_{BE} = 0.7V$ .  
 The base current,

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 - 0.7}{10k\Omega} = 430 \mu A$$

Collector current,  $I_C = \beta_{DC} I_B = 150 (430 \mu A) = 64.5 mA$

Emitter current,  $I_E = I_C + I_B = 64.5 mA + 430 \mu A = 64.9 mA$

Solve for  $V_{CE}$  and  $V_{CB}$ .

$$V_{CE} = V_{CC} - I_C R_C = 10V - (64.5 mA)(100\Omega) = 3.55V$$

$$V_{CB} = V_{CE} - V_{BE} = 3.55 - 0.7 = 2.85V$$