
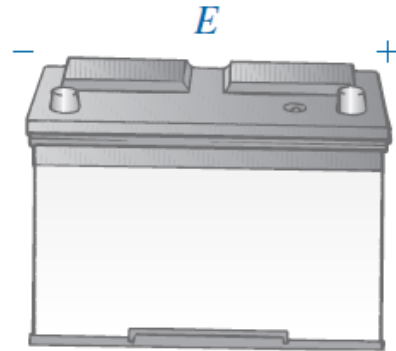


Parallel DC Circuit



By Ariful Islam
Dept. of EEE
University of Dhaka

VOLTAGE REGULATION AND THE INTERNAL RESISTANCE OF VOLTAGE SOURCES

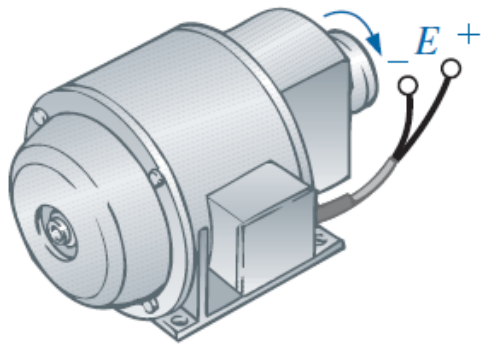every practical (real-world) supply has an internal resistance in series with the idealized voltage source



(a)

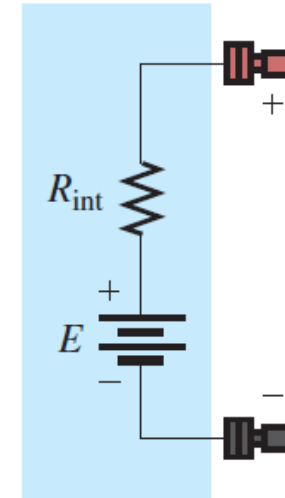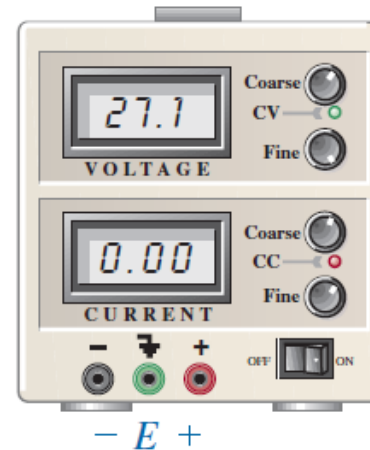

(b)

VOLTAGE REGULATION AND THE INTERNAL RESISTANCE OF VOLTAGE SOURCES

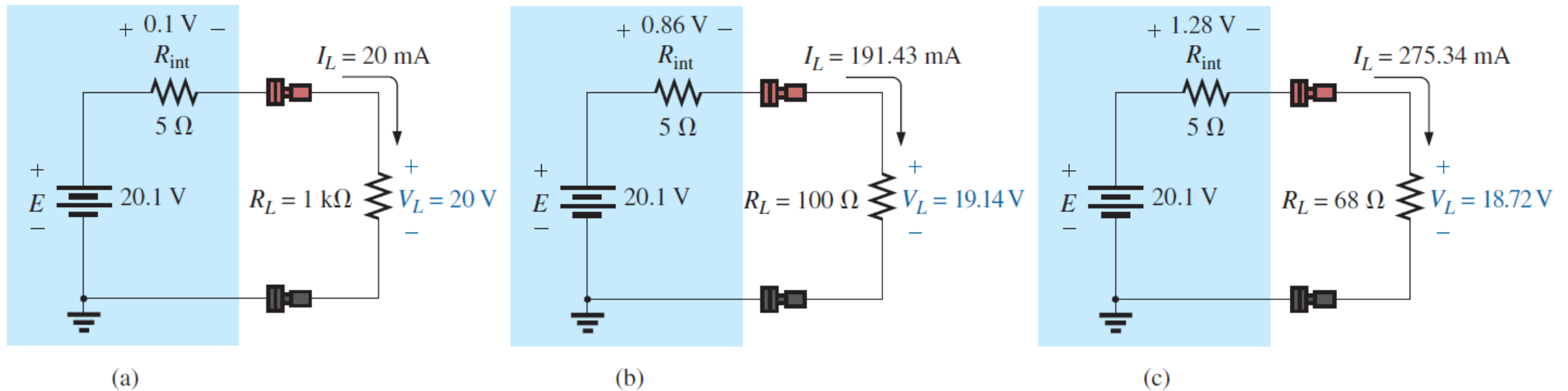


FIG. 66

Demonstrating the effect of changing a load on the terminal voltage of a supply.

VOLTAGE REGULATION AND THE INTERNAL RESISTANCE OF VOLTAGE SOURCES

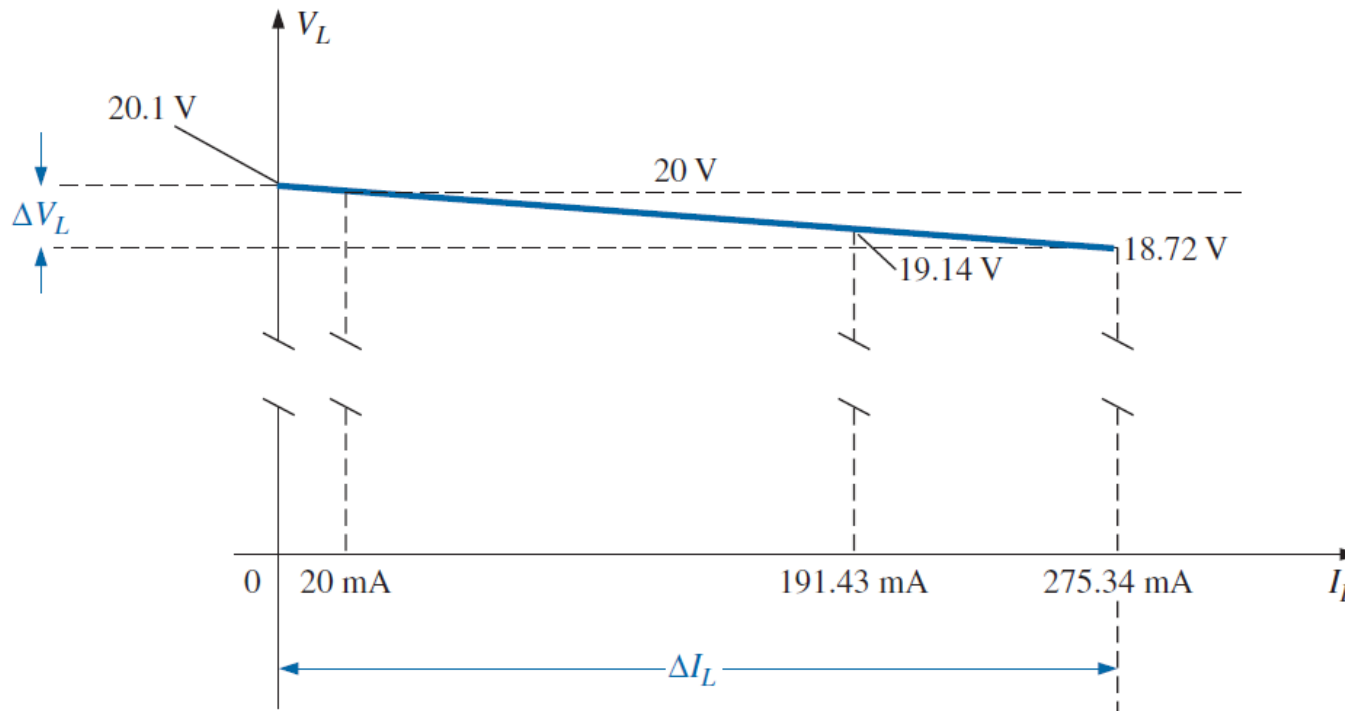


FIG. 67

Plotting V_L versus I_L for the supply in Fig. 66.

VOLTAGE REGULATION AND THE INTERNAL RESISTANCE OF VOLTAGE SOURCES

$$R_{\text{int}} = \frac{\Delta V_L}{\Delta I_L} \quad (\text{ohms, } \Omega) \quad (13)$$

which for the plot in Fig. 67 results in

$$R_{\text{int}} = \frac{\Delta V_L}{\Delta I_L} = \frac{20.1 \text{ V} - 18.72 \text{ V}}{275.34 \text{ mA} - 0 \text{ mA}} = \frac{1.38 \text{ V}}{275.34 \text{ mA}} = 5 \Omega$$

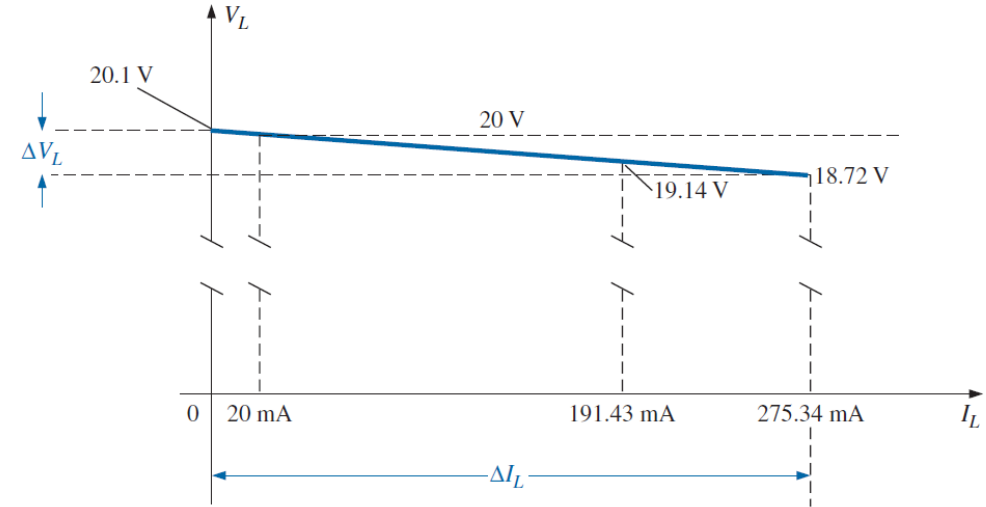


FIG. 67

Plotting V_L versus I_L for the supply in Fig. 66.

VOLTAGE REGULATION AND THE INTERNAL RESISTANCE OF VOLTAGE SOURCES

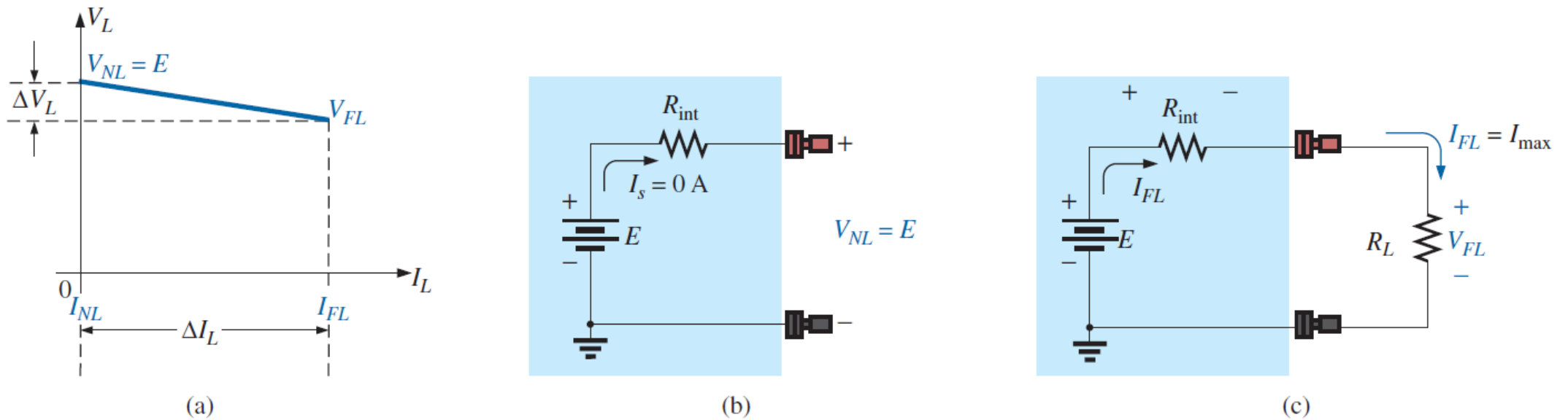


FIG. 68

Defining the properties of importance for a power supply.

VOLTAGE REGULATION AND THE INTERNAL RESISTANCE OF VOLTAGE SOURCES

$$VR = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

$$VR = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\% = \frac{20.1 \text{ V} - 18.72 \text{ V}}{18.72 \text{ V}} \times 100\% \cong \mathbf{7.37\%}$$

VOLTAGE REGULATION AND THE INTERNAL RESISTANCE OF VOLTAGE SOURCES

EXAMPLE 28

- Given the characteristics in Fig. 70, determine the voltage regulation of the supply.
- Determine the internal resistance of the supply.
- Sketch the equivalent circuit for the supply.

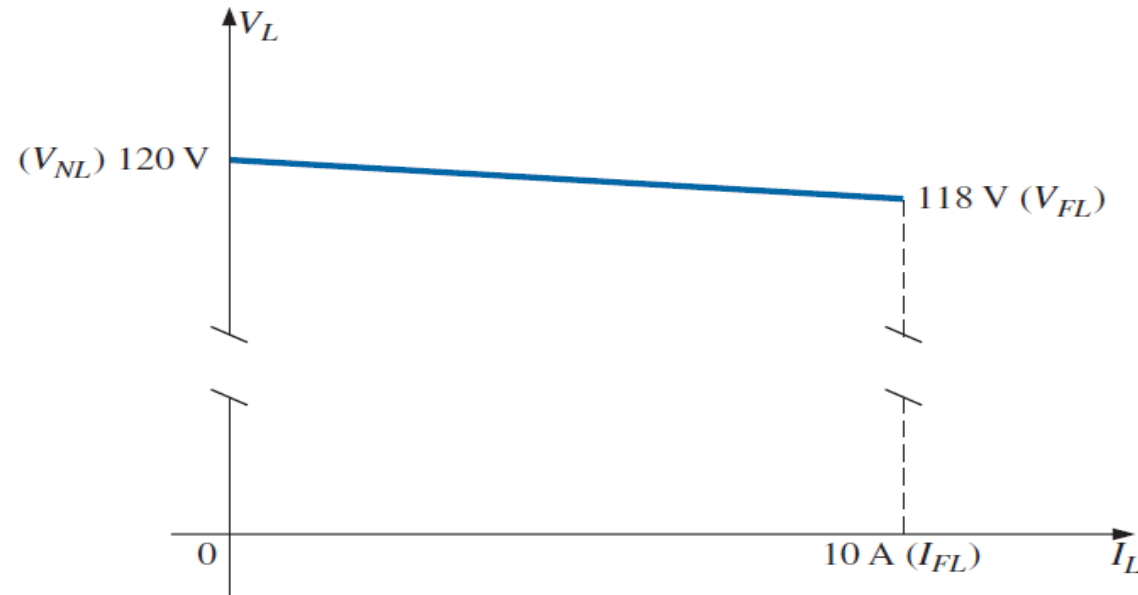


FIG. 70

Terminal characteristics for the supply of Example 28.

VOLTAGE REGULATION AND THE INTERNAL RESISTANCE OF VOLTAGE SOURCES

Solutions:

$$\begin{aligned} \text{a. } VR &= \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\% \\ &= \frac{120 \text{ V} - 118 \text{ V}}{118 \text{ V}} \times 100\% = \frac{2}{118} \times 100\% \\ VR &\cong \mathbf{1.7\%} \end{aligned}$$

$$\text{b. } R_{\text{int}} = \frac{\Delta V_L}{\Delta I_L} = \frac{120 \text{ V} - 118 \text{ V}}{10 \text{ A} - 0 \text{ A}} = \frac{2 \text{ V}}{10 \text{ A}} = \mathbf{0.2 \Omega}$$

c. See Fig. 71.

Parallel DC Circuits

EXAMPLE 3 Find the total resistance of the configuration in Fig. 6.

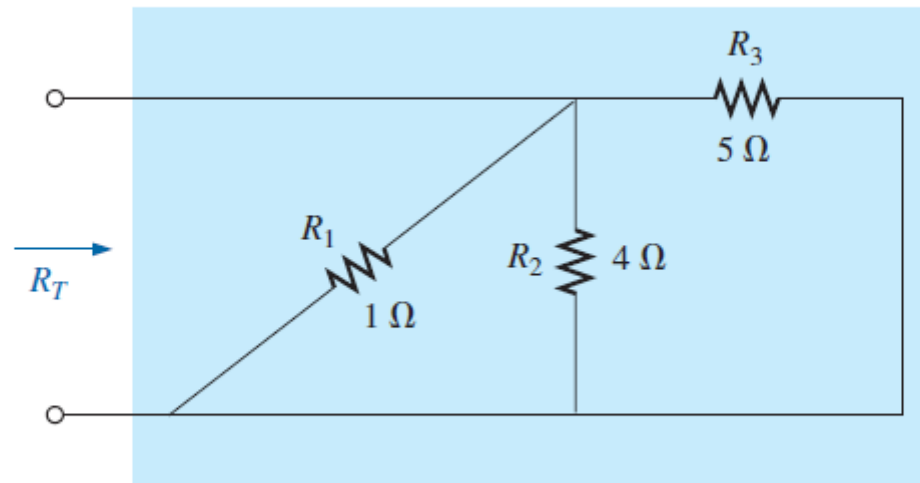


FIG. 6

Network to be investigated in Example 3.

Parallel DC Circuits

EXAMPLE 4

- What is the effect of adding another resistor of $100\ \Omega$ in parallel with the parallel resistors of Example 1 as shown in Fig. 8?
- What is the effect of adding a parallel $1\ \Omega$ resistor to the configuration in Fig. 8?

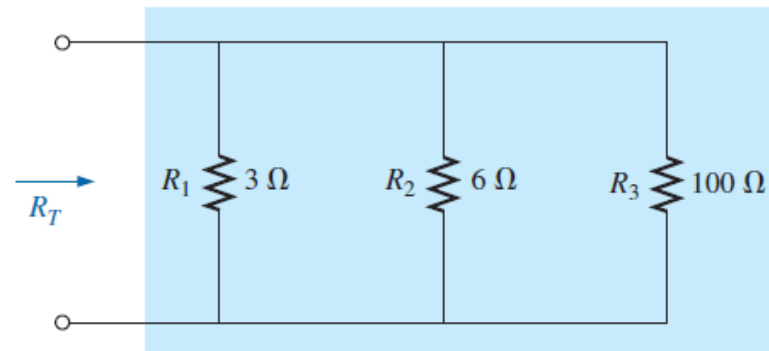


FIG. 8

Adding a parallel $100\ \Omega$ resistor to the network in Fig. 4.

Parallel DC Circuits

EXAMPLE 6 Find the total resistance for the configuration

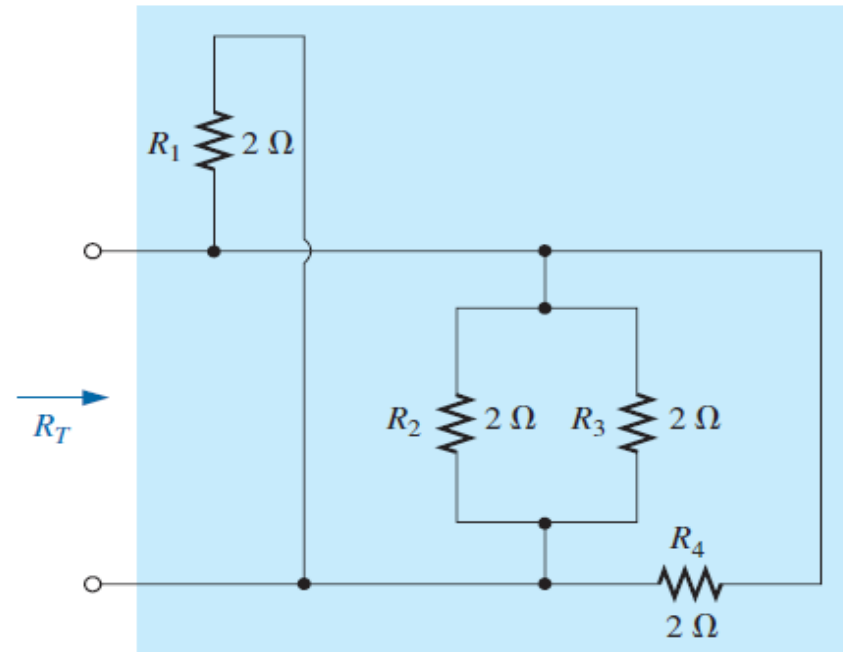


FIG. 10

Parallel configuration for Example 6.

Parallel DC Circuits

EXAMPLE 12 For the parallel network in Fig. 22:

- Find the total resistance.
- Calculate the source current.
- Determine the current through each parallel branch.
- Show that Eq. (9) is satisfied.

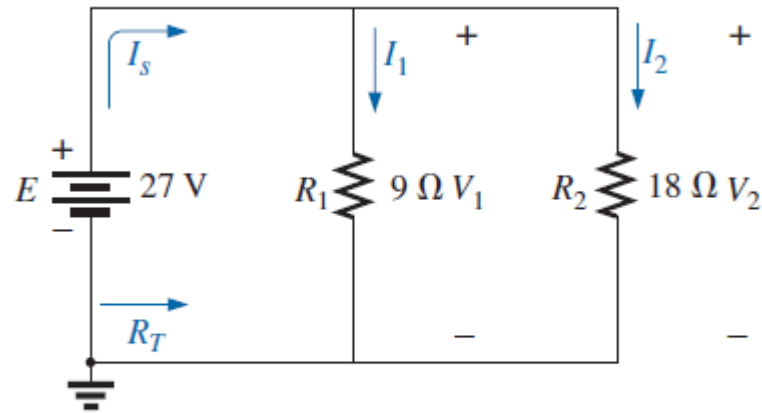


FIG. 22

Parallel network for Example 12.

Parallel DC Circuits

EXAMPLE 15 For the parallel network in Fig. 29 (all standard values):

- Determine the total resistance R_T .
- Find the source current and the current through each resistor.
- Calculate the power delivered by the source.
- Determine the power absorbed by each parallel resistor.
- Verify Eq. (10).


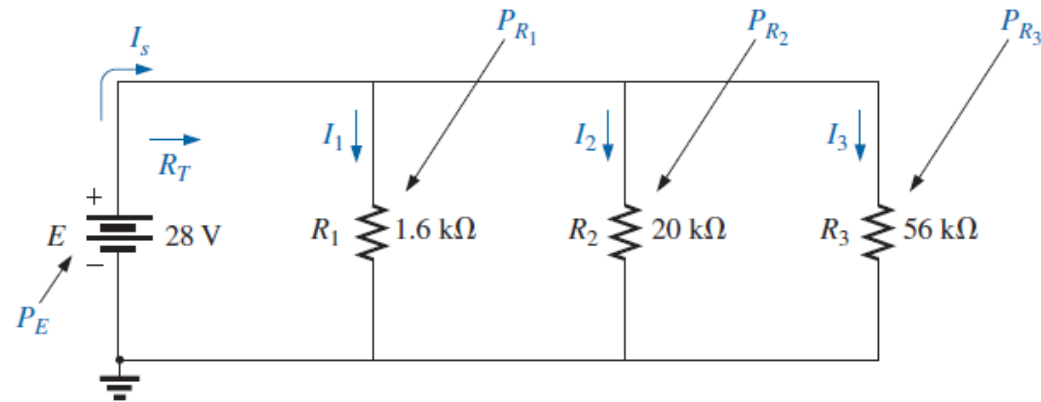


FIG. 29

Parallel network for Example 15.

Parallel DC Circuits

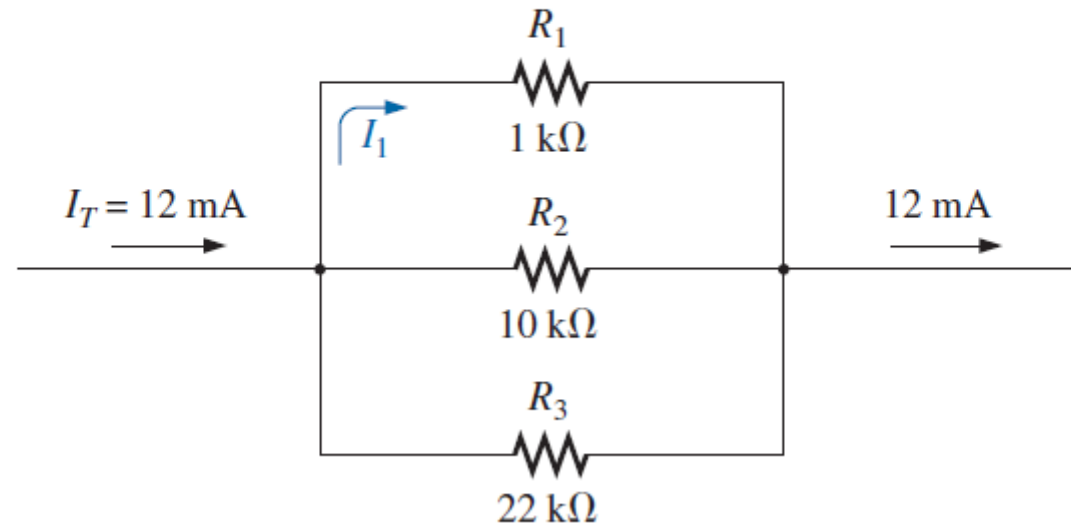EXAMPLE 22 For the parallel network in Fig. 41, determine current I_1 using Eq. (14).



VOLTAGE SOURCES IN PARALLEL

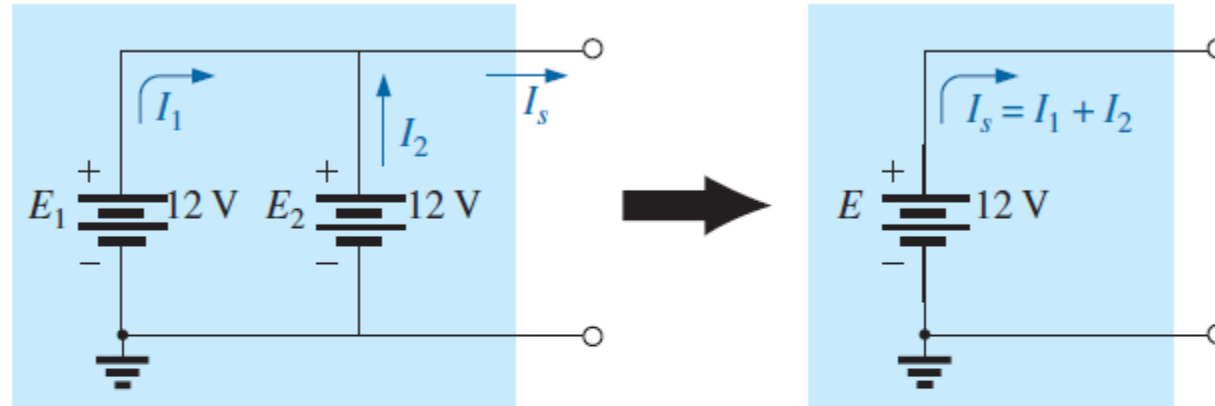


FIG. 46

Demonstrating the effect of placing two ideal supplies of the same voltage in parallel.

- Voltage sources can be placed in parallel only if they have the same voltage.
- The primary reason for placing two or more batteries or supplies in parallel is to increase the current rating above that of a single supply.

VOLTAGE SOURCES IN PARALLEL

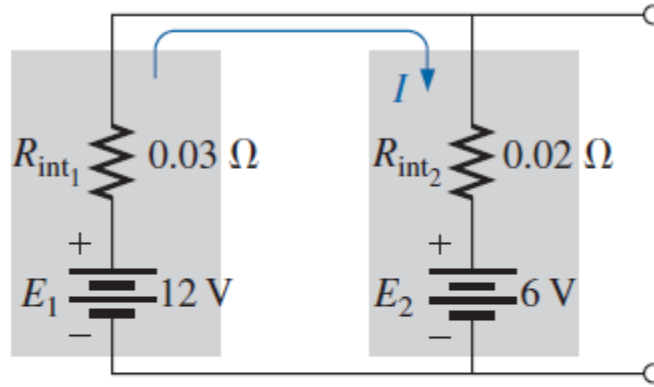


FIG. 47

Examining the impact of placing two lead-acid batteries of different terminal voltages in parallel.

$$I = \frac{E_1 - E_2}{R_{\text{int}1} + R_{\text{int}2}} = \frac{12\text{ V} - 6\text{ V}}{0.03\ \Omega + 0.02\ \Omega} = \frac{6\text{ V}}{0.05\ \Omega} = 120\text{ A}$$

Open Circuit

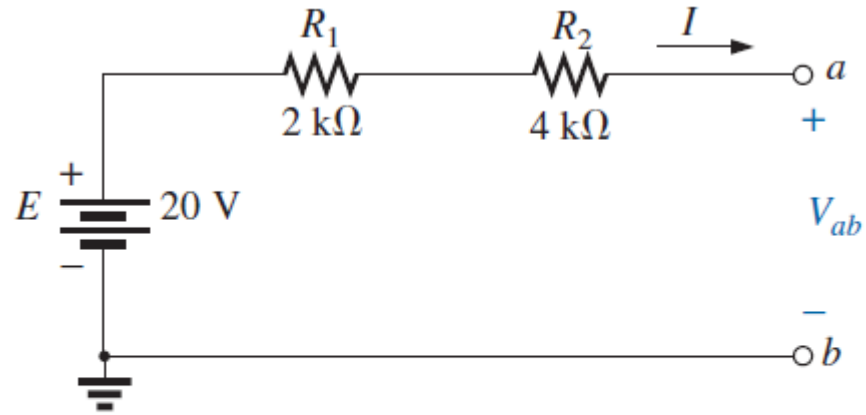


FIG. 53

Network for Example 25.

Open Circuit

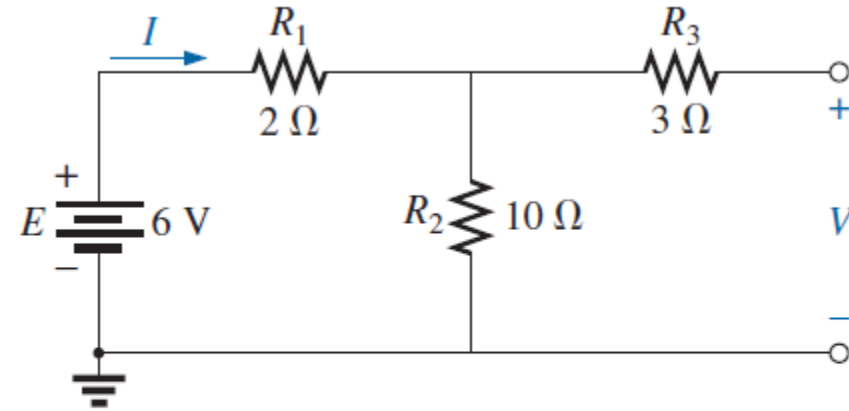


FIG. 58

Network for Example 28.

Voltmeter loading effect

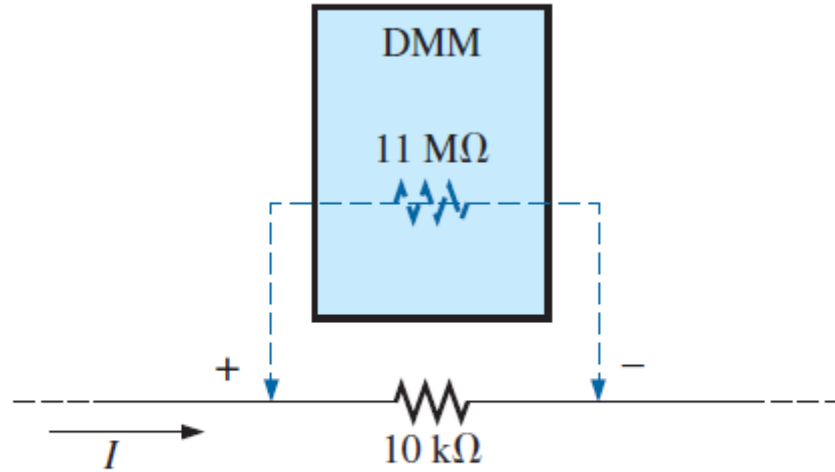


FIG. 60

Voltmeter loading.

$$R_T = 10\text{ k}\Omega \parallel 11\text{ M}\Omega = \frac{(10^4\ \Omega)(11 \times 10^6\ \Omega)}{10^4\ \Omega + (11 \times 10^6)} = 9.99\text{ k}\Omega$$