

Sheikh Hasina University, Netrokona
Department of Computer Science and Engineering
CSE-2205: Introduction to Mechatronics

Lec-20: Electrical System Models

Mechatronics: Electronic Control Systems in Mechanical Engineering by W. Bolton



Md. Ariful Islam
Assistant Professor
Dept. of Robotics and Mechatronics Engineering
University of Dhaka
&
Adjunct Faculty
Sheikh Hasina University, Netrokona
Department of Computer Science and Engineering

Electrical building blocks:



- inductors ✓
- capacitors ✓
- Resistors ✓

Lenz law

1) Inductors

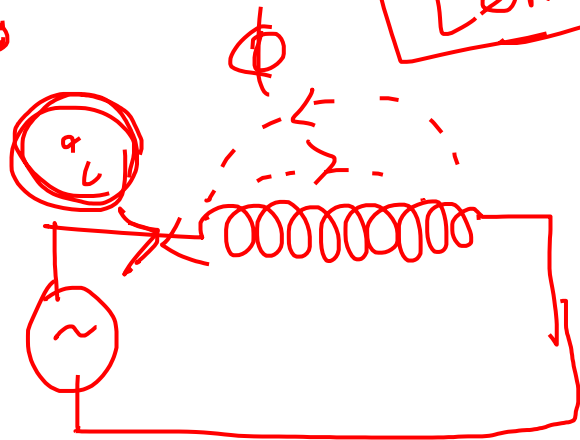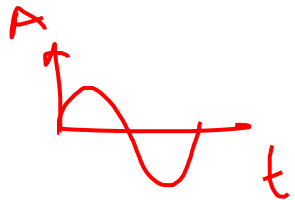
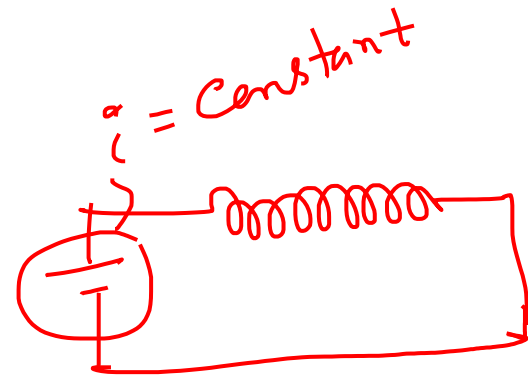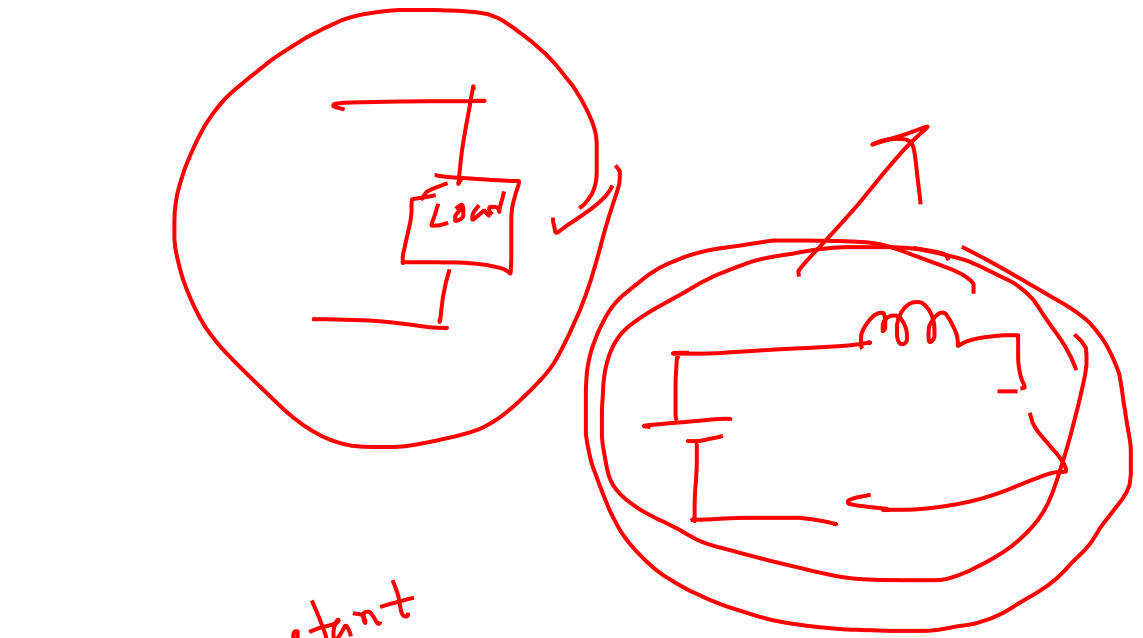
$$EMF \propto - \frac{di}{dt}$$
$$V = L \frac{di}{dt} \quad \text{--- (i)}$$



$$EMF \propto \frac{d}{dt}(i)$$

constant

$$EMF \propto \frac{d}{dt}(0)$$

$$V = L \frac{di}{dt}$$

$$i \cdot di$$

Energy stored by inductor:

$$\mathcal{E} = - \frac{d\phi}{dt}$$

$$\phi \propto I \quad \text{inductance}$$

$$\phi = LI$$

$$V = L \frac{dI}{dt}$$

$$P = VI = L \frac{dI}{dt} \cdot I$$

$$\Rightarrow L di = V dt$$

$$\Rightarrow di = \frac{1}{L} V dt$$

$$\Rightarrow \boxed{i = \frac{1}{L} \int V dt} - (ii)$$

sys model of inductor block.

~~2) Capacitors~~

$$p = -L \frac{dI}{dt} \cdot I$$

p = rate of change of
energy (work done)

$$\frac{dW}{dt} = -L I \frac{dI}{dt}$$

integrating

$$\Rightarrow W = - \int L I \frac{dI}{dt} dt$$

$$\Rightarrow W = - \int L \cdot I \cdot dI$$

$$W = -L \int_0^{I_0} I dI$$

$$\rightarrow W =$$

$$W = -L \frac{1}{2} I^2$$

$$W = -\frac{1}{2} L I^2$$

$$-L \int_{I_0}^I I dI =$$

$$-\frac{1}{2} L I^2 + \frac{1}{2} L I_0^2$$

I_0

Summary:


Induction:

~~i~~ $v = L \frac{di}{dt}$ ✓

$$i = \frac{1}{L} \int v dt$$
 ✓

$$E = W = \frac{1}{2} L i^2$$
 ✓

2) Capacitors:

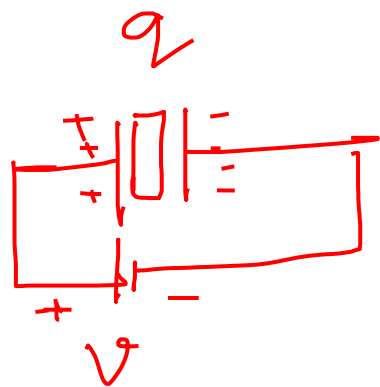

$$q \propto V$$

$$q = CV$$

capacitance

$$\Rightarrow V = \frac{q}{C}$$

$V = \frac{1}{C} \int i dt$

 (i)

← (e)

$$i = \frac{dq}{dt}$$

$$\Rightarrow dq = i dt$$

$$\Rightarrow \int dq = \int i dt$$

$$q = \int i dt$$

\Rightarrow

$$q \propto v$$

$$q = cv$$

$$\Rightarrow v = \frac{q}{c}$$

Differentiate w.r.t time

$$\Rightarrow \frac{dv}{dt} = \frac{1}{c} \frac{dq}{dt}$$

$$\Rightarrow \frac{dv}{dt} = \frac{1}{c} \cdot i$$

$$\Rightarrow \boxed{i = c \frac{dv}{dt}}$$

Energy stored by capacitors:

$$q \propto v$$

$$q = cv$$

$$v = \frac{q}{c}$$

$$\Rightarrow c = \frac{q}{v}$$

$$W = \boxed{FS}$$

Work done q

$$W = \int_0^q v dq$$

$$= \int_0^q \frac{q}{c} dq$$

$$W = \frac{1}{c} \int_0^q q \, dq$$

$$= \frac{1}{2} \frac{q^2}{c}$$

$$q = cv$$

$$W = \frac{1}{2} \frac{c^2 v^2}{c}$$

$$W = \frac{1}{2} c v^2$$

Summe:

$$v = \frac{1}{c} \int i dt$$

$$i = c \frac{dv}{dt}$$

$$E = W = \frac{1}{2} c v^2$$

3) Resistor:



$$V = \underline{\underline{R i}} \checkmark$$

$$i = \frac{V}{R} \checkmark$$


does not store energy, but dissipates it
power dissipated by a resistor:

$$P = q V i$$

$$= V \cdot \frac{V}{R}$$

$$P = \frac{V^2}{R} \checkmark$$

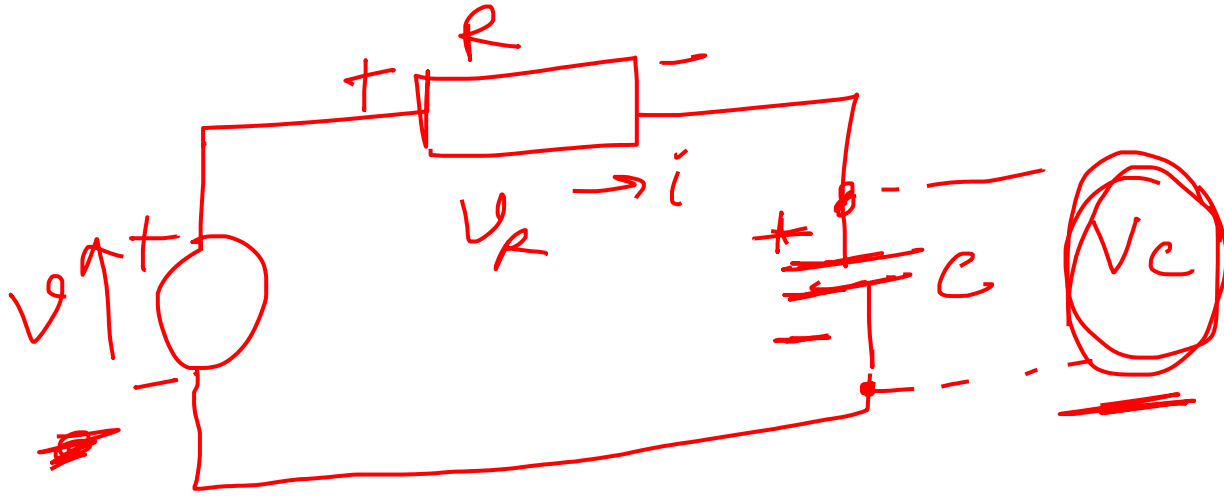Building up a model for an electrical system:



KVL:

$$v - v_R - v_C = 0$$

$$\Rightarrow v = v_R + v_C$$


$$\Rightarrow v = Ri + v_C$$

$$v = Ri + v_C$$
$$= R \cdot C \frac{dv_C}{dt} + v_C$$

$$\Rightarrow \boxed{v = RC \frac{dv_C}{dt} + v_C}$$

✓

Example: v & v_c

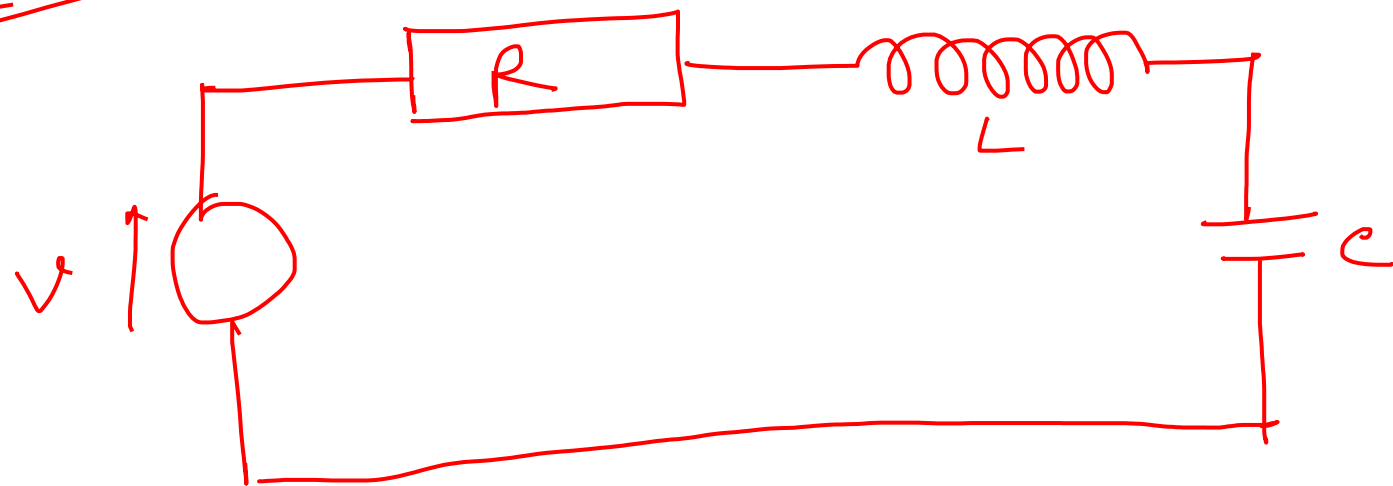

$$i = C \frac{dv_c}{dt}$$

KVL: $v - v_R - v_L - v_c = 0$


$$\Rightarrow v = v_R + v_L + v_c$$

$$v = iR + L \frac{di}{dt} + v_c$$

$$= C \frac{dv_c}{dt} R + L \frac{d}{dt} \left(C \frac{dv_c}{dt} \right) + v_c$$

$$v = RC \frac{dv_c}{dt} + LC \frac{d^2 v_c}{dt^2} + v_c$$

Example: input & inductor.

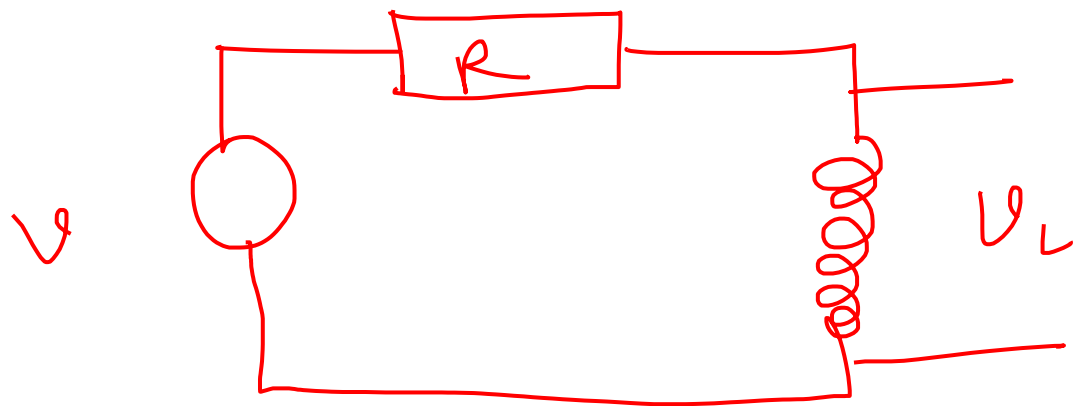

KVL

$$v - v_R - v_L = 0$$


$$\Rightarrow v = v_R + v_L$$

$$\Rightarrow v = \underline{i}R + v_L$$

$$v = \frac{1}{L} \int v_L dt$$

$$\Rightarrow v = \frac{R}{L} \int v_L dt + v_L$$

Example:

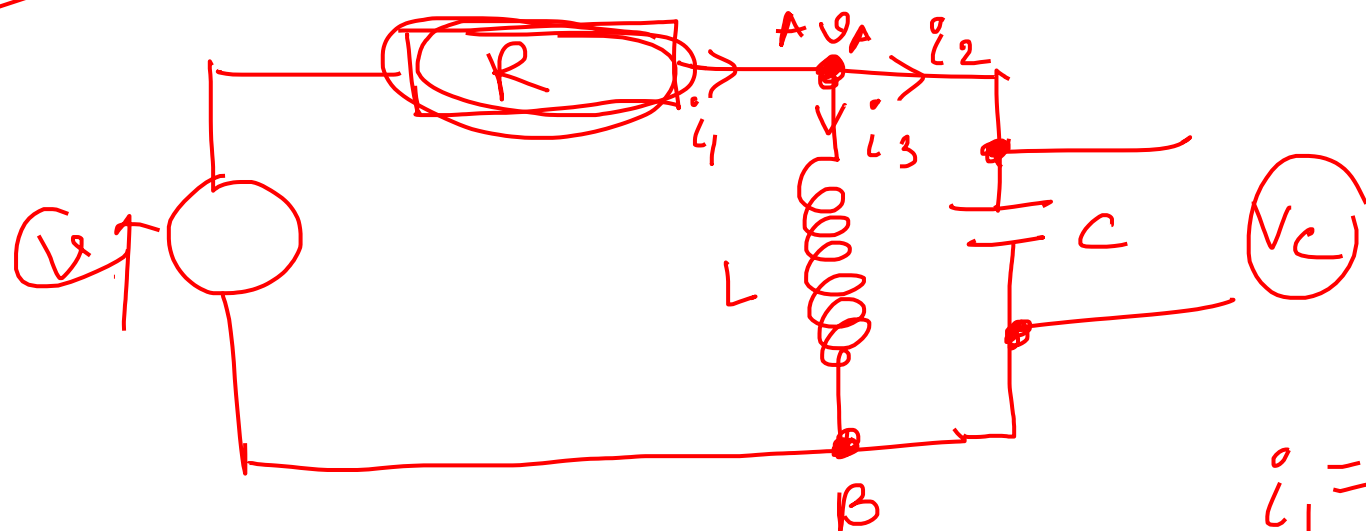

$$i = \frac{V}{R}$$

$$i_1 = \frac{V - V_A}{R}$$

$$i_2 = C \frac{dV_A}{dt}$$

$$i_3 = \frac{1}{L} \int V_A dt$$

KCL:

$$i_1 = i_2 + i_3$$

~~→~~

$$\hat{i}_1 = i_2 + i_3$$

$$\Rightarrow \frac{U - U_A}{R} = \frac{1}{L} \int U_A dt + C \frac{dU_A}{dt}$$

$$\Rightarrow U_A = U_C$$

$$\Rightarrow \frac{U - U_C}{R} = \frac{1}{L} \int U_C dt + C \frac{dU_C}{dt}$$

$$\Rightarrow \frac{U}{R} - \frac{U_C}{R} = \frac{1}{L} \int U_C dt + C \frac{dU_C}{dt}$$

$$\Rightarrow \frac{U}{R} = \frac{U_C}{R} + \frac{1}{L} \int U_C dt + C \frac{dU_C}{dt}$$

~~$$\Rightarrow \frac{v}{R} = \frac{1}{L} \int v_c dt$$~~

$$\Rightarrow \frac{v}{R} = \frac{v_c}{R} + \frac{1}{L} \int v_c dt + \frac{c dv_c}{dt}$$

$$\Rightarrow v = \frac{v_c}{R} \times R + \frac{R}{L} \int v_c dt + R c \frac{dv_c}{dt}$$

$$\Rightarrow v = v_c + \frac{R}{L} \int v_c dt + R c \frac{dv_c}{dt}$$

Electrical & mechanical analogies!

Resistor = Does not store energy

dashpot

~~Voltage~~

$$P = \frac{V}{R}$$

$$F = c \underline{v}$$
$$P = \underline{c v^2}$$

$\left(c = \frac{1}{R} \right)$ = velocity

voltage