

# Lecture 1


Introduction

# Introduction

- Electric Circuit
- System of Units
- Charge
- Electric Current
- Voltage
- Power and Energy
- Circuit Elements

# Electric Circuit


- An electric circuit is an interconnection of electrical elements.

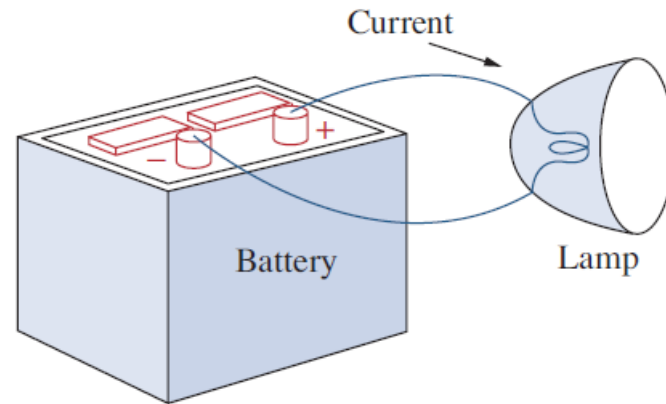

**Figure 1.1**  
A simple electric circuit.

# Electric Circuit

- An electric circuit is an interconnection of electrical elements.

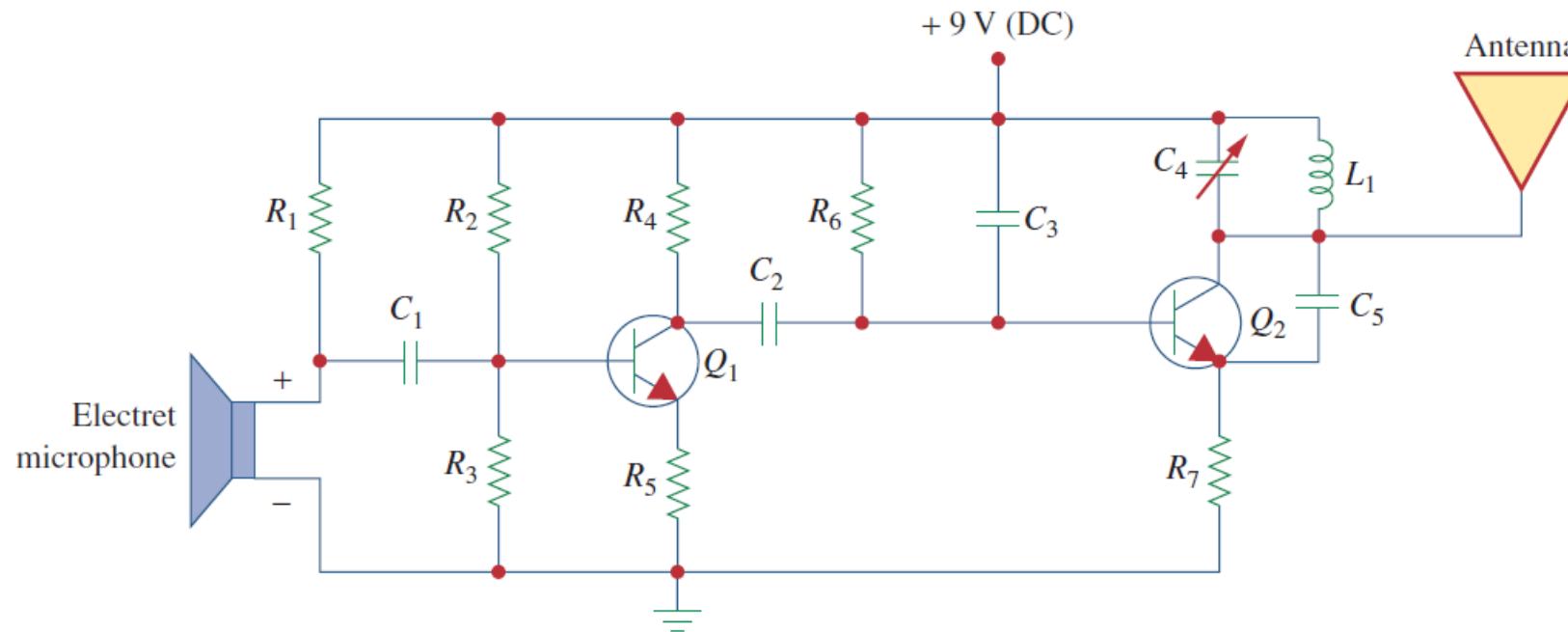

**Figure 1.2**

Electric circuit of a radio transmitter.

# System of Units

- As electrical engineers, we deal with measurable quantities.
- An international measurement language is the International System of Units (SI)

**TABLE 1.1**

Six basic SI units and one derived unit relevant to this text.


Quantity	Basic unit	Symbol
Length	meter	m
Mass	kilogram	kg
Time	second	s
Electric current	ampere	A
Thermodynamic temperature	kelvin	K
Luminous intensity	candela	cd
Charge	coulomb	C

# Charge

- Charge is an electrical property of the atomic particles of which matter consists, measured in coulombs (C).
- The coulomb is a large unit for charges. In 1 C of charge, there are electrons. Thus realistic or laboratory values of charges are on the order of pC, nC, or  $\mu\text{C}$
- The *law of conservation of charge* states that charge can neither be created nor destroyed, only transferred.

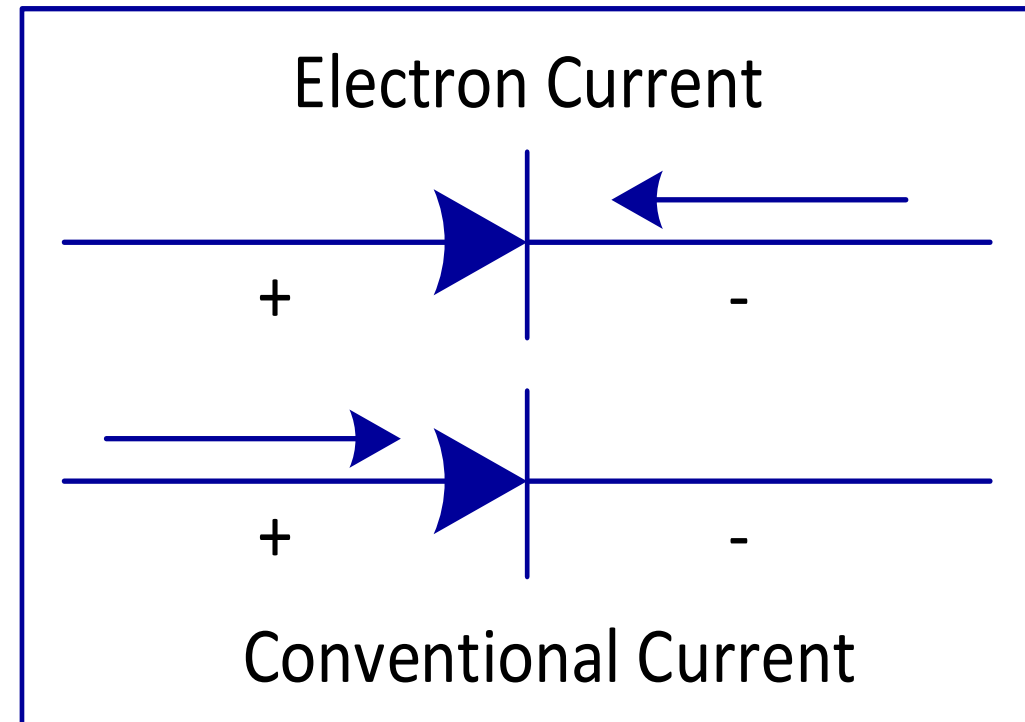
# Electric Current

- Current: The flow of electrons through a conductor
  - Measure in Ampere
  - Measured with Amp Meter
  - Electron Current flow
    - Negative to positive flow
  - Conventional Current flow
    - Positive to negative flow



# Electric Current

- Electric current is the time rate of change of charge, measured in amperes (A).

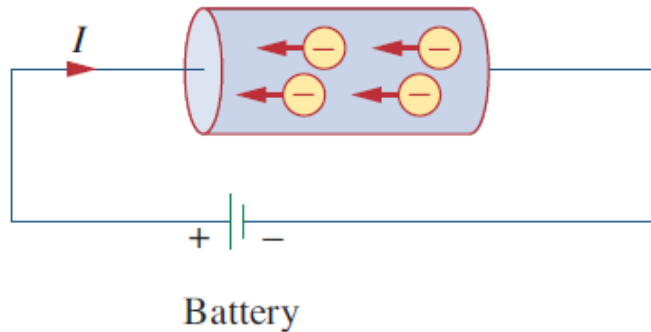

**Figure 1.3**


Electric current due to flow of electronic charge in a conductor.



# Electric Current

- Electric current is the time rate of change of charge, measured in amperes (A).

$$i \triangleq \frac{dq}{dt}$$

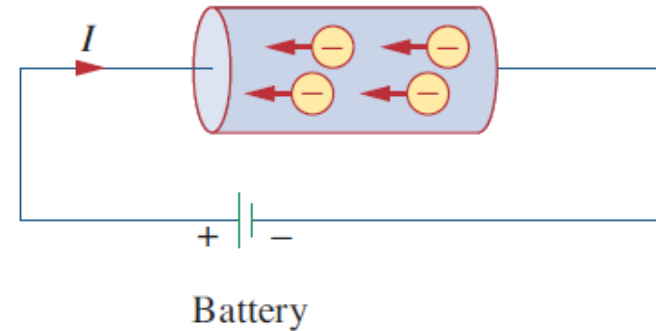

**Figure 1.3**

Electric current due to flow of electronic charge in a conductor.

- 1 ampere = 1 coulomb/second

# Electric Current





- The charge transferred between time and  $t$  is obtained by integrating both sides we obtain,

$$Q \triangleq \int_{t_0}^t i \, dt$$

# Electric Current

- Direct Current-DC
  - ✓ Current flows in one direction only.
  - ✓ Car Battery
  - ✓ Photovoltaic cells
- Alternating Current-AC
  - ✓ Current flows in one direction, then the other, and alternates back and forth.
  - ✓ This is what is used in one's home single phase.
  - ✓ Can be transformed

# Electric Current

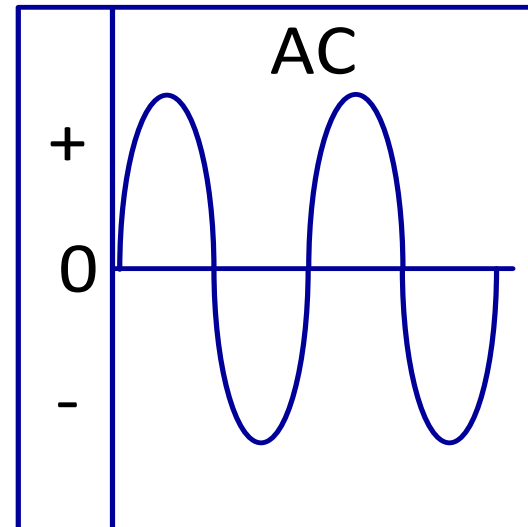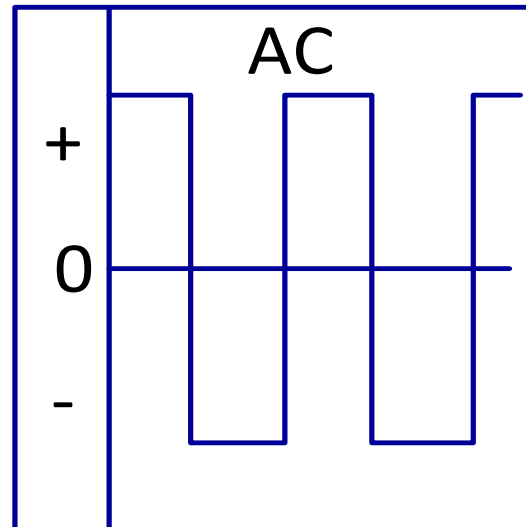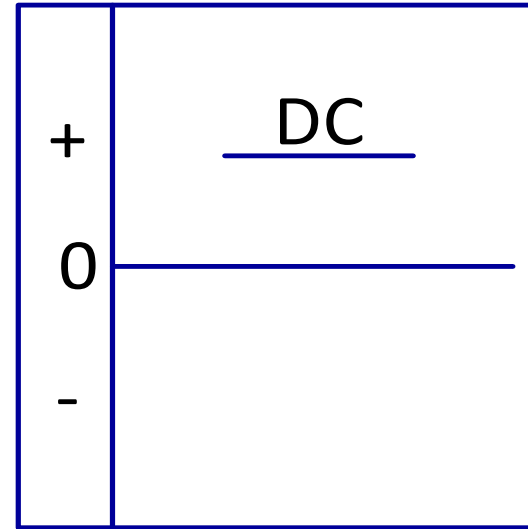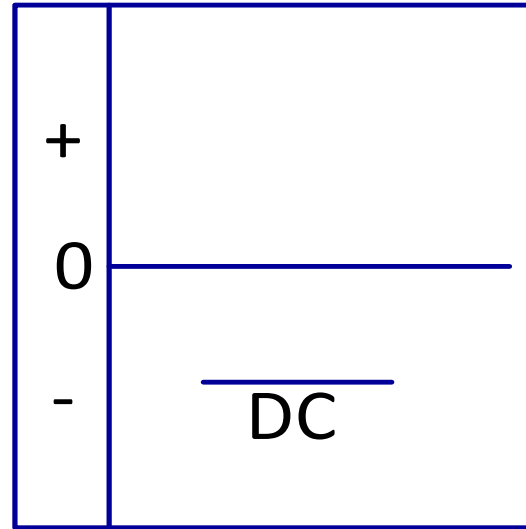

# Electric Current

## Example 1.2

The total charge entering a terminal is given by  $q = 5t \sin 4\pi t$  mC. Calculate the current at  $t = 0.5$  s.

# Electric Current

## Example 1.2

The total charge entering a terminal is given by  $q = 5t \sin 4\pi t$  mC. Calculate the current at  $t = 0.5$  s.

**Solution:**

$$i = \frac{dq}{dt} = \frac{d}{dt}(5t \sin 4\pi t) \text{ mC/s} = (5 \sin 4\pi t + 20\pi t \cos 4\pi t) \text{ mA}$$

At  $t = 0.5$ ,

$$i = 5 \sin 2\pi + 10\pi \cos 2\pi = 0 + 10\pi = 31.42 \text{ mA}$$

# Voltage


- The voltage  $V_{ab}$  between two points a and b in an electric circuit is the energy (or work) needed to move a unit charge from a to b; mathematically,

$$V_{ab} \triangleq \frac{dw}{dq}$$

- 1 volt = 1 joule/coulomb = 1 newton-meter/coulomb


# Voltage

- Voltage (or potential difference) is the energy required to move a unit charge through an element, measured in volts (V).

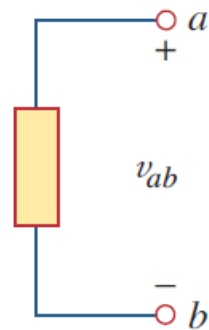

**Figure 1.6**

Polarity of voltage  $v_{ab}$ .

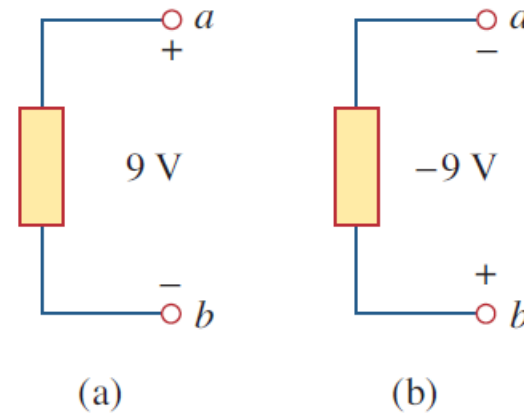

**Figure 1.7**


Two equivalent representations of the same voltage  $v_{ab}$ : (a) Point  $a$  is 9 V above point  $b$ ; (b) point  $b$  is -9 V above point  $a$ .



# Power and Energy

- Power is the time rate of expending or absorbing energy, measured in watts (W).

$$p \triangleq \frac{dw}{dt}$$

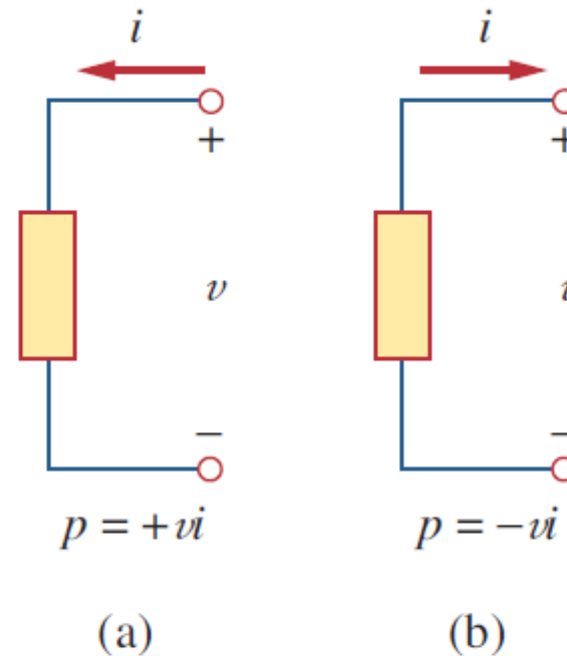


**Figure 1.8**

Reference polarities for power using the passive sign convention: (a) absorbing power, (b) supplying power.


# Power and Energy

- By the passive sign convention, current enters through the positive polarity of the voltage. In this case,  $p = +vi$  or  $p = vi > 0$  implies that the element is absorbing power.
- However, if  $p = -vi$  or  $vi < 0$  or, as in Fig. 1.8(b), the element is releasing or supplying power.

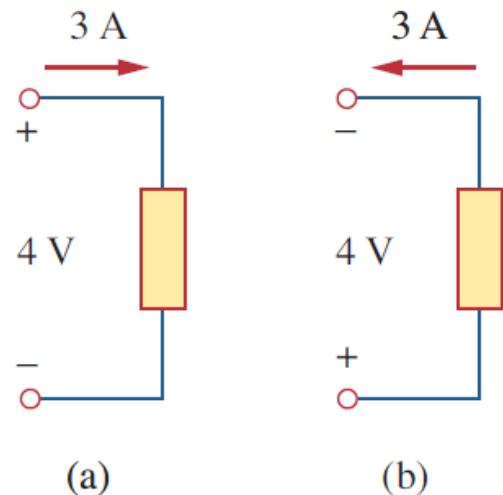

**Figure 1.9**

Two cases of an element with an absorbing power of 12 W: (a)  $p = 4 \times 3 = 12$  W, (b)  $p = 4 \times 3 = 12$  W.

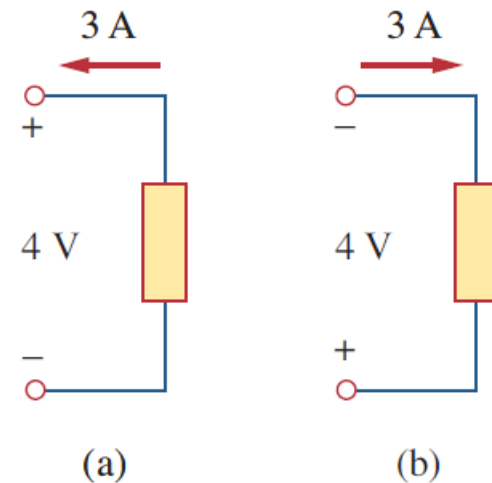

**Figure 1.10**

Two cases of an element with a supplying power of 12 W: (a)  $p = -4 \times 3 = -12$  W, (b)  $p = -4 \times 3 = -12$  W.

# Power and Energy

- The law of conservation of energy must be obeyed in any electric circuit.
- For this reason, the algebraic sum of power in a circuit, at any instant of time, must be zero:

$$\sum p = 0$$

$$w = \int_{t_0}^t p \, dt = \int_{t_0}^t vi \, dt$$

# Power and Energy

- Energy is the capacity to do work, measured in joules (J).
- The electric power utility companies measure energy in watt-hours (Wh), where-

$$1 \text{ Wh} = 3,600 \text{ J}$$

# Power and Energy

Find the power delivered to an element at  $t = 3$  ms if the current entering its positive terminal is

$$i = 5 \cos 60\pi t \text{ A}$$

and the voltage is: (a)  $v = 3i$ , (b)  $v = 3 \, di/dt$ .

# Power and Energy

## **Solution:**

(a) The voltage is  $v = 3i = 15 \cos 60\pi t$ ; hence, the power is

$$p = vi = 75 \cos^2 60\pi t \text{ W}$$

At  $t = 3 \text{ ms}$ ,

$$p = 75 \cos^2 (60\pi \times 3 \times 10^{-3}) = 75 \cos^2 0.18\pi = 53.48 \text{ W}$$

(b) We find the voltage and the power as

$$v = 3 \frac{di}{dt} = 3(-60\pi)5 \sin 60\pi t = -900\pi \sin 60\pi t \text{ V}$$

$$p = vi = -4500\pi \sin 60\pi t \cos 60\pi t \text{ W}$$

At  $t = 3 \text{ ms}$ ,

$$\begin{aligned} p &= -4500\pi \sin 0.18\pi \cos 0.18\pi \text{ W} \\ &= -14137.167 \sin 32.4^\circ \cos 32.4^\circ = -6.396 \text{ kW} \end{aligned}$$

# Circuit Elements

- An electric circuit is simply an interconnection of the elements.
- Two types of elements in electric circuits:
  - ✓ *Passive elements* = resistors, capacitors, and inductors
  - ✓ *active elements* = generators, batteries, and operational amplifiers
- An active element is capable of generating energy while a passive element is not.


# Circuit Elements

- The most important active elements are voltage or current sources that generally deliver power to the circuit connected to them.
- There are two kinds of sources: independent and dependent sources.




# Circuit Elements

- **Independent Sources-** An ideal independent source is an active element that provides a specified voltage or current that is completely independent of other circuit elements.

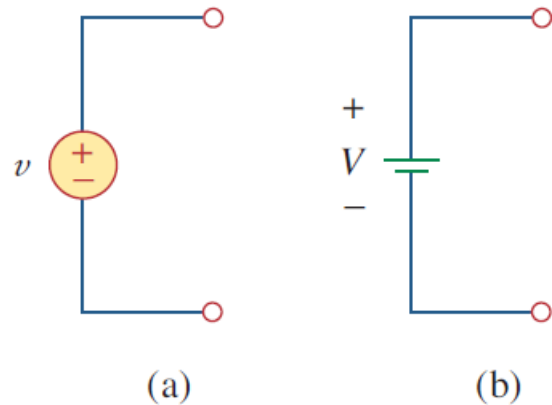

**Figure 1.11**

Symbols for independent voltage sources:  
(a) used for constant or time-varying voltage, (b) used for constant voltage (dc).

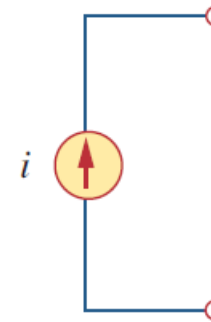


**Figure 1.12**

Symbol for independent current source.

# Circuit Elements

- **Dependent Sources-** An ideal dependent (or controlled) source is an active element in which the source quantity is controlled by another voltage or current.

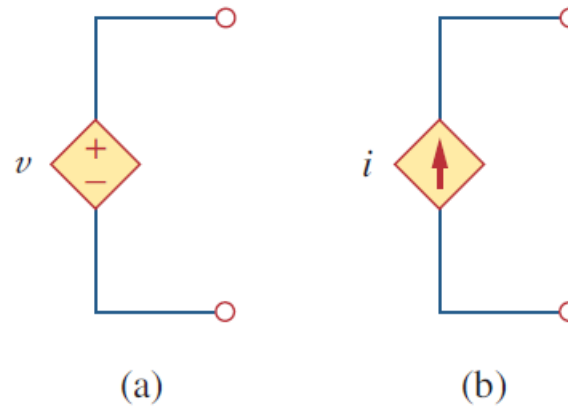

**Figure 1.13**


Symbols for: (a) dependent voltage source, (b) dependent current source.

# Circuit Elements

There are four possible types of dependent sources, namely:

- i. A voltage-controlled voltage source (VCVS).
- ii. A current-controlled voltage source (CCVS).
- iii. A voltage-controlled current source (VCCS).
- iv. A current-controlled current source (CCCS).

# Circuit Elements

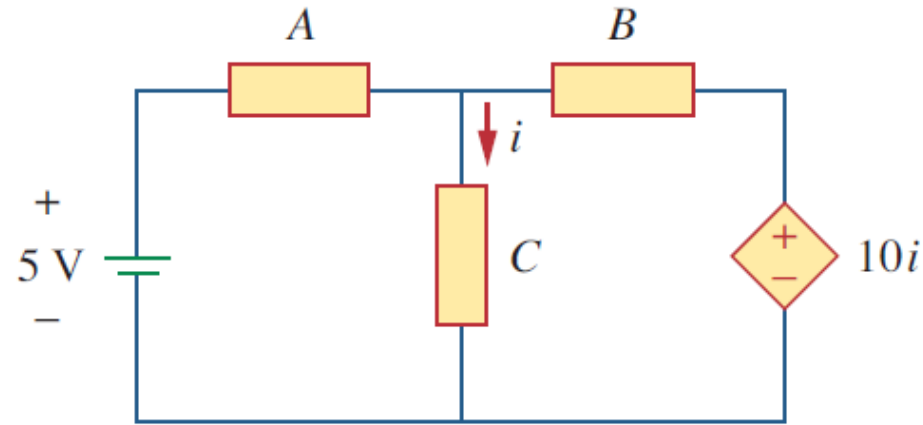


**Figure 1.14**

The source on the right-hand side is a current-controlled voltage source.

# Circuit Elements

Calculate the power supplied or absorbed by each element in Fig. 1.15.

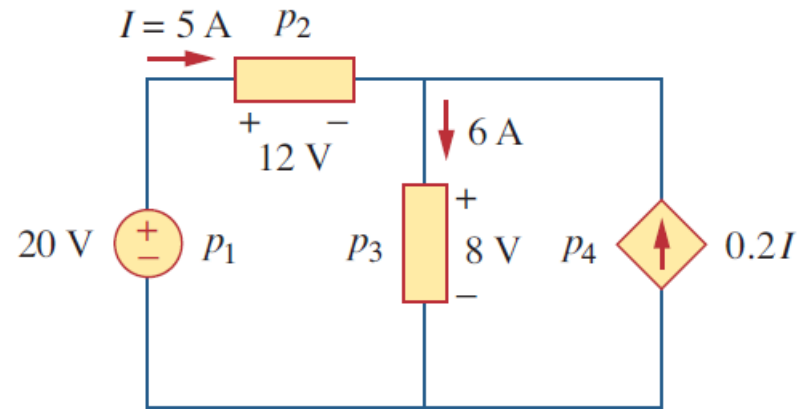

**Figure 1.15**  
For Example 1.7.

# Circuit Elements

## **Solution:**

We apply the sign convention for power shown in Figs. 1.8 and 1.9. For  $p_1$ , the 5-A current is out of the positive terminal (or into the negative terminal); hence,

$$p_1 = 20(-5) = -100 \text{ W} \quad \text{Supplied power}$$

For  $p_2$  and  $p_3$ , the current flows into the positive terminal of the element in each case.

$$p_2 = 12(5) = 60 \text{ W} \quad \text{Absorbed power}$$

$$p_3 = 8(6) = 48 \text{ W} \quad \text{Absorbed power}$$

# Circuit Elements

$$p_4 = 8(-0.2I) = 8(-0.2 \times 5) = -8 \text{ W} \quad \text{Supplied power}$$

We should observe that the 20-V independent voltage source and  $0.2I$  dependent current source are supplying power to the rest of the network, while the two passive elements are absorbing power. Also,

$$p_1 + p_2 + p_3 + p_4 = -100 + 60 + 48 - 8 = 0$$