

Sheikh Hasina University, Netrokona
Department of Computer Science and Engineering
CSE-2205: Introduction to Mechatronics

Lec-24: Programmable Logic Controller (PLC)


Mechatronics: Electronic Control Systems in Mechanical Engineering by W. Bolton

Md. Ariful Islam
Assistant Professor
Dept. of Robotics and Mechatronics Engineering
University of Dhaka
&
Adjunct Faculty
Sheikh Hasina University, Netrokona
Department of Computer Science and Engineering


Logic functions

(A)	(B)	
0	0	✓
1	0	✓
0	1	✓
1	1	✓

NC

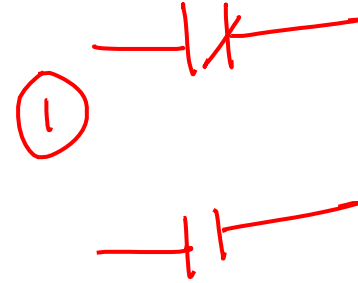


NO


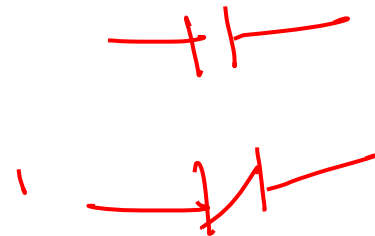


1) AND

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


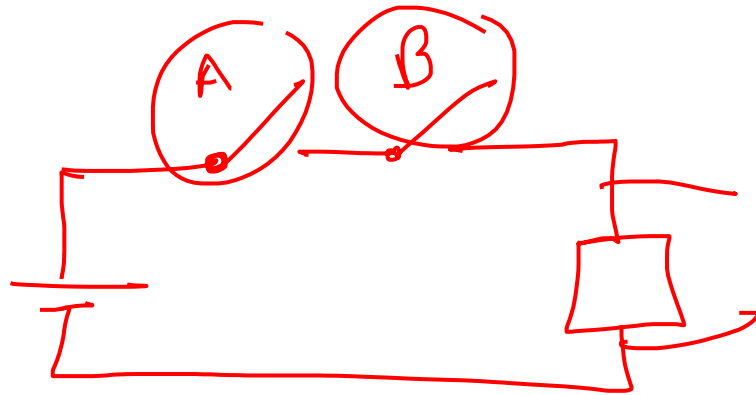


Ladder:

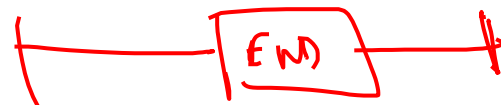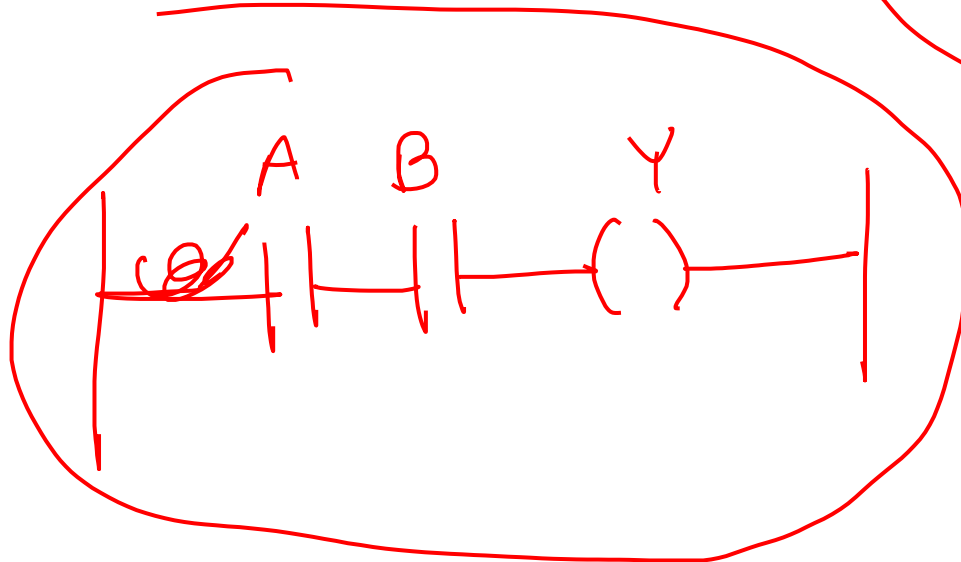


2) OR:

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

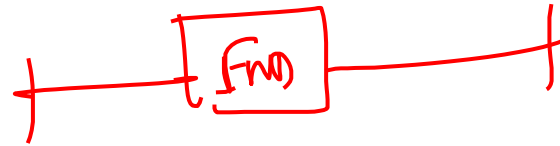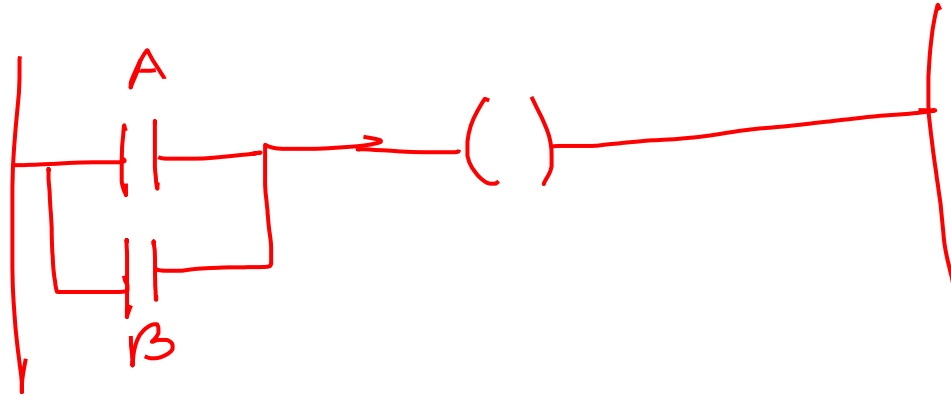


3) NOT


A	Y
0	1
1	0

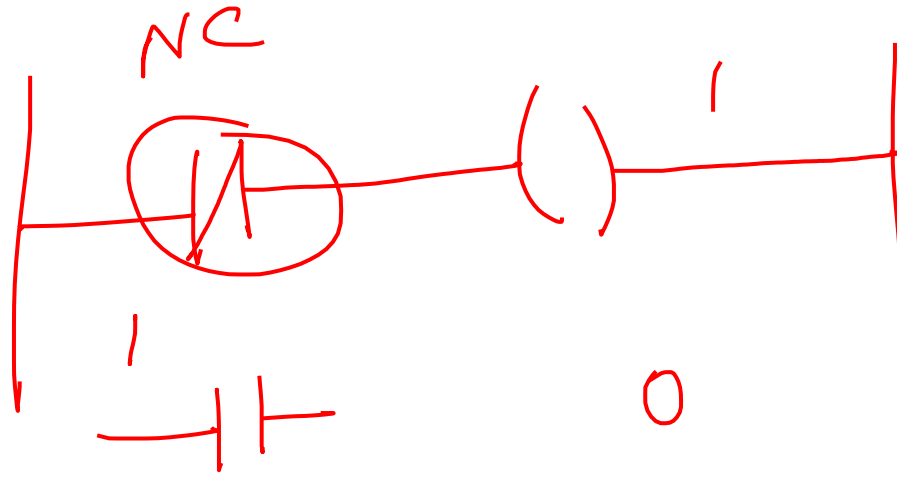

4) NAND:


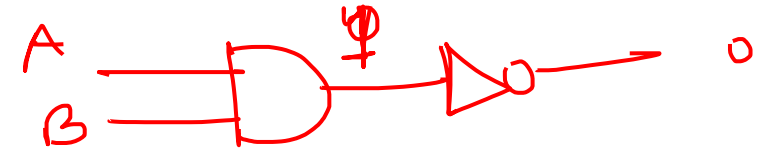


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

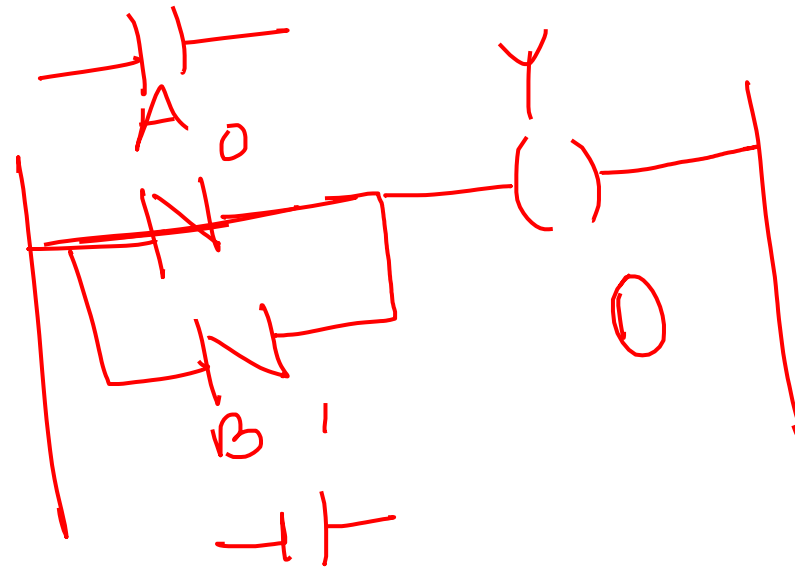

5) NOR:


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

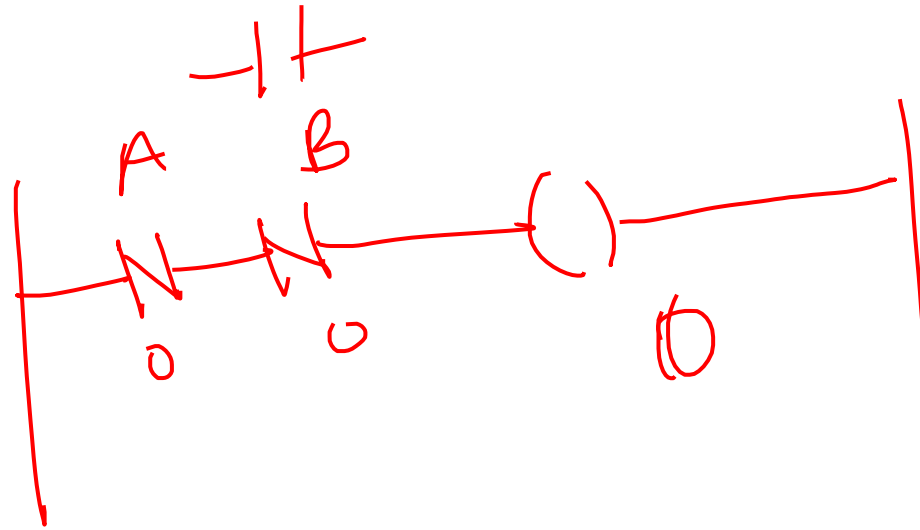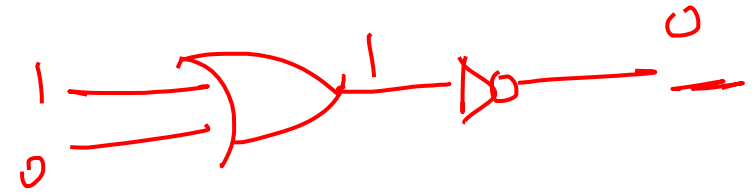



6) EX-OR:

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

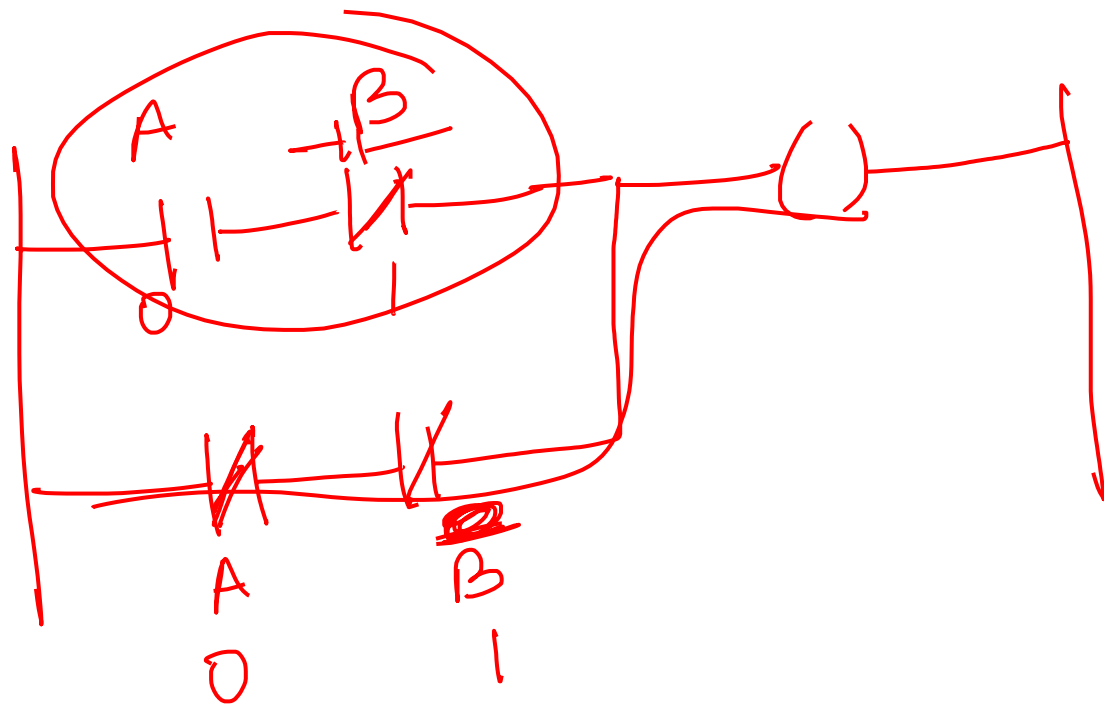
$$SOP = \underline{\underline{\overline{A}B}} + \underline{\underline{A\overline{B}}}$$




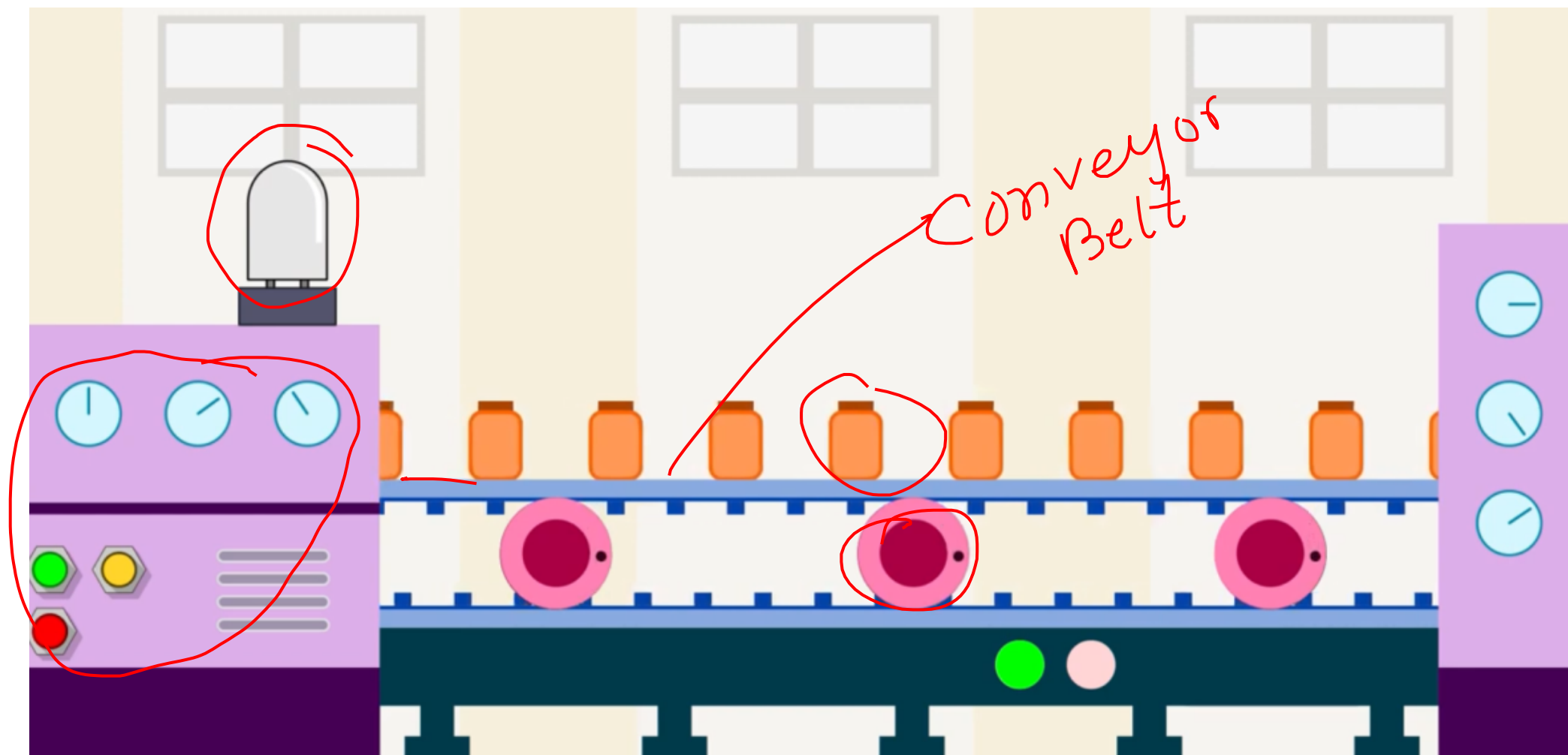

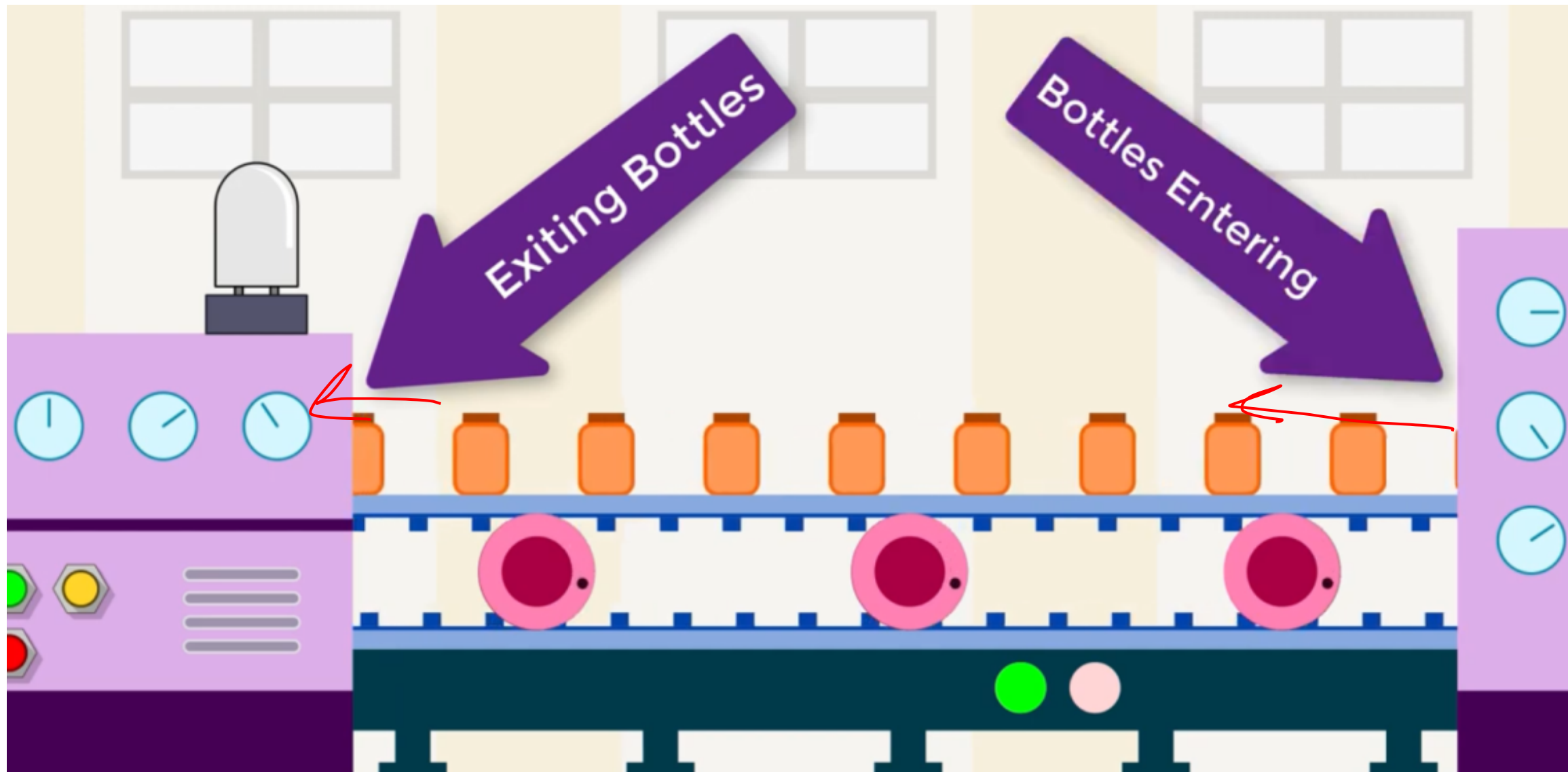

Implementing Automation

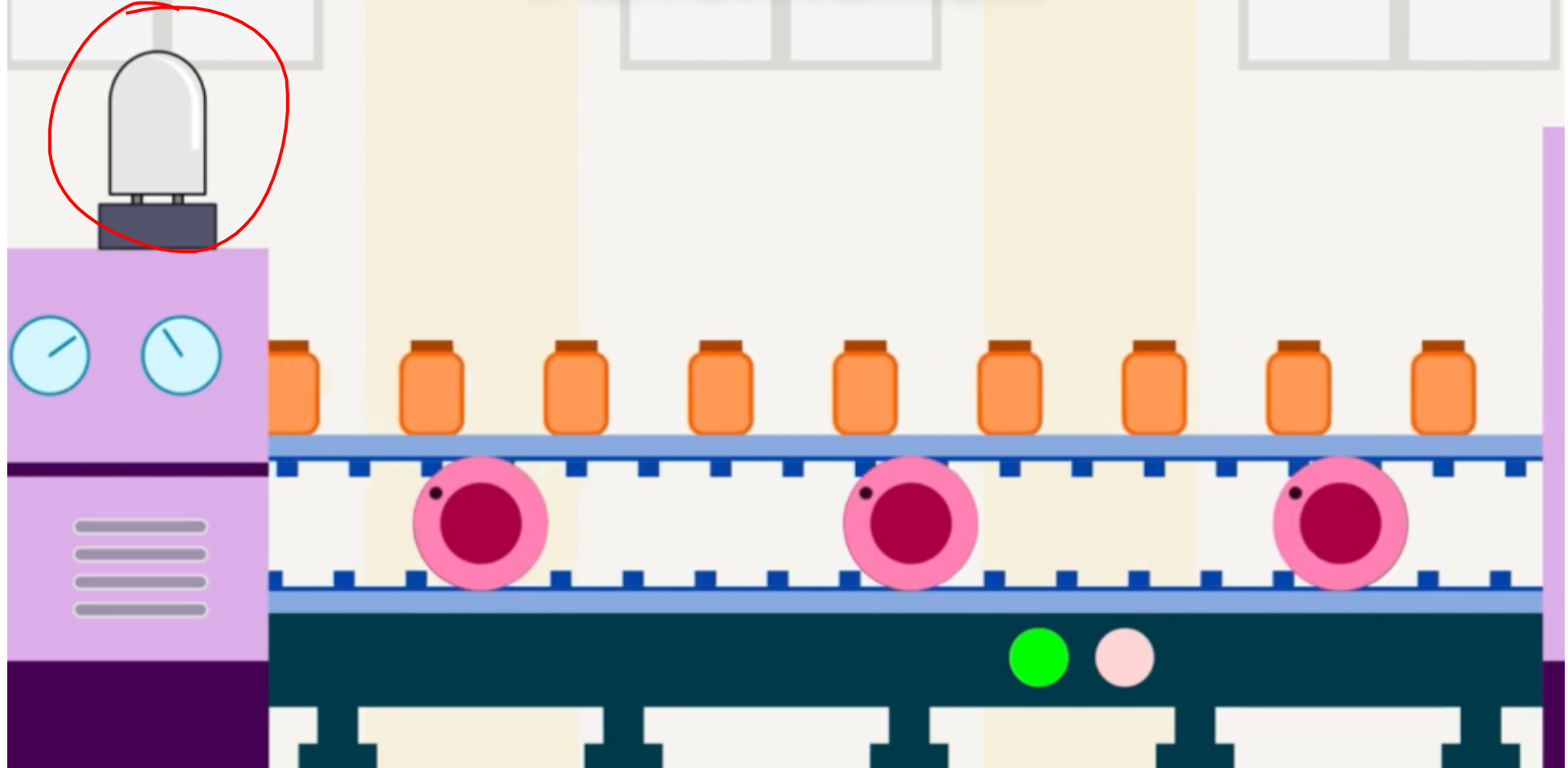

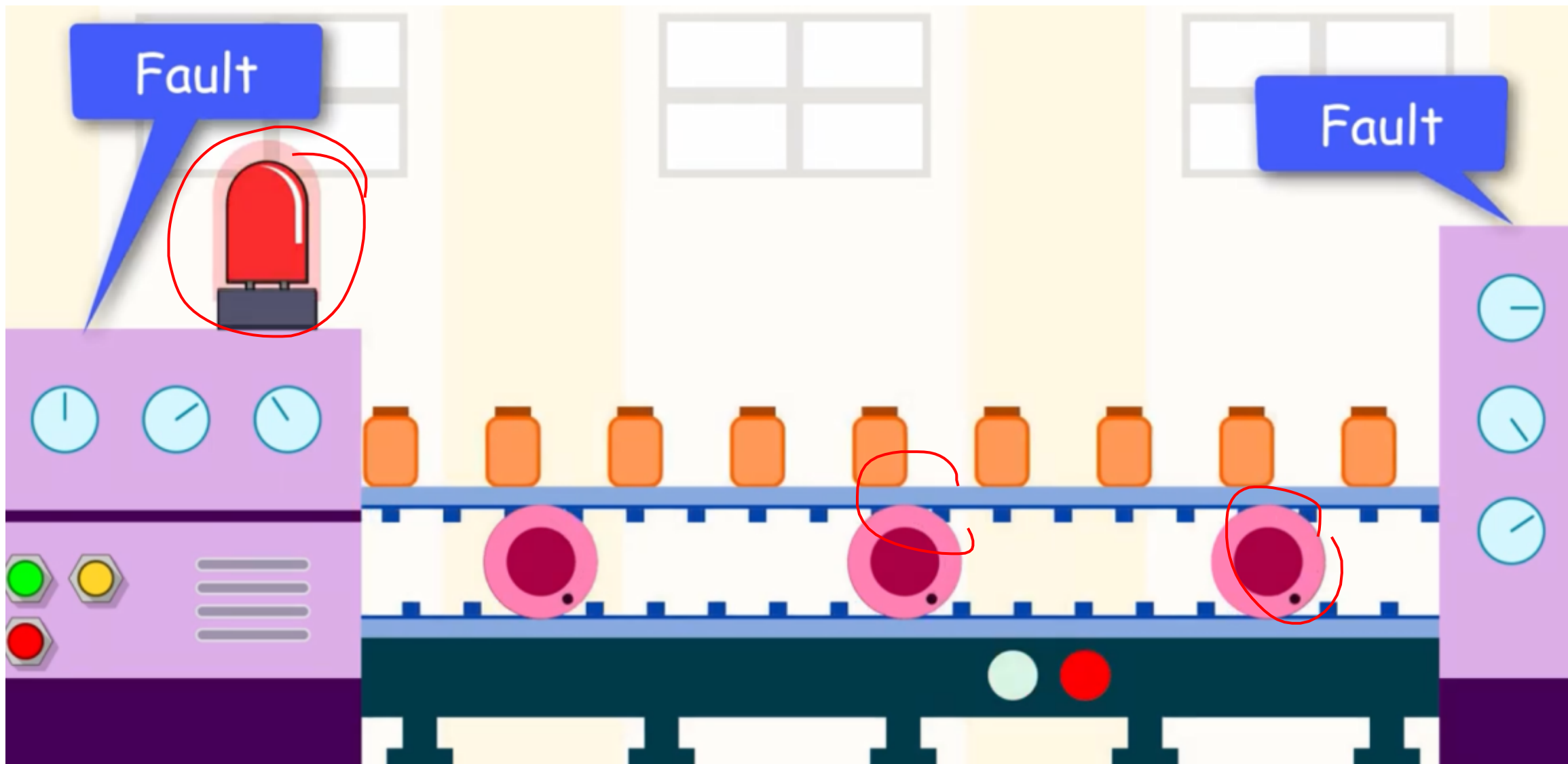


2 Inputs

Machine
Running Status


Machine
Running Status


I1


I2

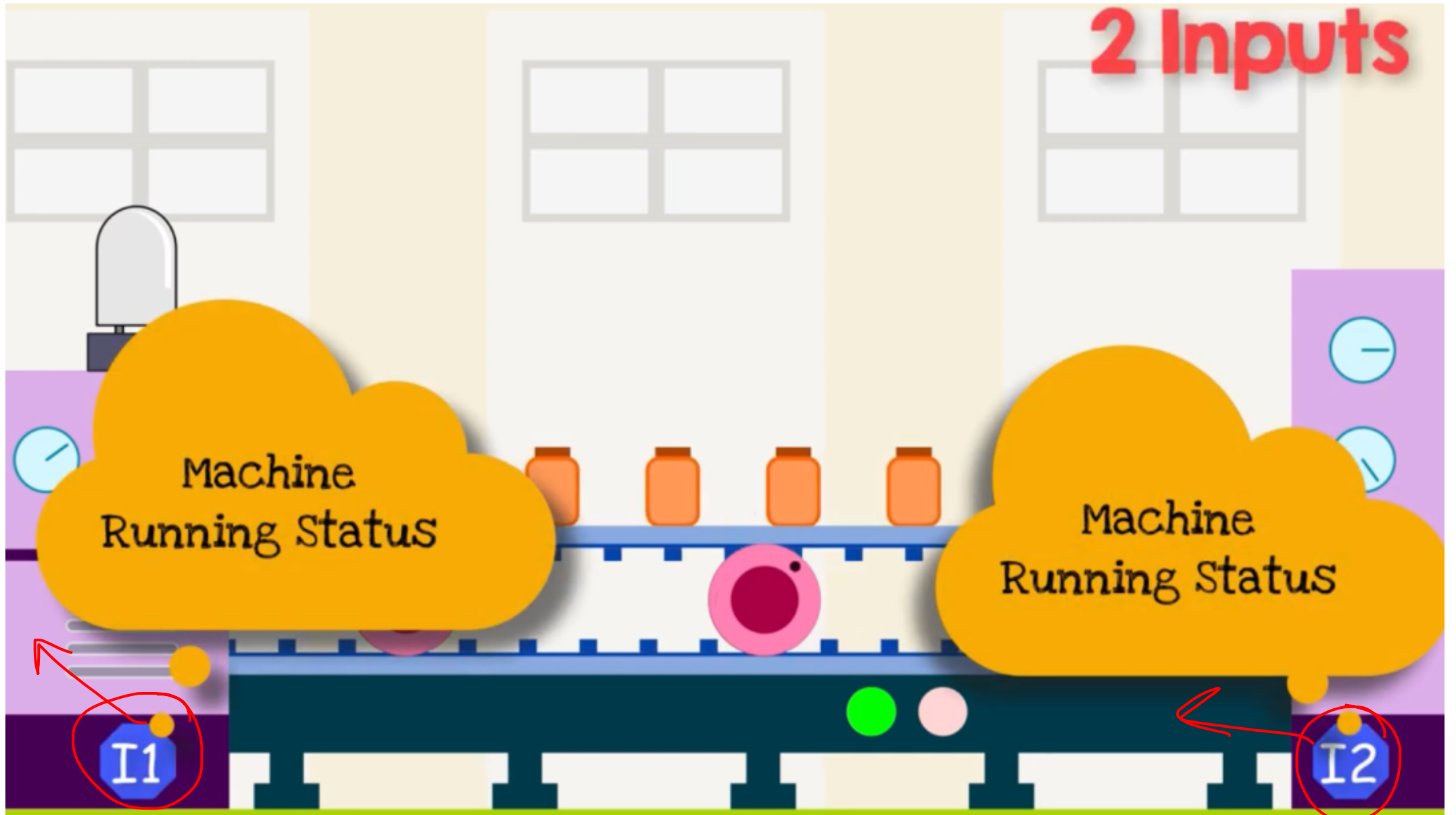


2 Inputs
2 Outputs

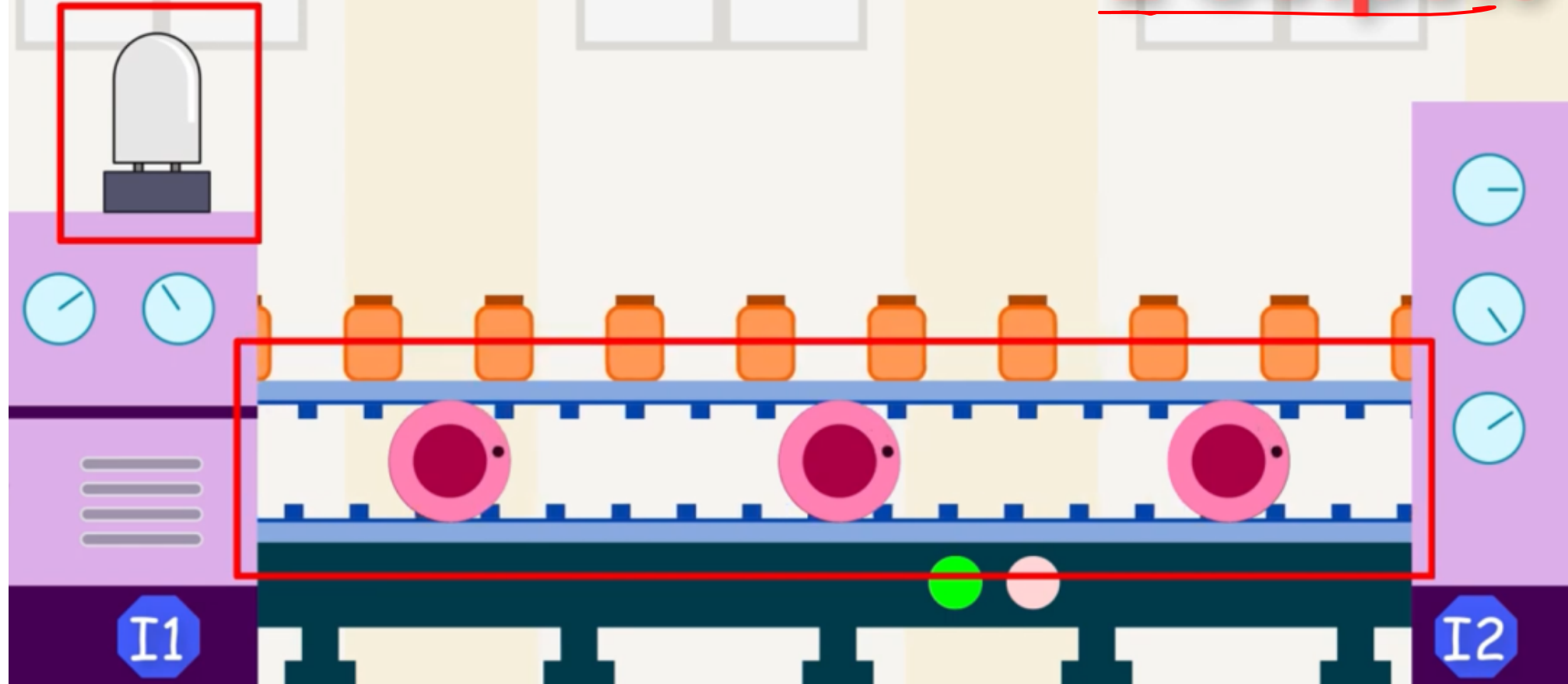

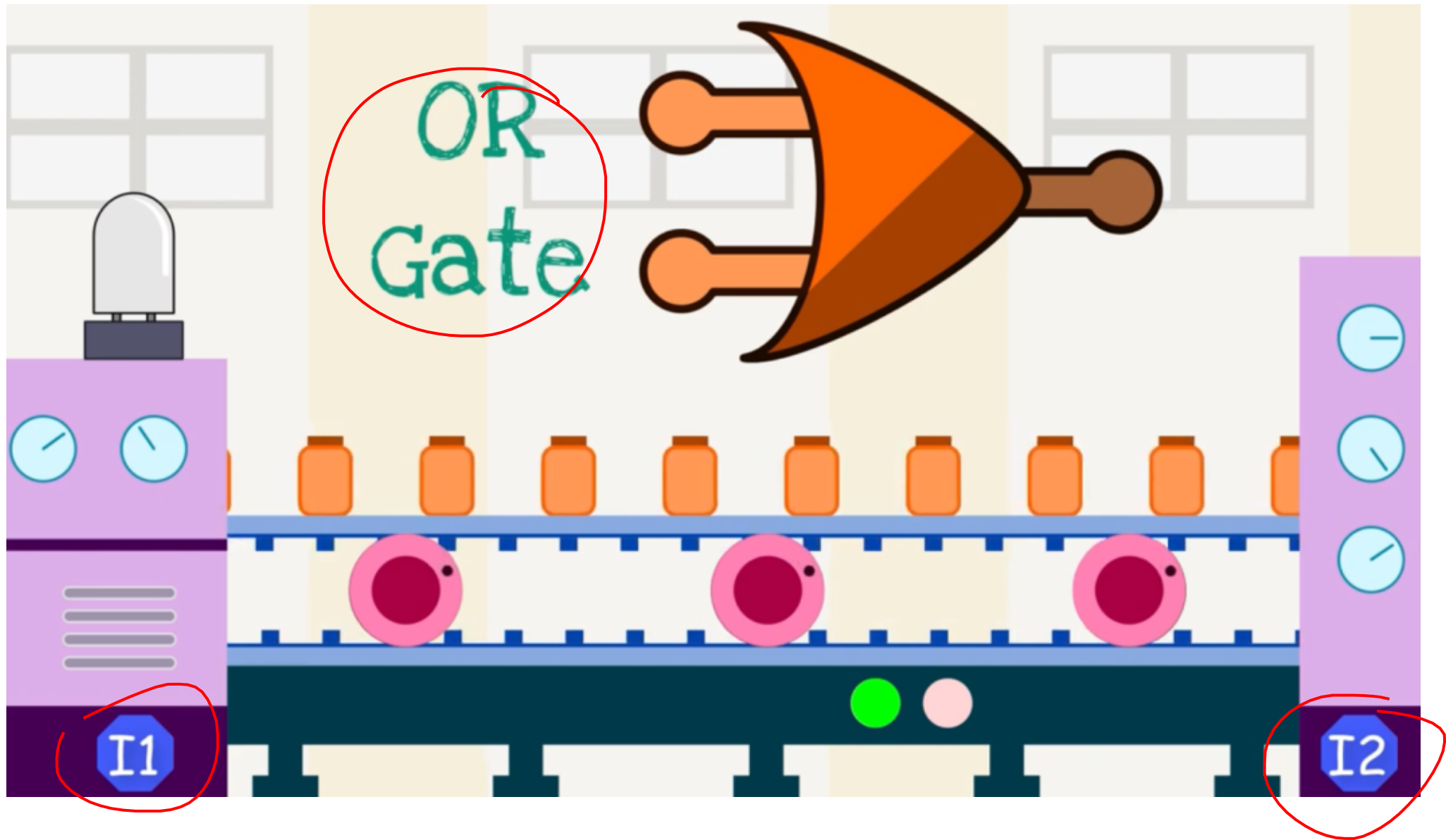


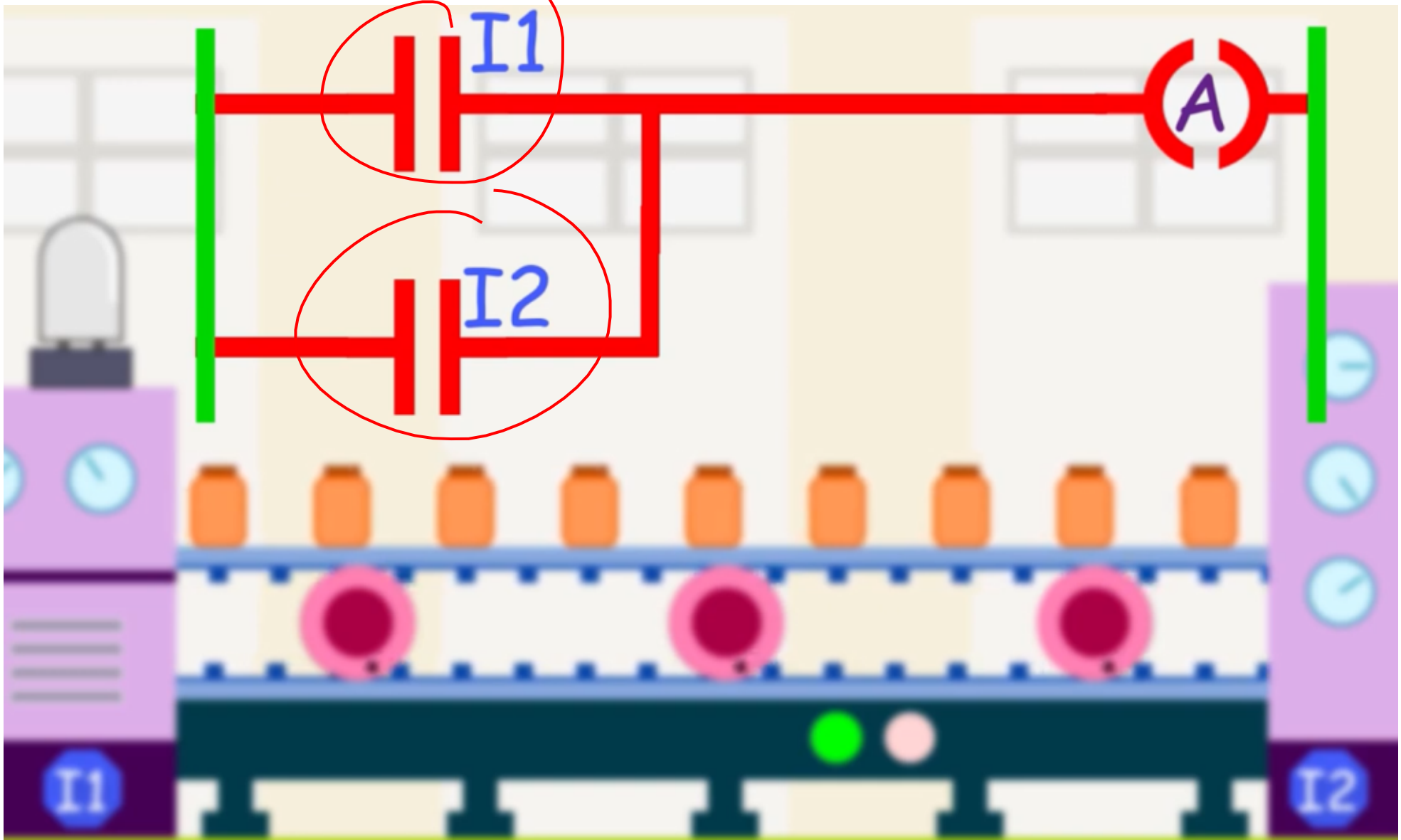


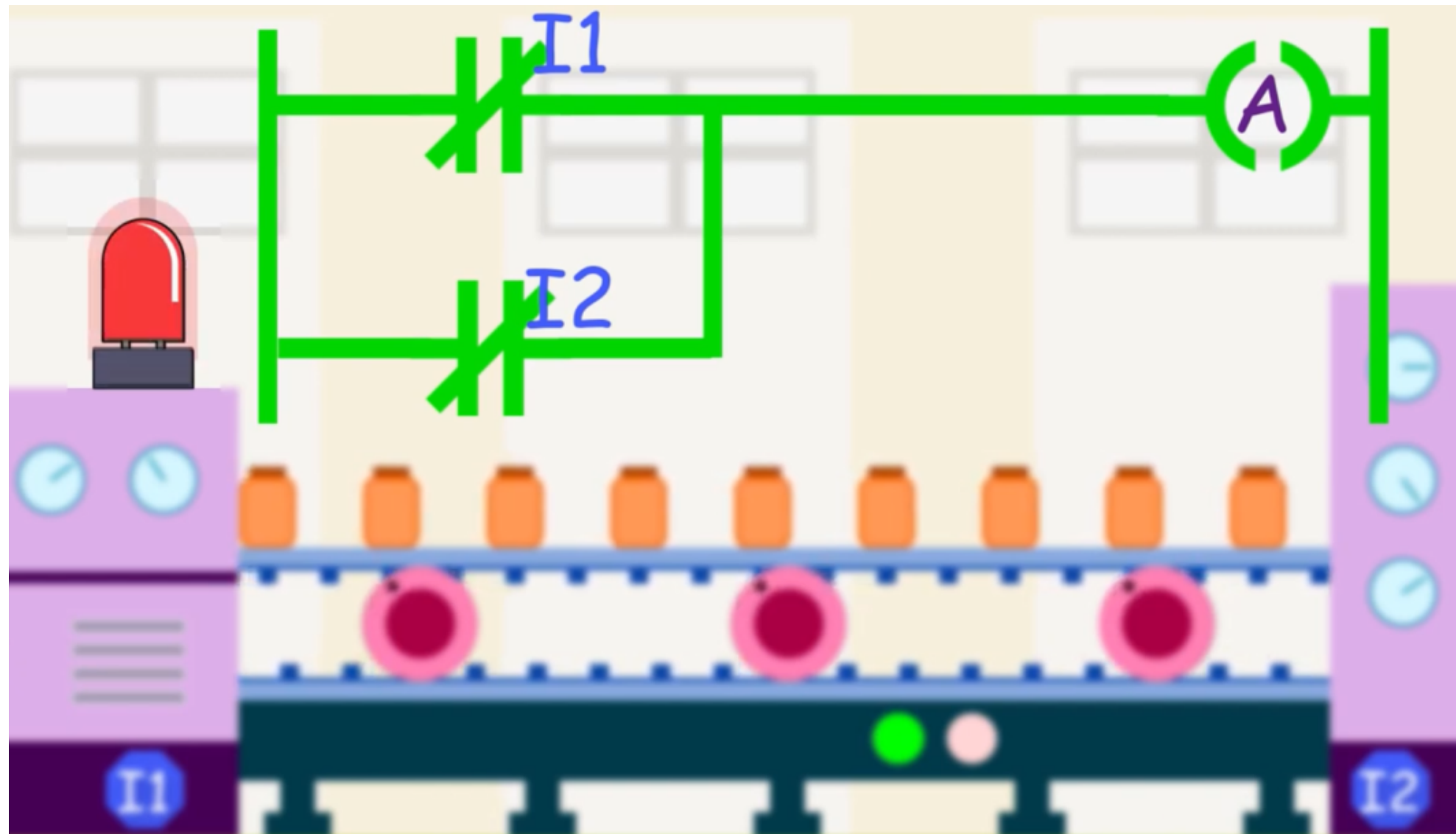

$$1) Y = (A+B).(C+D)$$



$$1) Y = (A+B) \cdot (C+D)$$

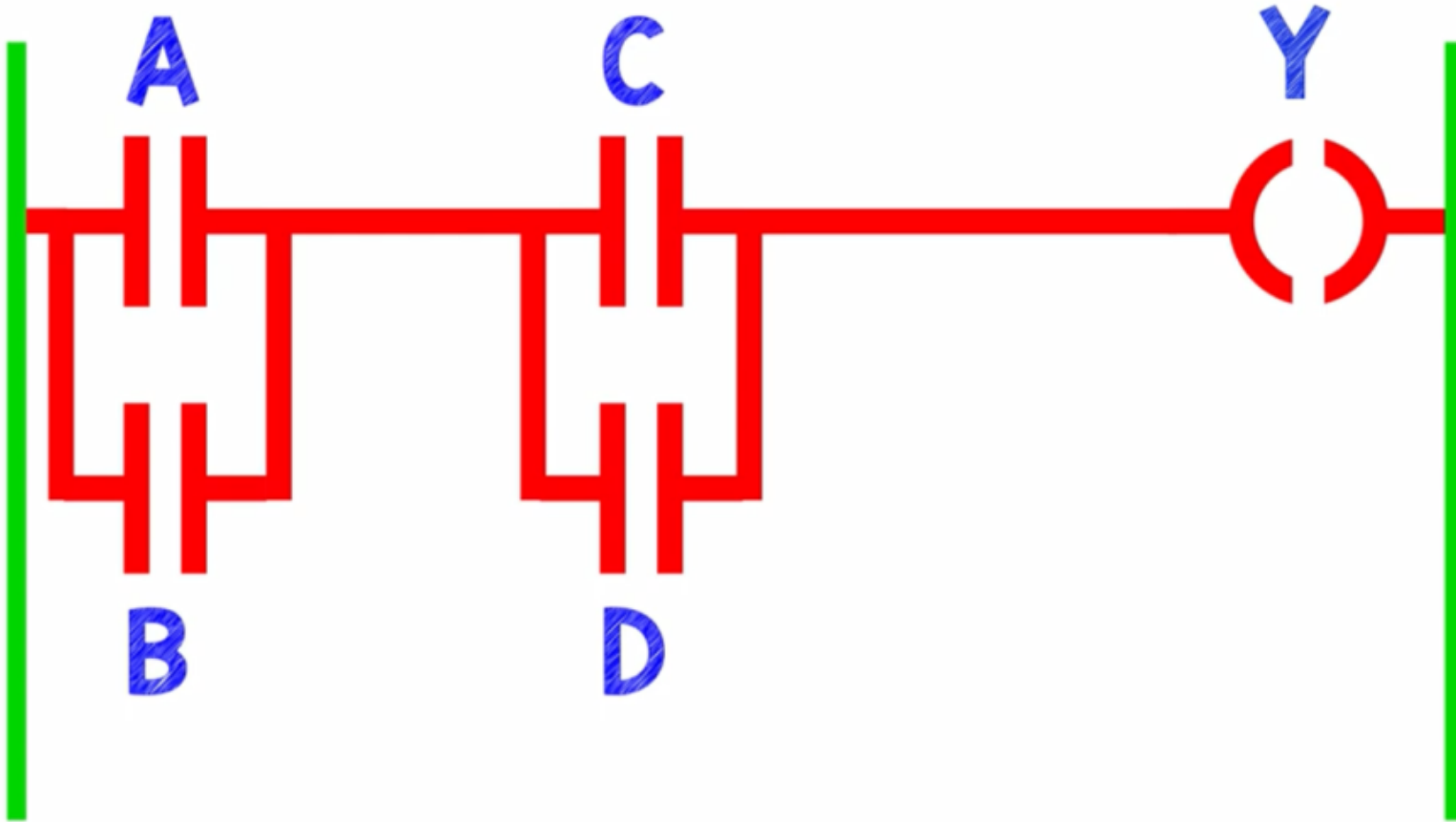

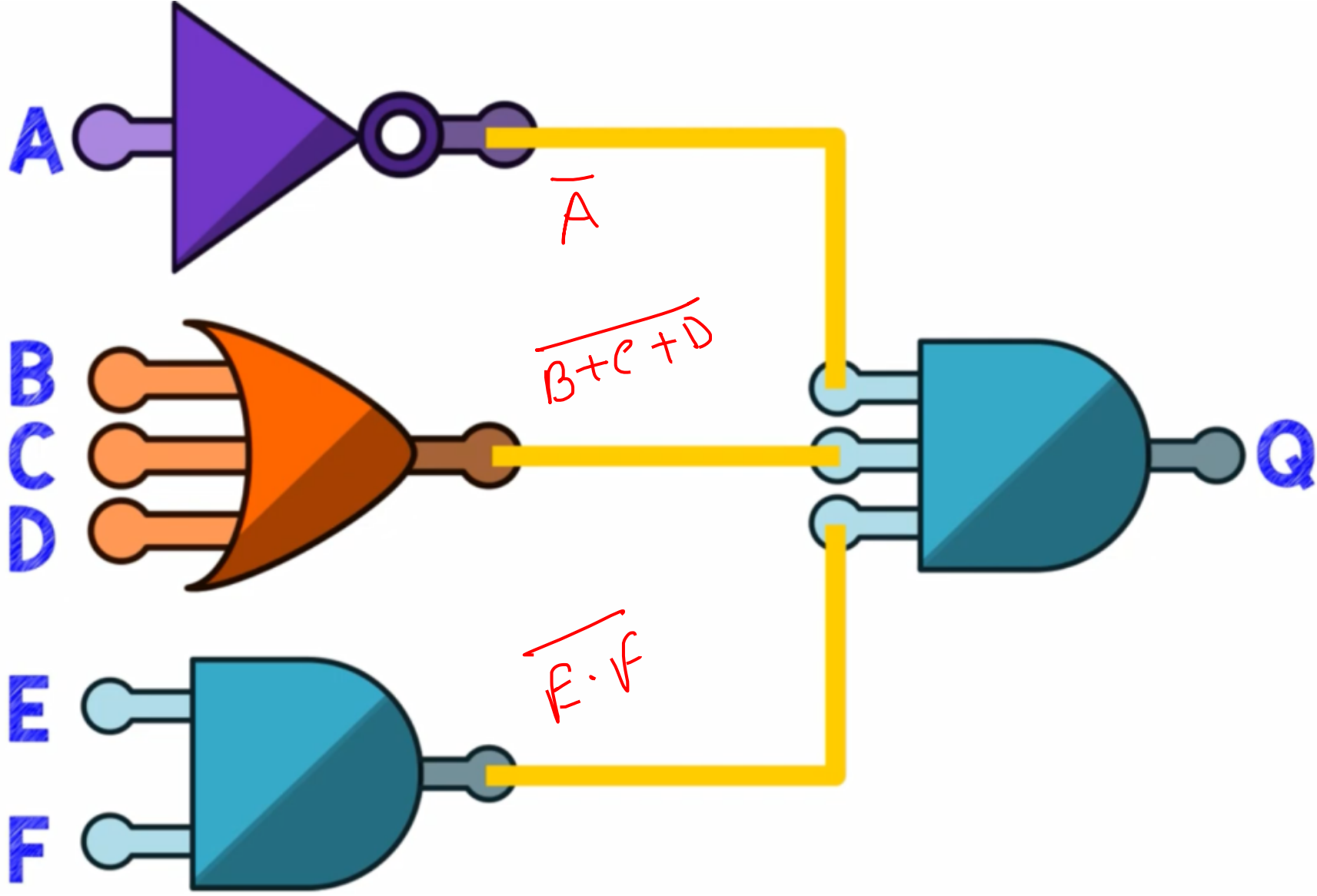

$$Q = \bar{A} \cdot (B + C + D) \cdot (E \cdot F)$$

$$Q = \bar{A} (B + C + D) (E \cdot F)$$

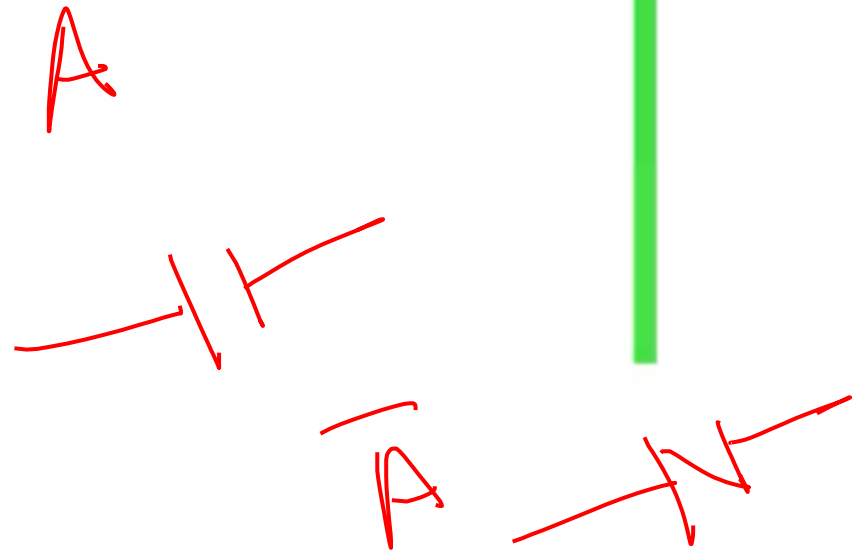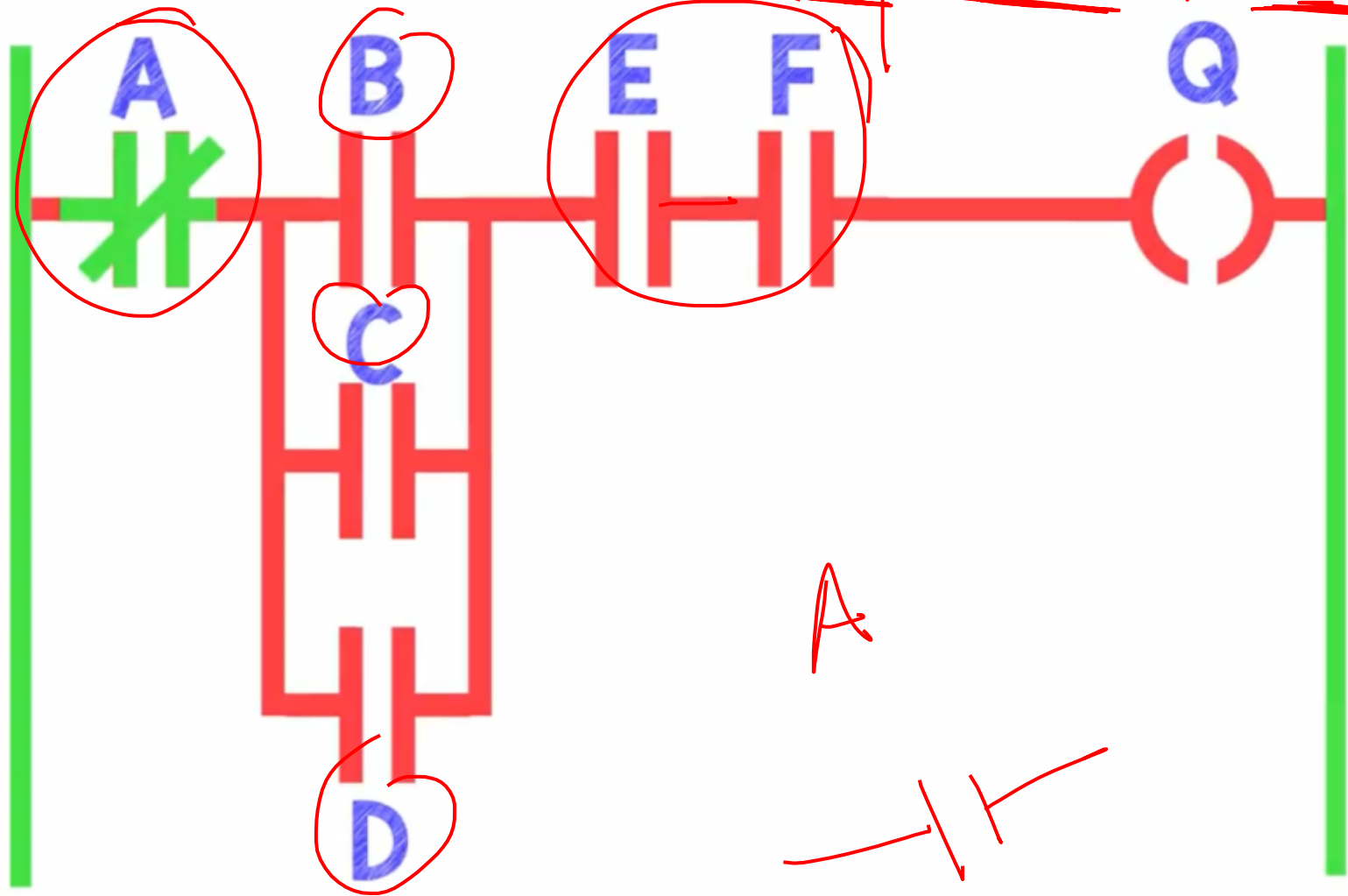


$$Q = \underline{A} + \underline{(B \oplus C)}$$

XOR


$$Q = A + (B \oplus C) \\ = \textcircled{A} + X$$

$$Q = A + X$$

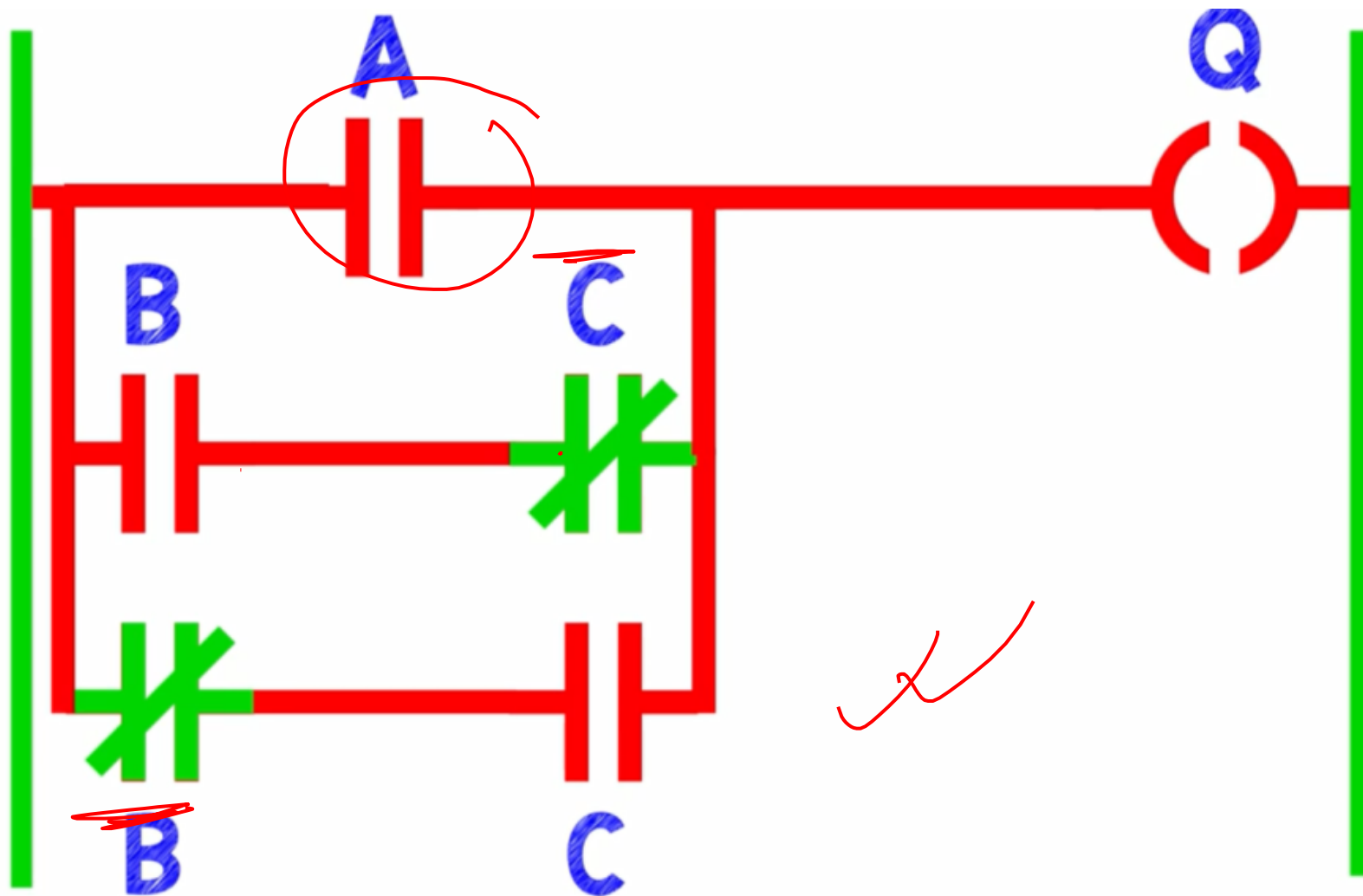
$$X = \underline{B\bar{C}} + \underline{\bar{B}C}$$



Latching:

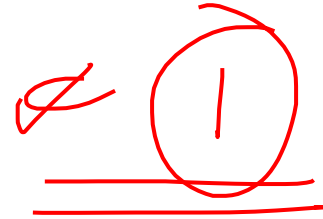



Self-maintaining ckt:

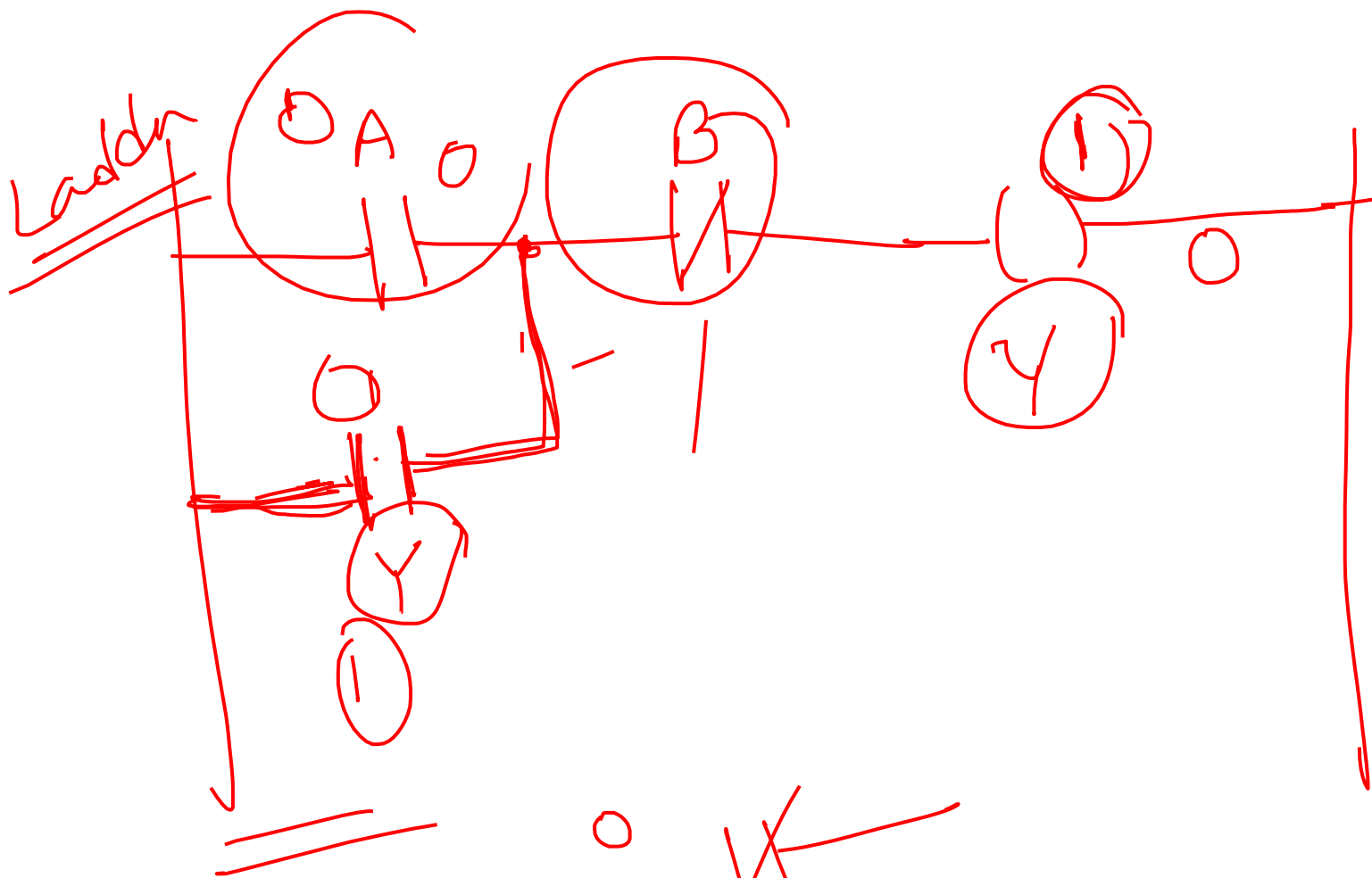


sequence


A	B	Y
1	0	1
0	0	1
0	1	0

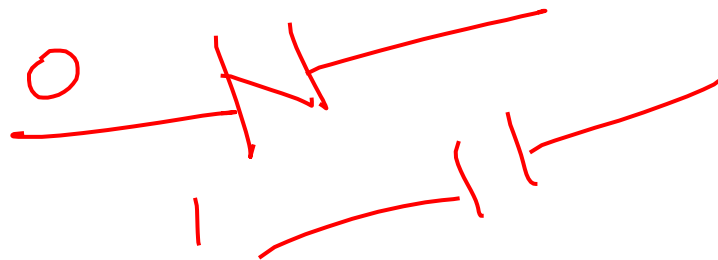

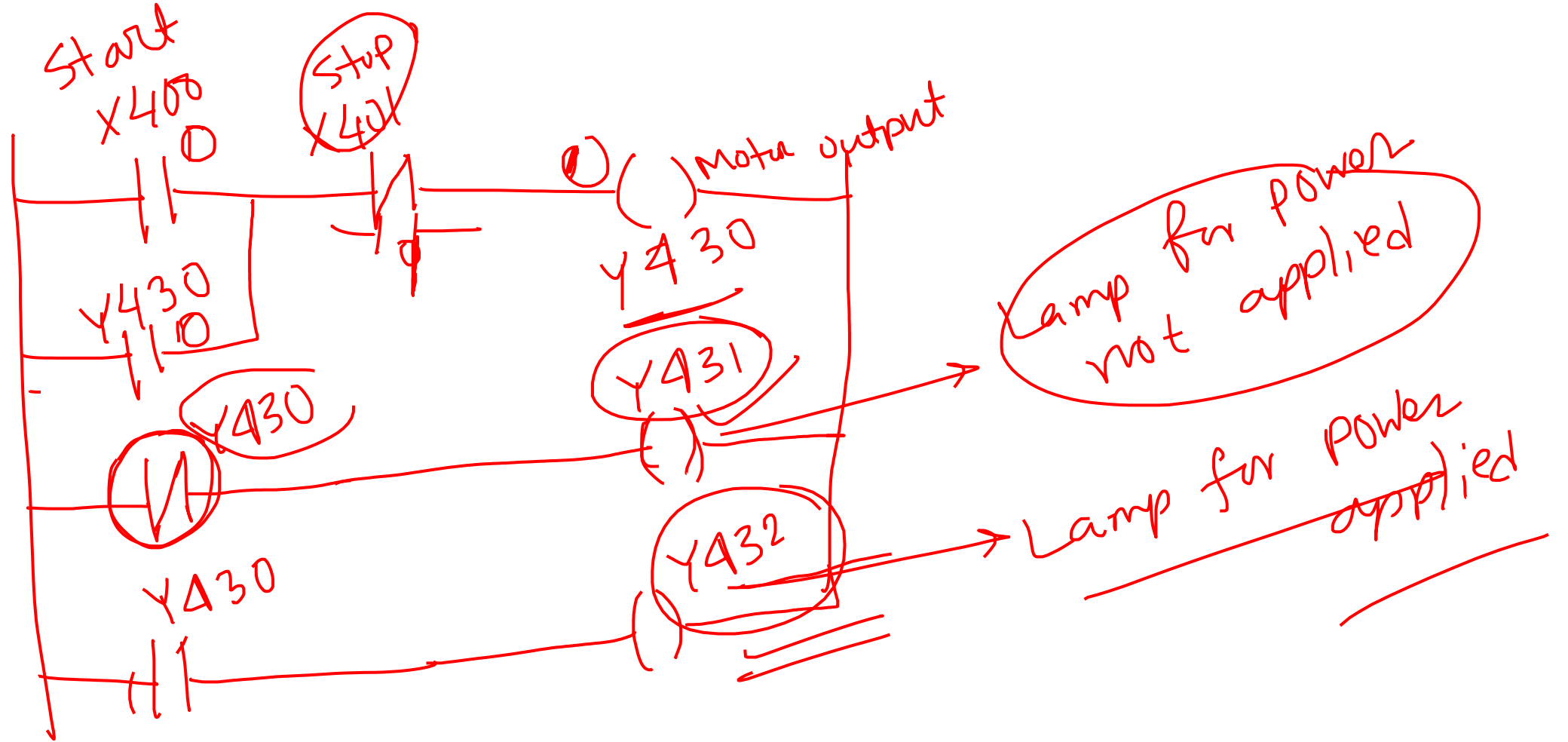


Multiple outputs:

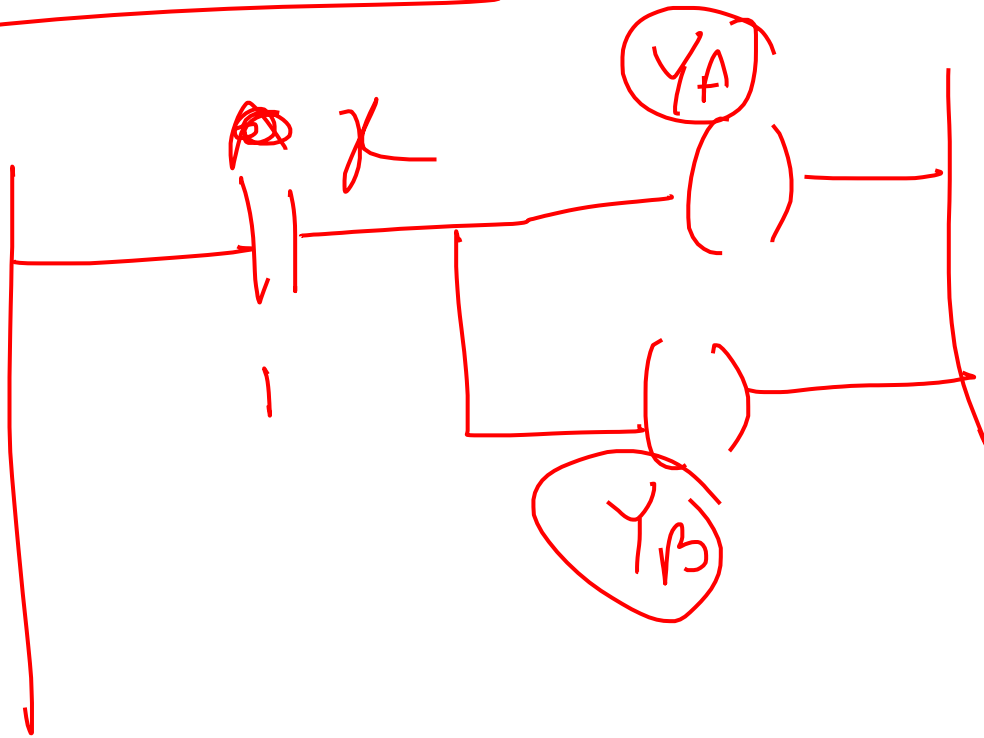

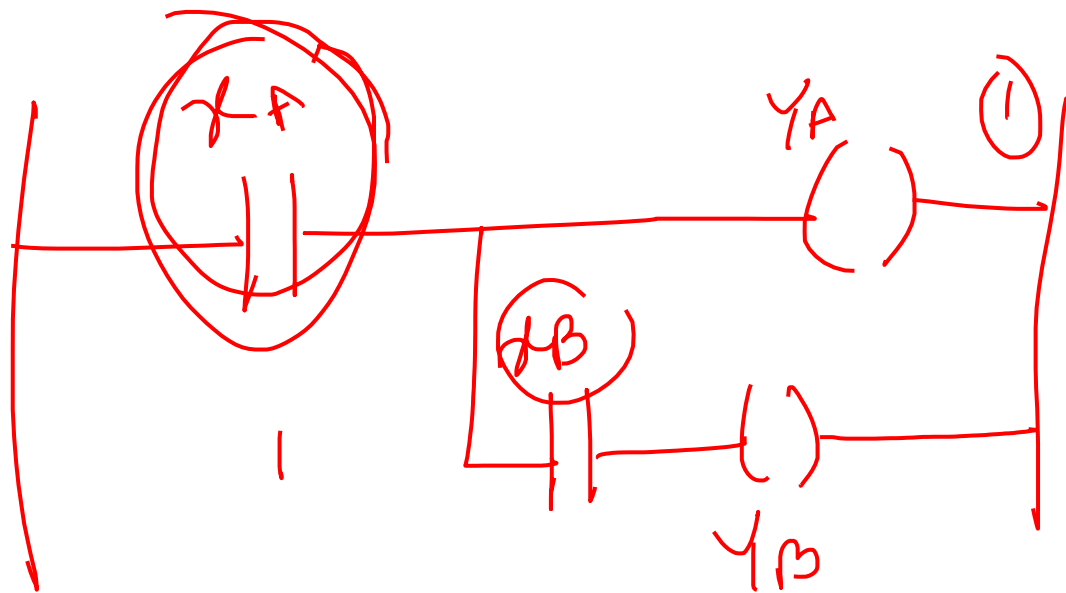

x_A	x_B	y_A	y_B
(1)	0	1	0
(0)	1	0	0

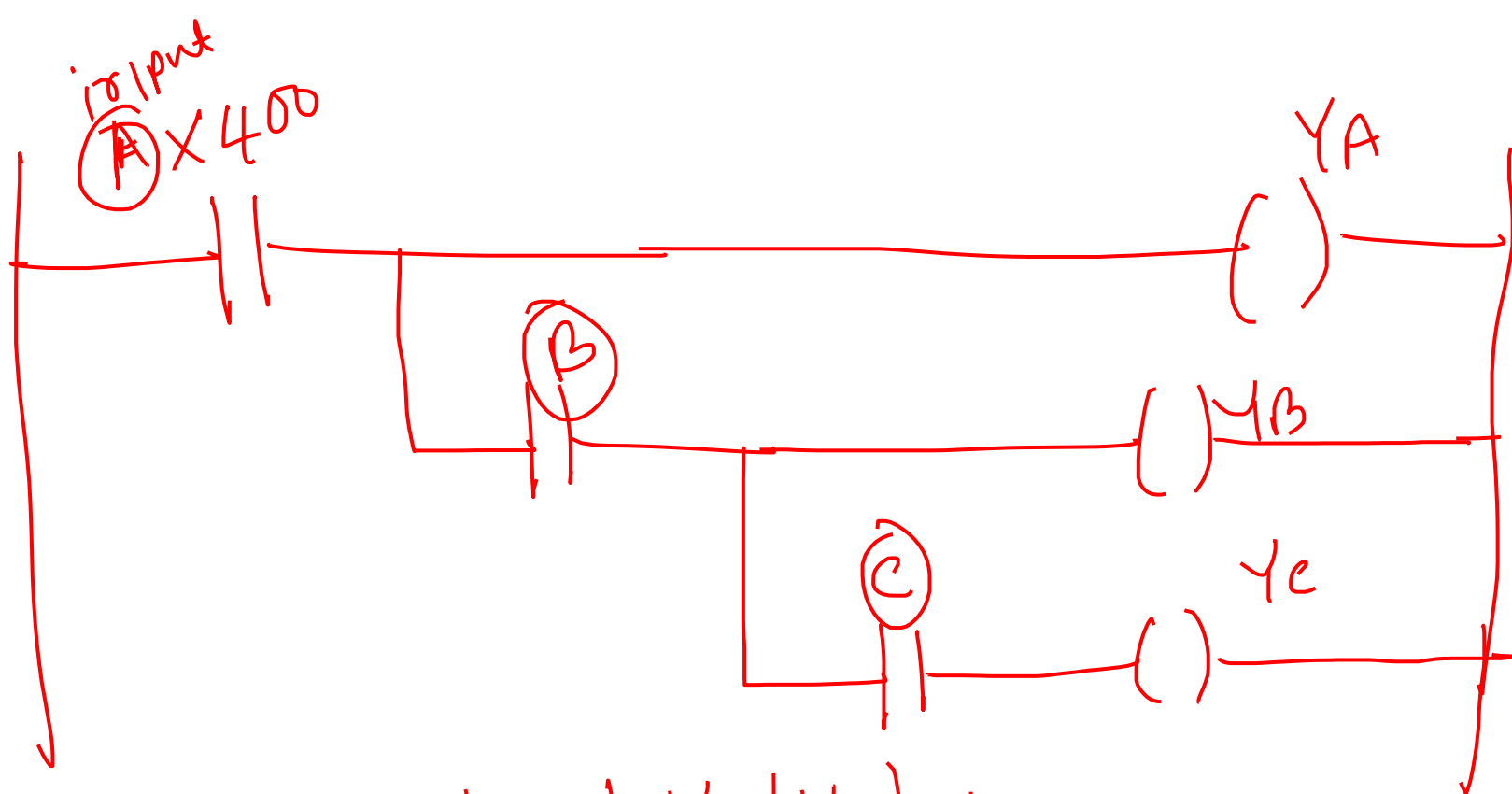

X_A	X_B	X_C	Y_A	Y_B	Y_C
1	0	0	1	0	0
1	1	0	1	1	0