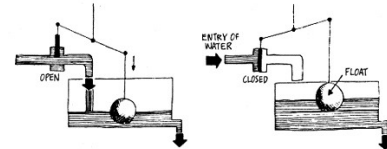


# Feedback Techniques and Op-amps

## Concept of feedback

### Valve example




- As the water nears the specified level, the valve is closed.
- Negative feedback is most commonly used to control systems.

2
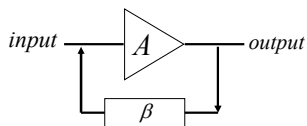
## Types of feedback

What is feedback?

- Feedback is a technique where a proportion of the output of a system (amplifier) is **fed back** and **recombined** with input.




- There are two types of feedback amplifier.
  - **Positive feedback**
  - **Negative feedback**

3

## Types of feedback..
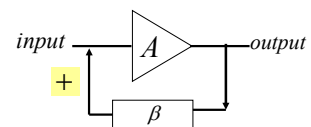
### 1. Positive Feedback

- Positive feedback is the process when the output is **added** to the input, amplified again, and this process continues.




- **Example:** In a PA system, you get feedback when you put the microphone in front of a speaker and the sound gets uncontrollably loud (you have probably heard this unpleasant effect).

4

## Types of feedback..
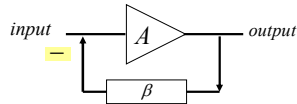
### 2. Negative Feedback

- Negative feedback is when the output is **subtracted** from the input.




- Example: Speed control.** If the car starts to speed up above the desired set-point speed, negative feedback causes the throttle to close, thereby reducing speed; similarly, if the car slows, negative feedback acts to open the throttle.
- The use of negative feedback reduces the gain. Part of the output signal is taken back to the input with a negative sign.

5

## Types of feedback..

### Negative Feedback Gain

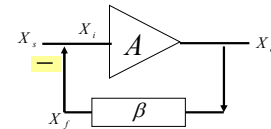

The gain with feedback (or closed-loop gain)  $A_f$  as follows:

$$X_o = A.X_i \quad X_i = X_s - X_f \quad X_f = \beta.X_o$$

$$A_f = \frac{X_o}{X_s} = \frac{A}{1 + \beta A}$$

The quantity  $\beta A$  is called the loop gain, and the quantity  $(1 + \beta A)$  is called the amount of feedback.

6

## Advantages of Negative Feedback

### 1. Stabilization of gain

- make the gain less sensitive to changes in circuit components e.g. due to changes in temperature.

### 2. Reduce non-linear distortion

- make the output proportional to the input, keeping the gain constant, independent of signal level.

### 3. Reduce the effect of noise

- minimize the contribution to the output of unwanted signals generated in circuit components or extraneous interference.

7

## Advantages of Negative Feedback....

### 4. Extend the bandwidth of the amplifier

- Reduce the gain and increase the bandwidth

### 5. Modification the input and output impedances


- raise or lower the input and output impedances by selection of the appropriate feedback topology.

## Disadvantages of Negative Feedback

1. Circuit gain - Reduce
2. Stability - Tend to be oscillate

8

### Feedback Amplifier Topologies

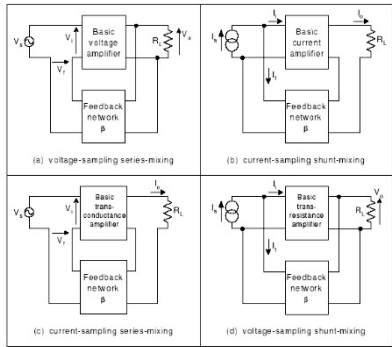

9

### Feedback Topologies

#### Feedback relationship

	Gain	Input resistance	Output resistance
Without feedback	$A$	$R_i$	$R_o$
Series-shunt	$A_f = \frac{A}{1 + \beta A}$	$R_{if} = R_i (1 + \beta A)$	$R_{of} = \frac{R_o}{1 + \beta A}$
Series-series	$A_f = \frac{A}{1 + \beta A}$	$R_{if} = R_i (1 + \beta A)$	$R_{of} = R_o (1 + \beta A)$
Shunt-shunt	$A_f = \frac{A}{1 + \beta A}$	$R_{if} = \frac{R_i}{1 + \beta A}$	$R_{of} = \frac{R_o}{1 + \beta A}$
Shunt-series	$A_f = \frac{A}{1 + \beta A}$	$R_{if} = \frac{R_i}{1 + \beta A}$	$R_{of} = R_o (1 + \beta A)$

10